


# **CPT\_S 260 Intro to Computer Architecture**

## **Lecture 29**


**Single Cycle MIPS Control**  
**March 28, 2022**

**Ganapati Bhat**  
**School of Electrical Engineering and Computer Science**  
**Washington State University**


# Recap: Branch Instructions

 

# Recap: R-Type/Load/Store Datapath

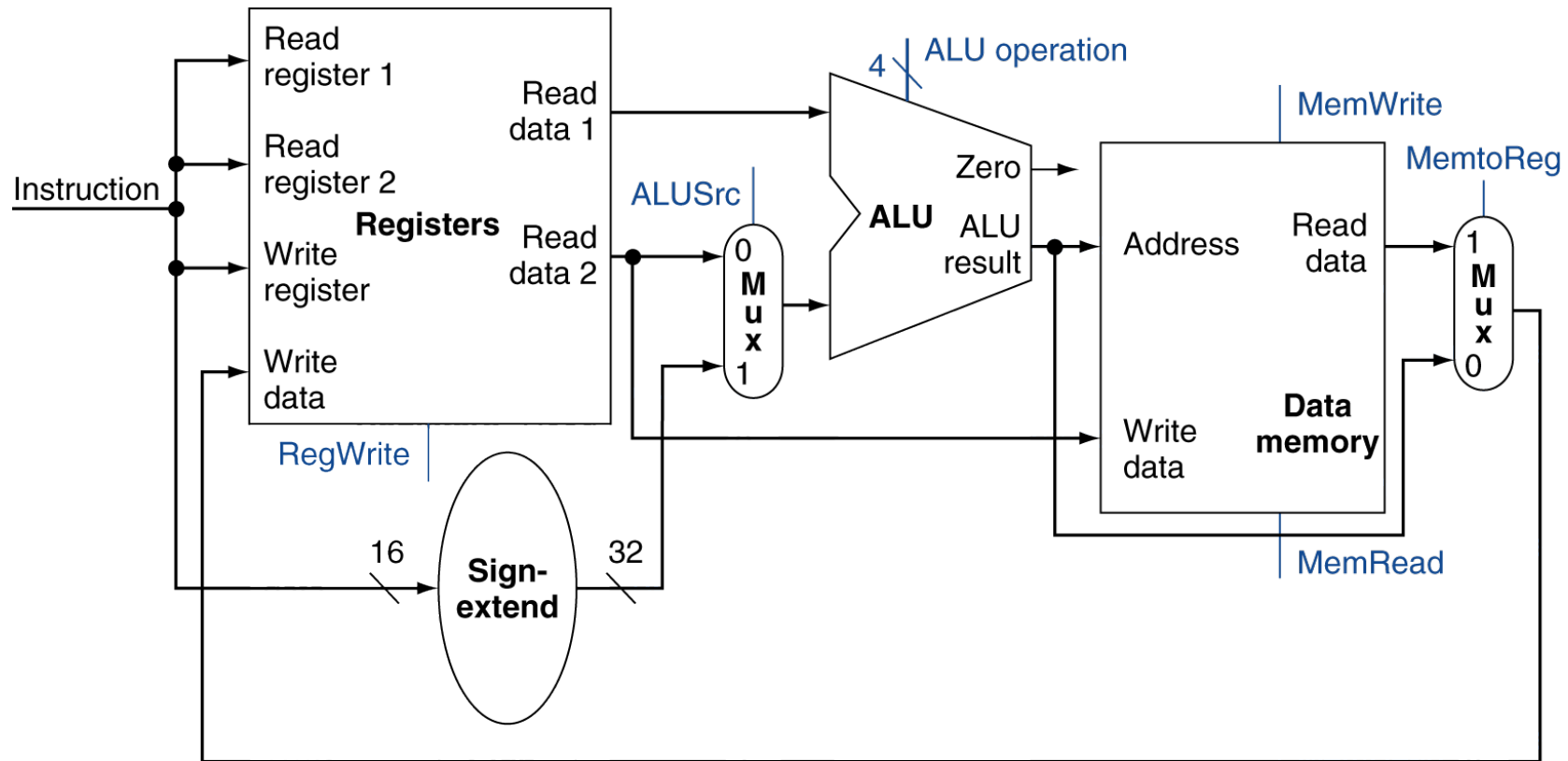


# Recap: Full Datapath

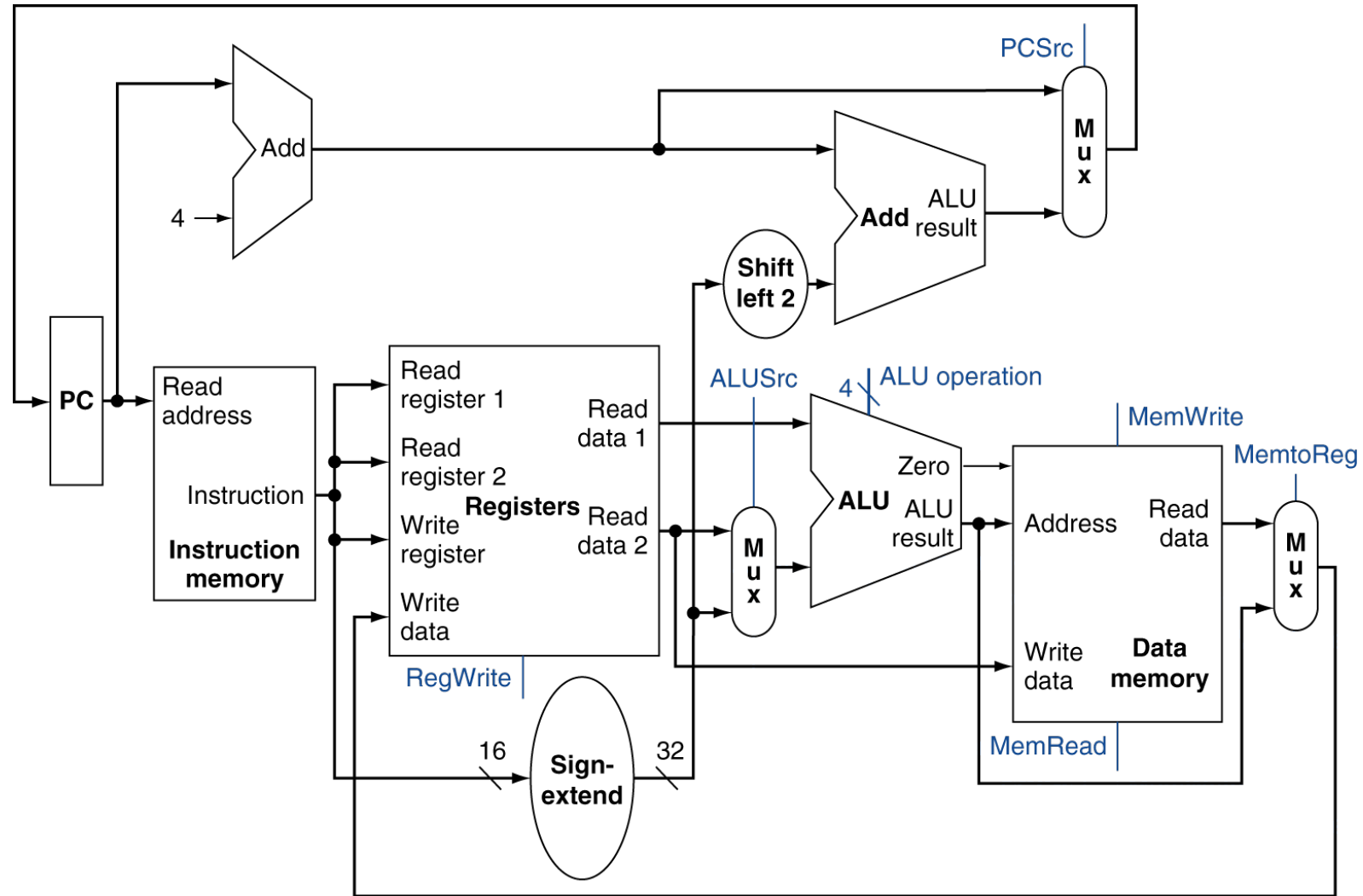

# Recap: ALU Control
 
## ▪ ALU used for


- Load/Store: F = add
- Branch (e.g., beq): F = subtract
- R-type: F depends on funct field




ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set-on-less-than
1100	NOR
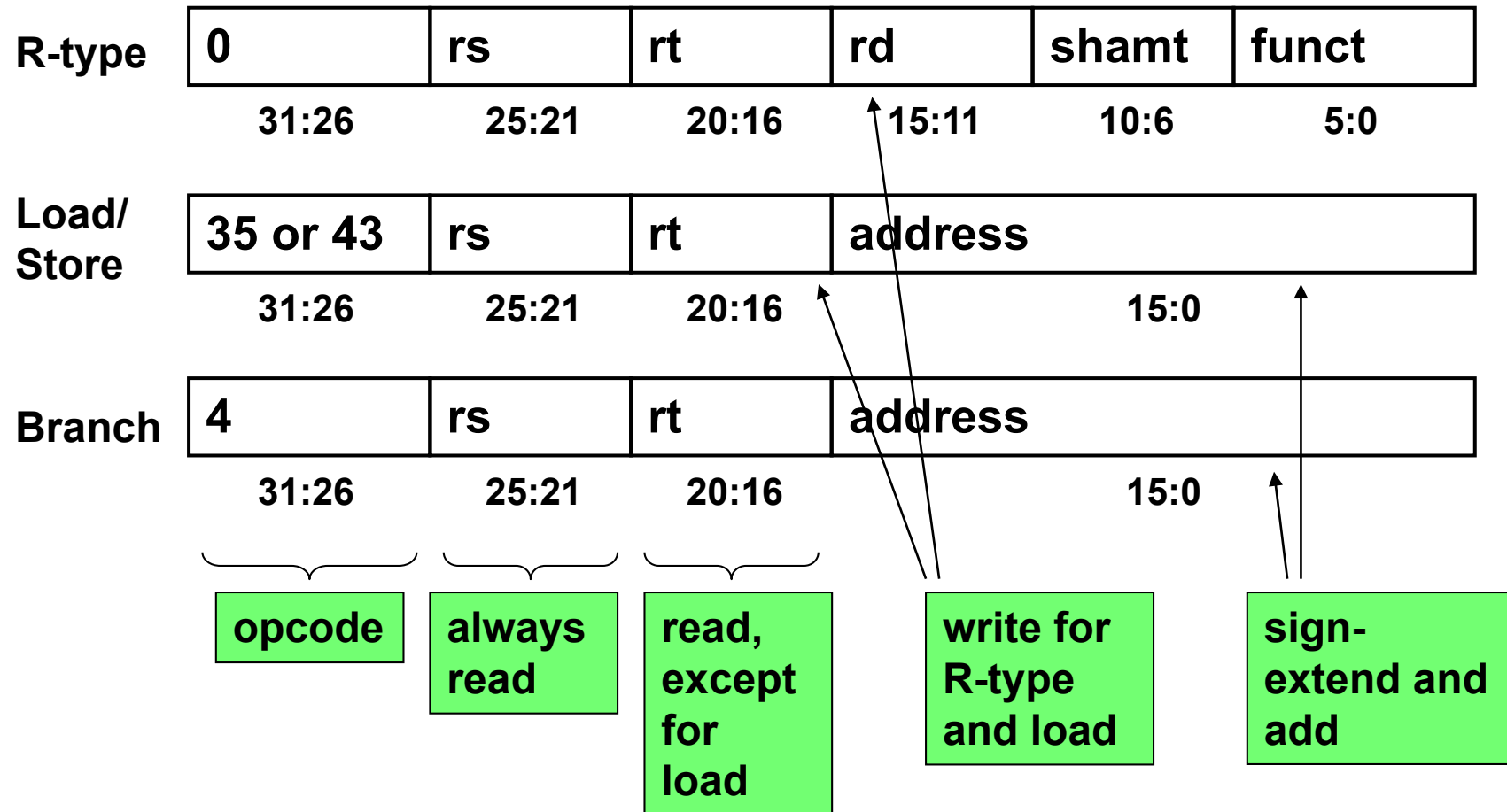
# The Main Control Unit


- Control signals derived from instruction



# Datapath with Control

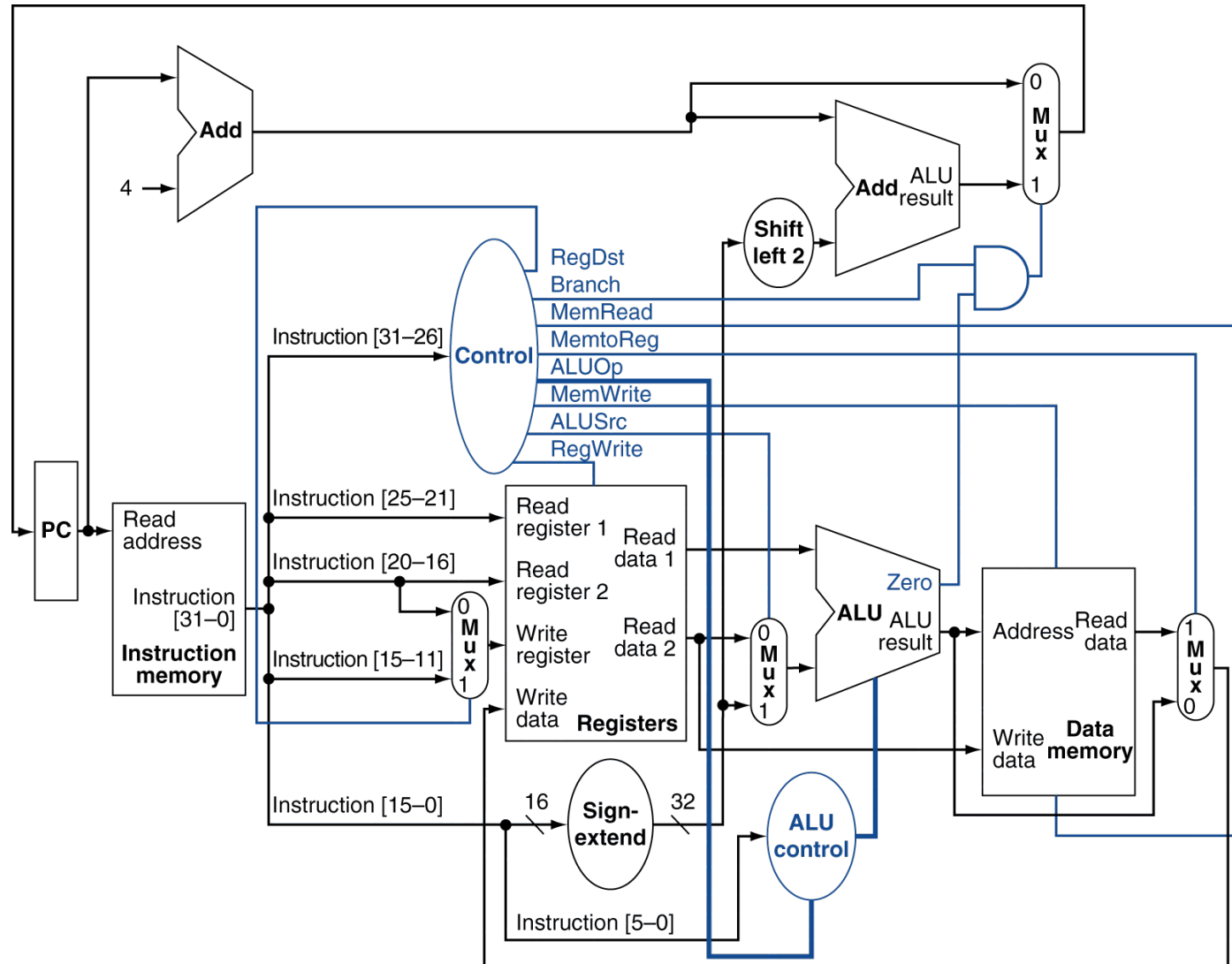


# R-Type Instruction

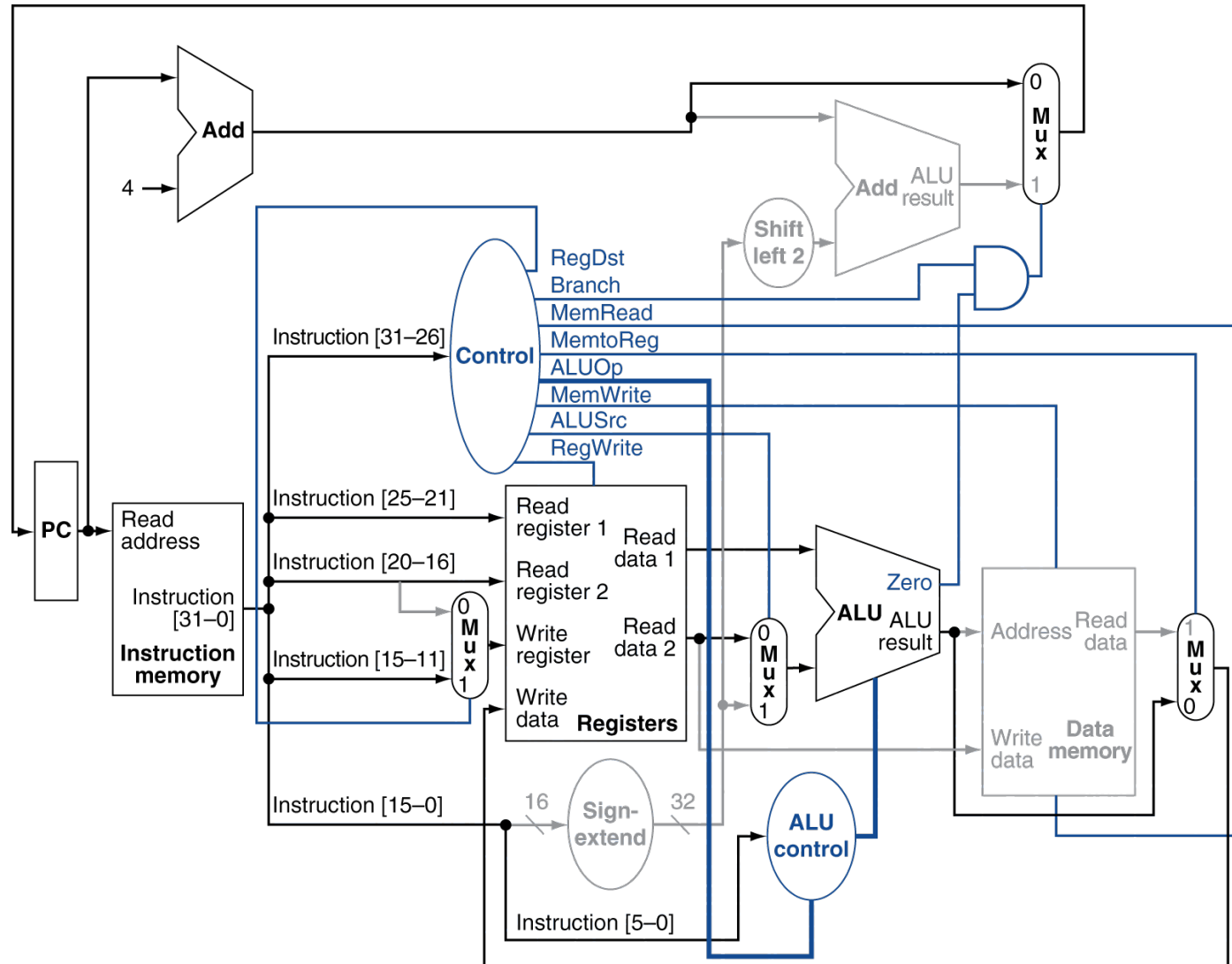





# Load Instruction

 


# Branch Instructions

 

# BEQ Instruction

 


# Implementing Jumps

 

- **Jump uses word address**
- **Update PC with concatenation of**
  - Top 4 bits of old PC + 26-bit jump address + 00
- **Need an extra control signal decoded from opcode**

# Datapath with Jumps Added

 

# Performance Issues

---

- **Longest delay determines clock period**
  - Critical path: load instruction
  - Instruction memory → register file → ALU → data memory → register file
- **Not feasible to vary period for different instructions**
- **Violates design principle**
  - Making the common case fast
- **We will improve performance by pipelining**

# Example 1

---

**8.** [5 points] In the snippet of MIPS assembler code below, how many times is instruction memory accessed? How many times is data memory accessed? (Count only accesses to memory, not registers.)

```
lw $v1, 0($a0)
addi $v0, $v0, 1
sw $v1, 0($a1)
addi $a0, $a0, 1
```

## Example #2: True/False Question

---

- The 'beq' instruction always modifies the program counter register (PC).
  - True
  - $PC = PC + 4$  even if  $r1 \neq r2$
  - PC always advances (PC+4) during execution of this instruction.



## Example #3: True/False Question

---

- The 'add' instruction does not modify the PC.
  - False
  - $PC = PC + 4$
  - PC always advances (PC+4) during execution of this instruction.

## Example #4: True/False Question

---

- The 'jal' instruction always modifies the PC.
  - True
  - The 'jal' instruction is an 'unconditional branch'. Thus, the PC should be modified to include target branch address.

## Example #5: True/False Question


---

- The instruction 'beq \$1,\$2,1' will advance the PC by one word if [\$1]=[\$2]. (note: [] indicates content of the register)
  - False
  - $PC = PC + 4 + 4 \times 1$
  - The PC will change to  $PC + 4 + 4 \times 1$  which is not essentially one word (4 bytes) change.

**This example focuses on MIPS single cycle architecture discussed before!**

**This example continues on next slide (parts c,d,e,f)!**

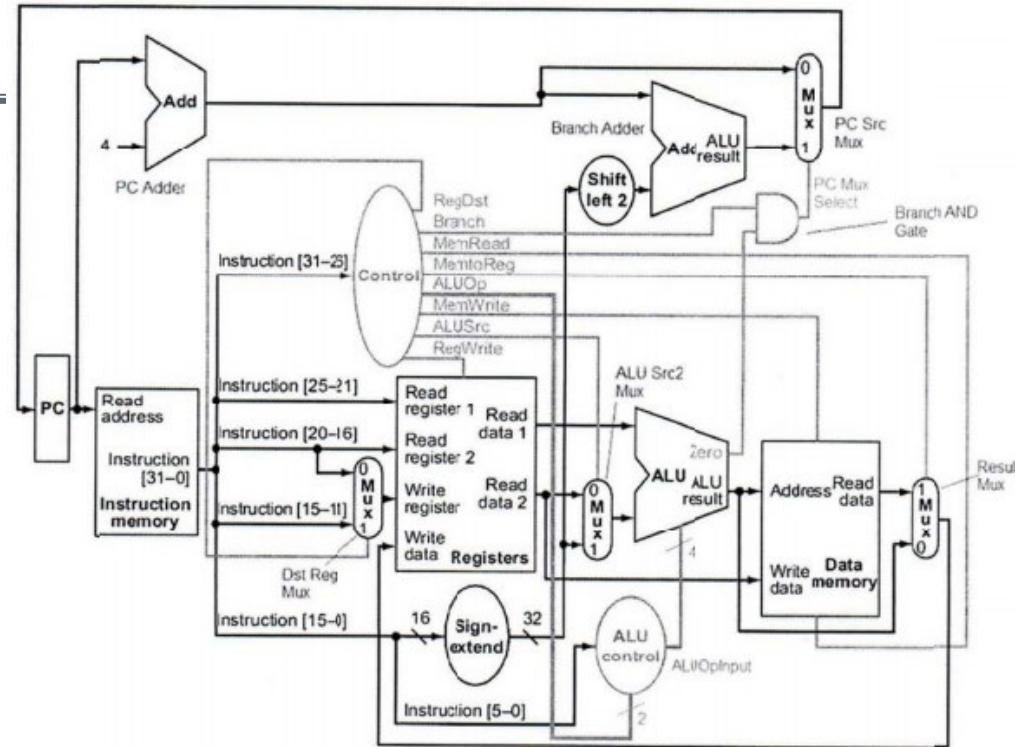1. Consider the following simple single cycle MIPS architecture, which is the same architecture discussed in the class.



- a. What is the value (i.e., '0', '1', 'x') of each one of the following control signals during execution of 'ADD' instruction?

```
RegDst = 1
Branch = 0
MemtoReg = 0
AluSrc = 0
```

```
Jump = 0
MemRead = 0
MemWrite = 0
RegWrite = 1
```

- b. What is the value (i.e., '0', '1', 'x') of each one of the following control signals during execution of 'J' instruction?

RegDst = 0  
Branch = X  
MemtoReg = 0  
AluSrc = 0

```

Jump = 1
MemRead = 0
MemWrite = 0
RegWrite = 0

```

# Example #6

Continued from previous slide! (single cycle MIPS architecture)

- c. What is the value (i.e., '0', '1', 'x') of each one of the following control signals during execution of 'BEQ' instruction?

RegDst = x  
Branch = 1  
MemtoReg = x  
AluSrc = 0

Jump = 0  
MemRead = 0  
MemWrite = 0  
RegWrite = 0

- d. What is the value (i.e., '0', '1', 'x') of each one of the following control signals during execution of 'SW' instruction?

RegDst = x  
Branch = 0  
MemtoReg = x  
AluSrc = 1

Jump = 0  
MemRead = 0  
MemWrite = 1  
RegWrite = 0

- e. Assume instruction "J 1012d" is located in address 1000d (i.e., address 1000 decimal) in the instruction memory. What is the value of PC in decimal after this instruction is executed.

J address (Instruction[25-0]):

J 1012d → 012d = 00...0111110100

We shift left the above number by 2:

00...011111010000

Finally, we should concatenate the four most significant bit of this value:

PC + 4 = 1004d → 00...011111010000 → four most significant bits are '0000'

PC<sub>new</sub> = 0000 00...011111010000 = 4048d

- f. Assume instruction "BEQ \$t1, \$t2, 10d" is located in address 1000d (i.e., address 1000 decimal) in the instruction memory. We also know that \$t1 = 10d, and \$t2 = 10d. What is the value of PC in decimal after this instruction is executed.

For BEQ, we should check the condition, if it is true (as it here), we should calculate the new value for PC using the relative PC addressing:

PC<sub>new</sub> = Sign-extend (branch address) ≤ 2 + (PC<sub>old</sub> + 4)

branch address = 10d = 00...01010  
shift left by 2 → 00...010100  
sign-extend → 00...01010

PC + 4 = 1004d = 00...01111101100

PC<sub>new</sub> = 00...01010 + 00...01111101100 = 1044d

**This example continues on next slide!**

- 

<b>R</b>	opcode	rs	rt	rd	shamt	funct
	31 26 25	21 20	16 15	11 10	6 5	
<b>I</b>	opcode	rs	rt	immediate		
	31 26 25	21 20	16 15			
<b>J</b>	opcode	address				
	31 26 25					



# Example #7

Continued from previous slide!

- a. Assume that the following instruction is in the datapath to execute. The instruction is located in address 1000d (i.e., address 1000 decimal) in the instruction memory. We also know that \$t1 = 10d, and \$t2 = 24d.

BEQ \$t1, \$t2, 10

- What is the value of PC after this instruction is executed.
- What is the value of selection pin for each multiplexer in the datapath (0 or 1). The MUXs are labeled as M1, M2, M3, and M4.

Condition is not right  $\Rightarrow$  Branch is not taken  $\Rightarrow$

$\Rightarrow PC \rightarrow PC + 4$

$1000d + 4d = 1004d = 1111101100b$

BEQ is an I-type Instruction

inst(25-20) = rs  $\Rightarrow$  M1 selection is 0

inst(20-16) = rt

ALU operation is subtraction of \$t1 and \$t2  $\Rightarrow$  M2 sel is 0

Branch is not taken  $\Rightarrow$  M3, M4 should take PC+4 as the next value of PC  $\Rightarrow$  M3, M4 sel's should be 0 (both)

- b. Specify the value of each control signal listed in the following table during execution of each instruction listed in the first column.

Instruction	RegDst	Branch	MemRead	MemtoReg	MemWrite	AluSrc	RegWrite
add \$9, \$7, \$8	1	0	0	0	0	0	1
lw \$5, 10(\$8)	0	0	1	1	0	1	1
sw \$4, 0(\$3)	X	0	0	X	1	1	0