

CPT_S 260 Intro to Computer Architecture

Lecture 22

Digital Design I
March 2, 2022


Ganapati Bhat
School of Electrical Engineering and Computer Science
Washington State University

Topics Covered

- **Performance of the computer**
 - Instruction Count
 - Clock Cycle Time
 - Clock Cycle Instruction (CPI)
- **Instruction Set Architecture (MIPS)**
- **We will now construct the datapath and control unit (CU) that connects the previous two topics together**
 - Sequential processor that implements all MIPS instructions

Digital System

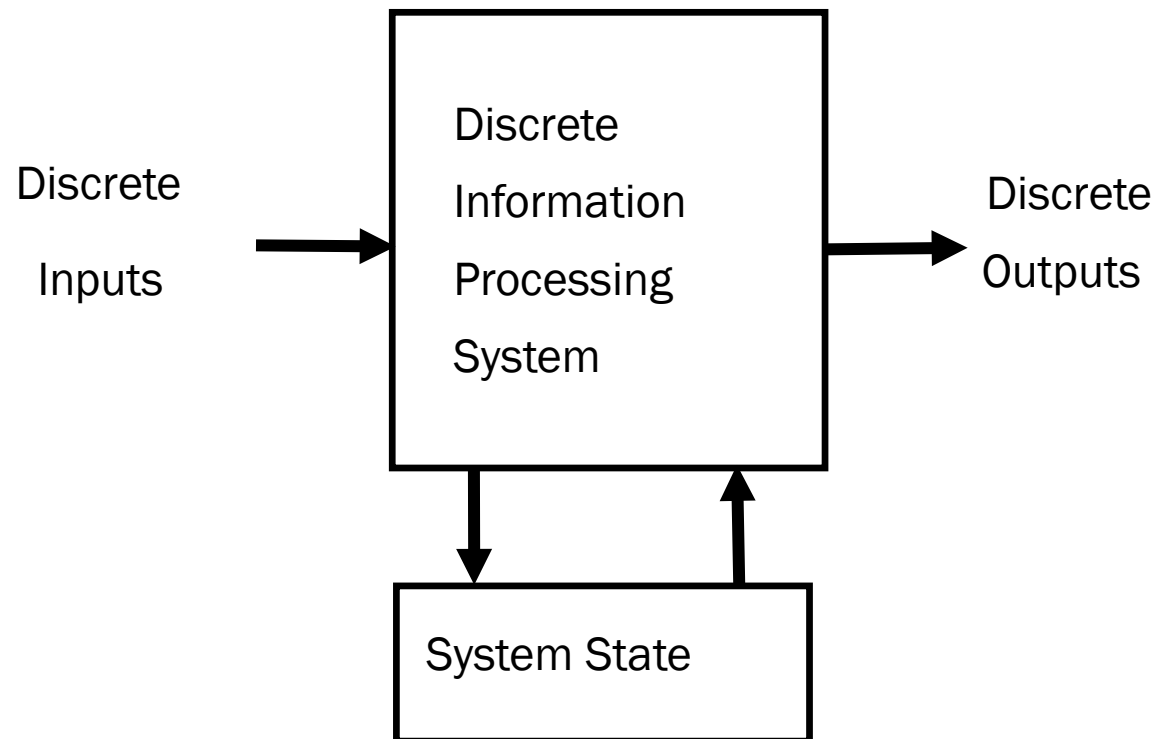- Takes a set of discrete information inputs and discrete internal information (system state) and generates a set of discrete information outputs.



Types of Digital Systems

- **No state present**

- Combinational Logic System
- $\text{Output} = \text{Function}(\text{Input})$

- **State present**

- State updated at discrete times
 - » Synchronous Sequential System
- State updated at any time
 - » Asynchronous Sequential System
- $\text{State} = \text{Function}(\text{State}, \text{Input})$
- $\text{Output} = \text{Function}(\text{State})$ or $\text{Function}(\text{State}, \text{Input})$

Logic Design Basics

- **Information encoded in binary**
 - Low voltage = 0, High voltage = 1
 - One wire per bit
 - Multi-bit data encoded on multi-wire buses
- **Combinational element**
 - Operate on data
 - Output is a function of input
- **State (sequential) elements**
 - Store information


Signal

- **An information variable represented by physical quantity**
- **For digital systems, the variable takes on discrete values.**
- **Two level, or binary values are the most prevalent values in digital systems.**
- **Binary values are represented abstractly by:**
 - digits 0 and 1
 - words (symbols) False (F) and True (T)
 - words (symbols) Low (L) and High (H)
 - and words On and Off
- **Binary values are represented by values or ranges of values of physical quantities**


Signal Examples

- Analog signals are continuous in nature, whereas digital signals are discrete

Analog Signal

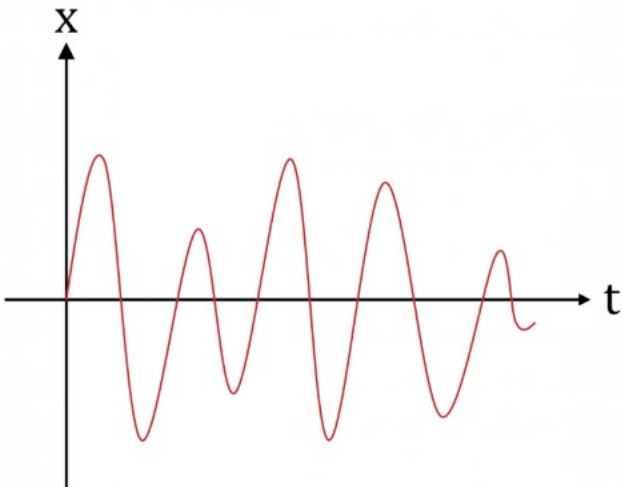

Digital Signal

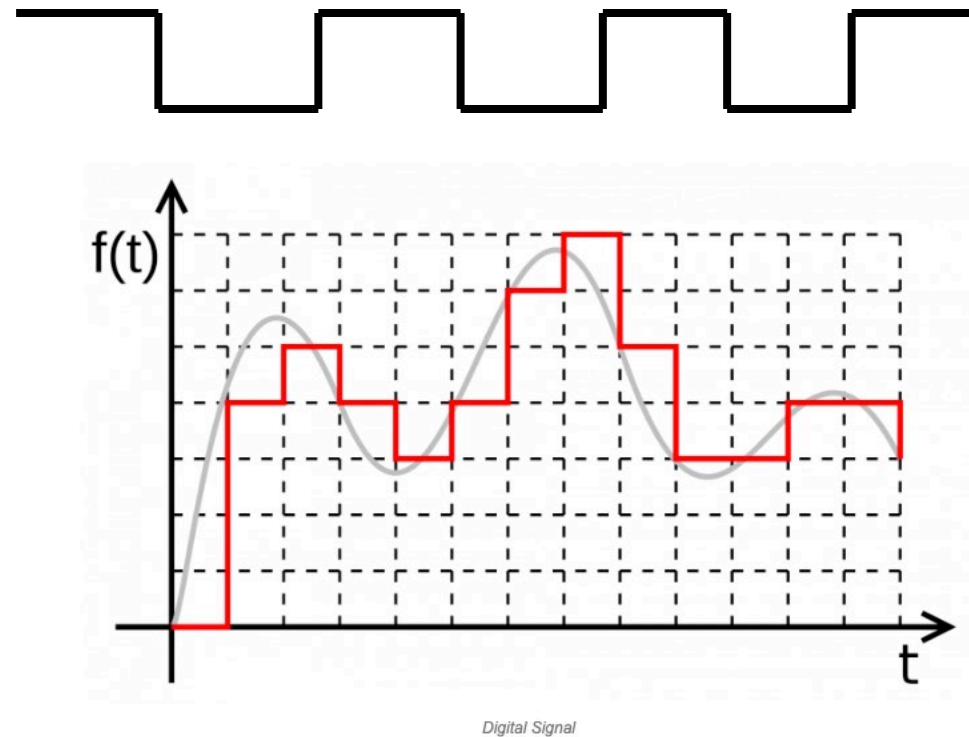

Basic Logic Gates

- **NOT, AND, and OR Gates**
- **NAND and NOR Gates**
- **Exclusive-OR (XOR) Gate**

Truth Tables


- *Truth table* – a tabular listing of the values of a function for all possible combinations of values on its arguments
- Example: Truth tables for the basic logic operations:

AND		
X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

OR		
X	Y	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1


NOT	
X	$Z = \overline{X}$
0	1
1	0

NOT Gate -- Inverter

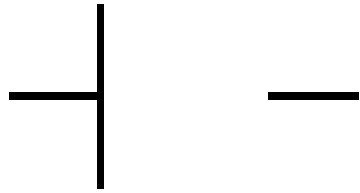


X	Y
0	1
1	0

AND Gate

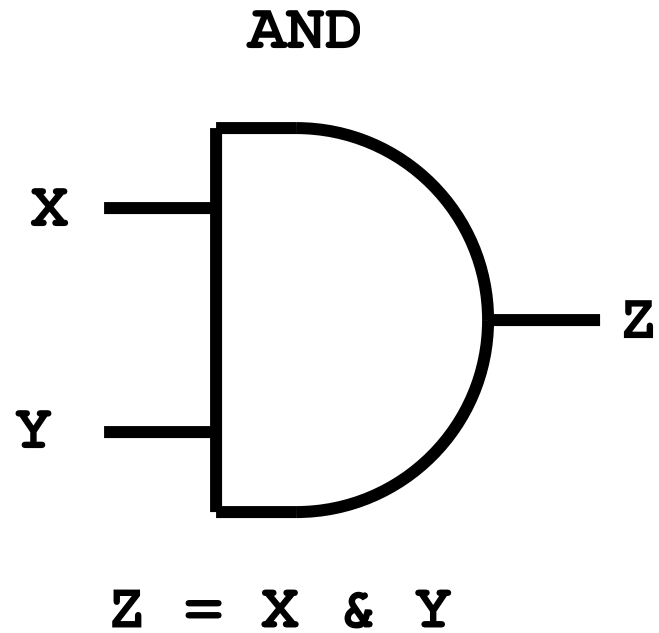

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1


OR Gate

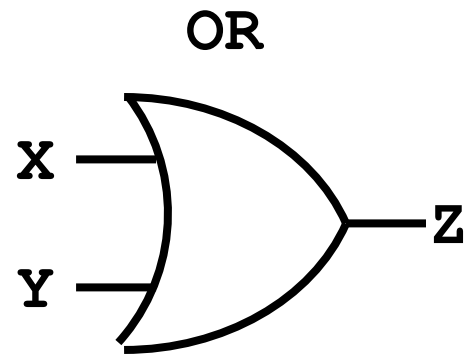

$$Z = X \mid Y$$

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

NAND Gate

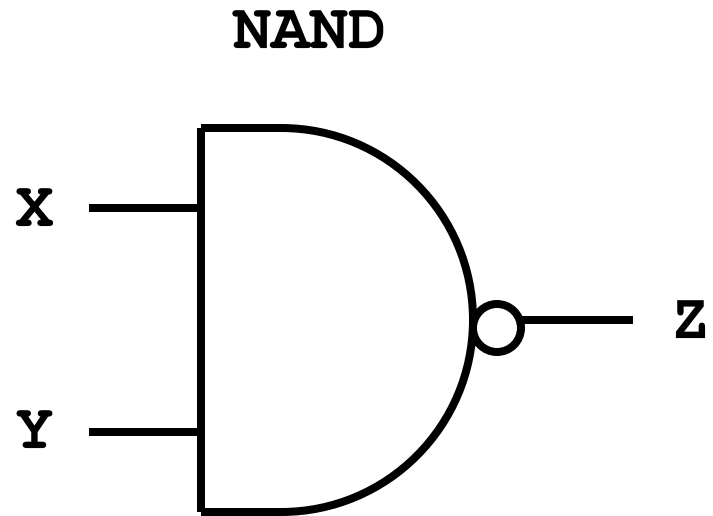


$$Z = \sim (X \& Y)$$

`nand(Z,X,Y)`

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0


NAND Gate

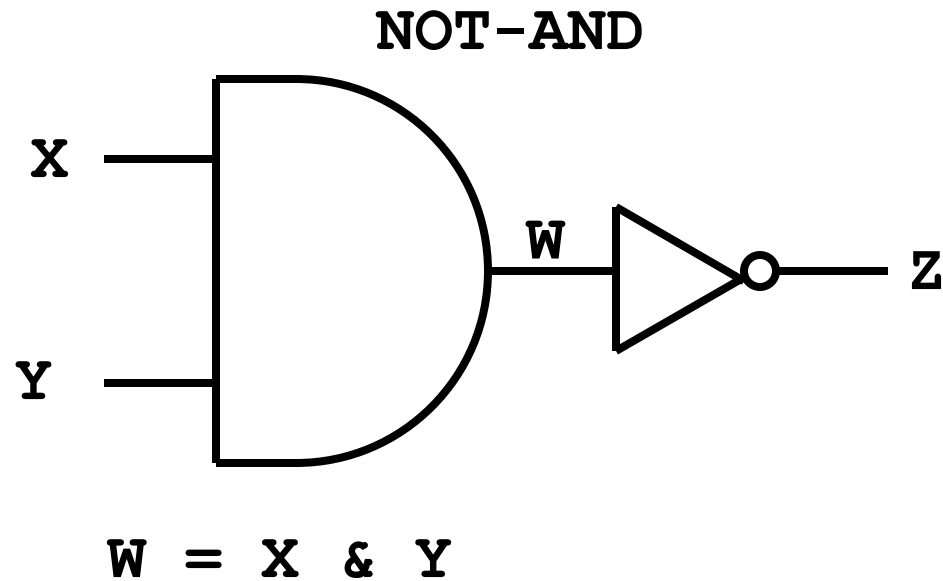

X	Y	W	Z
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

$$Z = \sim W = \sim (X \& Y)$$

NOR Gate

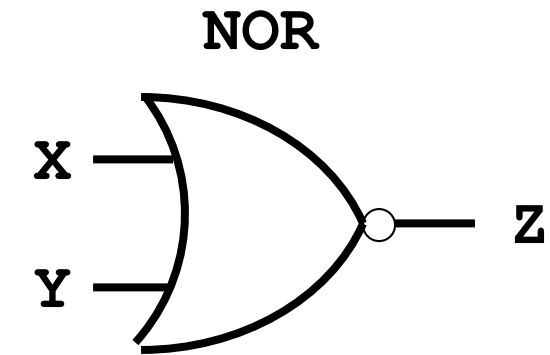


$$Z = \sim (X \mid Y)$$

`nor(Z,X,Y)`

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

NOR Gate

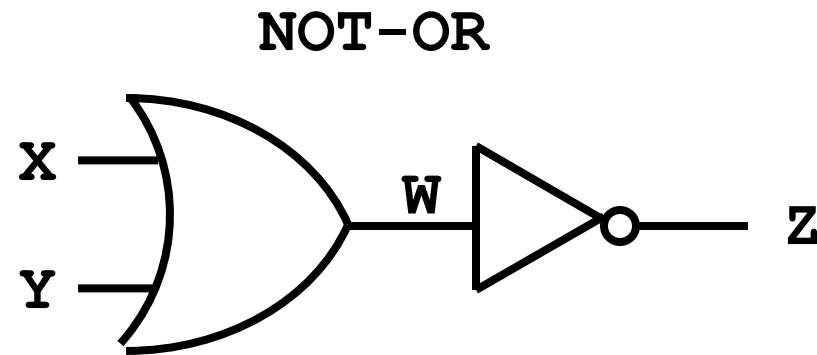


$$W = X \mid Y$$

$$Z = \sim W = \sim (X \mid Y)$$


X	Y	W	Z
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

NAND and NOR

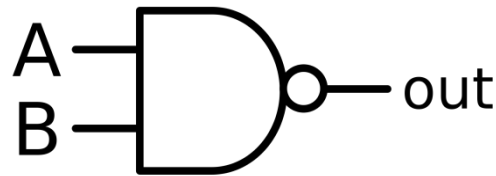- NAND : NOT of AND : $A \text{ nand } B = \overline{A \cdot B}$
- NOR : NOT of OR : $A \text{ nor } B = \overline{A + B}$
- NAND and NOR are *universal gates*, i.e., they can be used to construct any complex logical function




NAND

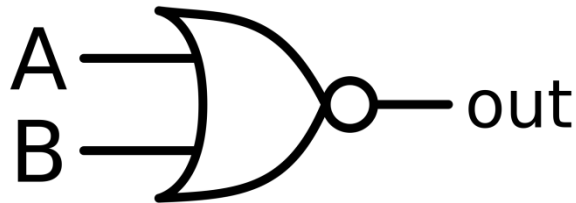

NOR


Exclusive-OR Gate

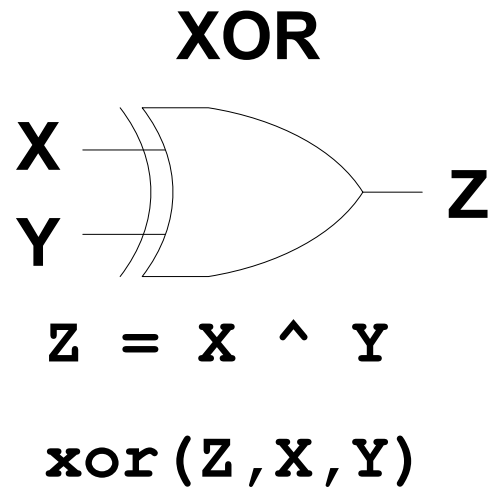

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

Stateless (Combinational) Digital Circuits

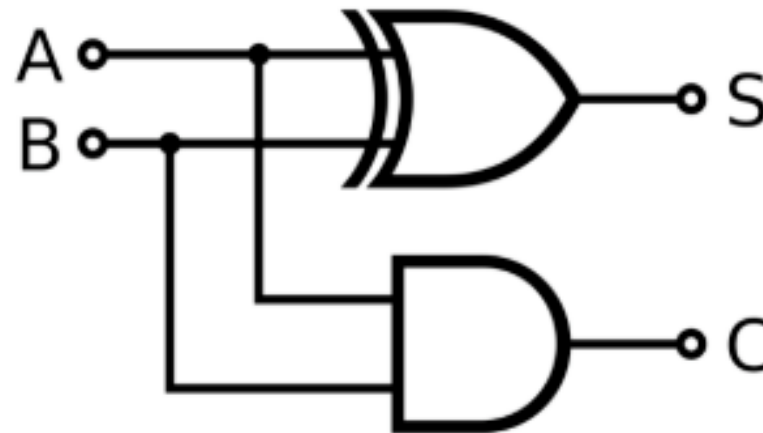- This Circuit does not have an internal state. The signals simply flow left to right, from inputs to outputs.




- $S = \neg(A \vee B)$
- $C = A \wedge B$

Combinational Elements


- AND Gate

- $Y = A \& B$

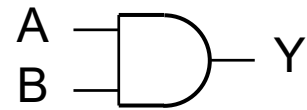


- Adder

- $Y = A + B$

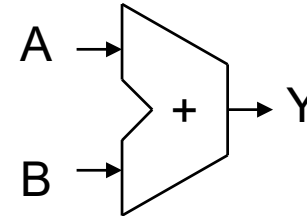


- Multiplexer

- $Y = S ? I1 : I0$

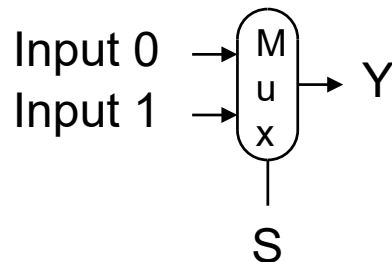


- Arithmetic/Logic Unit

- $Y = F(A, B)$

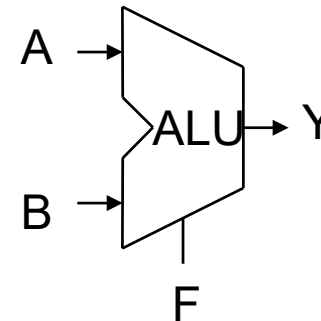


NAND and NOR

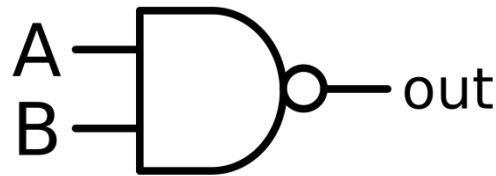- NAND : NOT of AND : $A \text{ nand } B = \overline{A \cdot B}$
- NOR : NOT of OR : $A \text{ nor } B = \overline{A + B}$
- NAND and NOR are *universal gates*, i.e., they can be used to construct any complex logical function



NAND

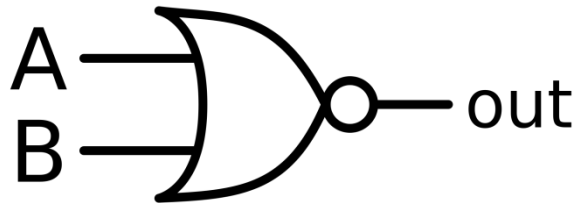

NOR

Types of Digital Systems

- **No state present**


- Combinational Logic System
- $\text{Output} = \text{Function}(\text{Input})$

- **State present**

- State updated at discrete times
 - » Synchronous Sequential System
- State updated at any time
 - » Asynchronous Sequential System
- $\text{State} = \text{Function}(\text{State}, \text{Input})$
- $\text{Output} = \text{Function}(\text{State})$ or $\text{Function}(\text{State}, \text{Input})$

Stateful (Sequential) Digital Circuits

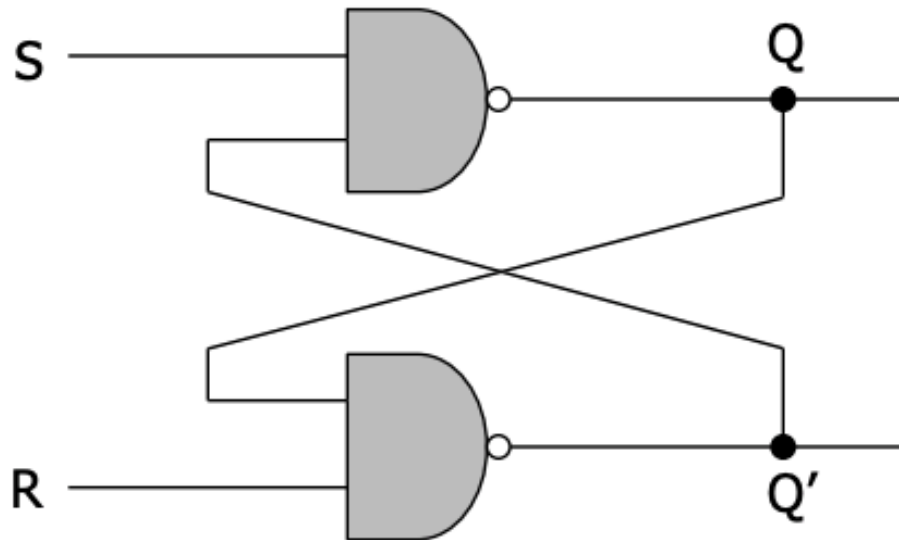- This circuit utilizes one of the wire loops from the right to the left providing feedback
- “flip flop” building blocks to preserve state.




R-S Latch


Input		Output
R	S	Q
1	1	Q_{prev}
1	0	1
0	1	0
0	0	Invalid

Synchronous vs Asynchronous

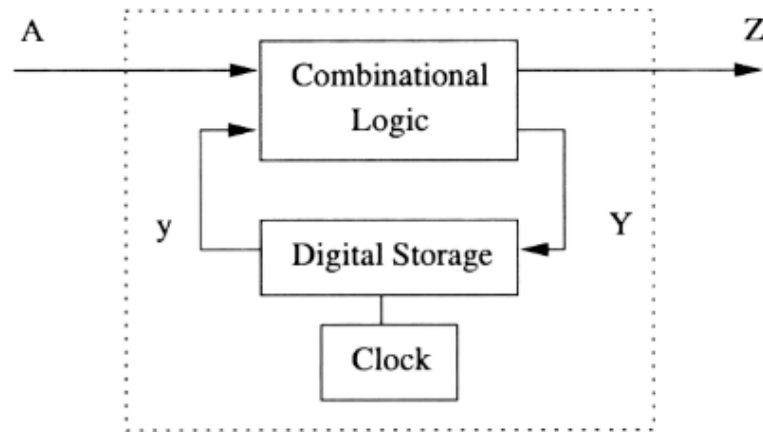
- Synchronizing periodic clock connected to the clock inputs of all the memory elements of the circuit, to synchronize all internal changes of state.



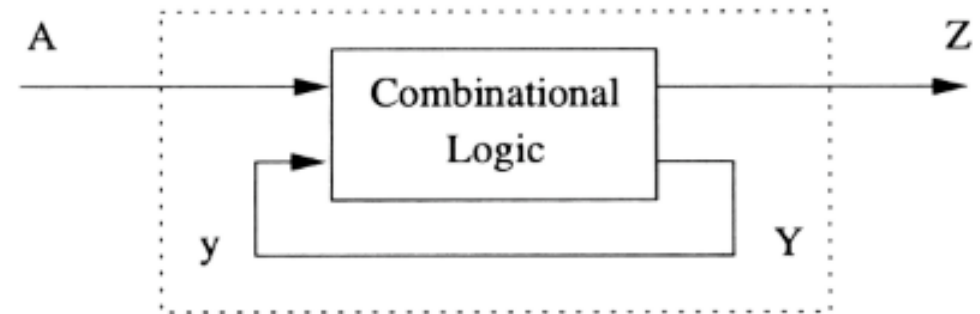- *asynchronous* if it does not employ a periodic clock signal C to synchronize its internal changes of state.
- Therefore the state changes occur in direct response to signal changes on primary (data) input lines,



A Digital Computer Example

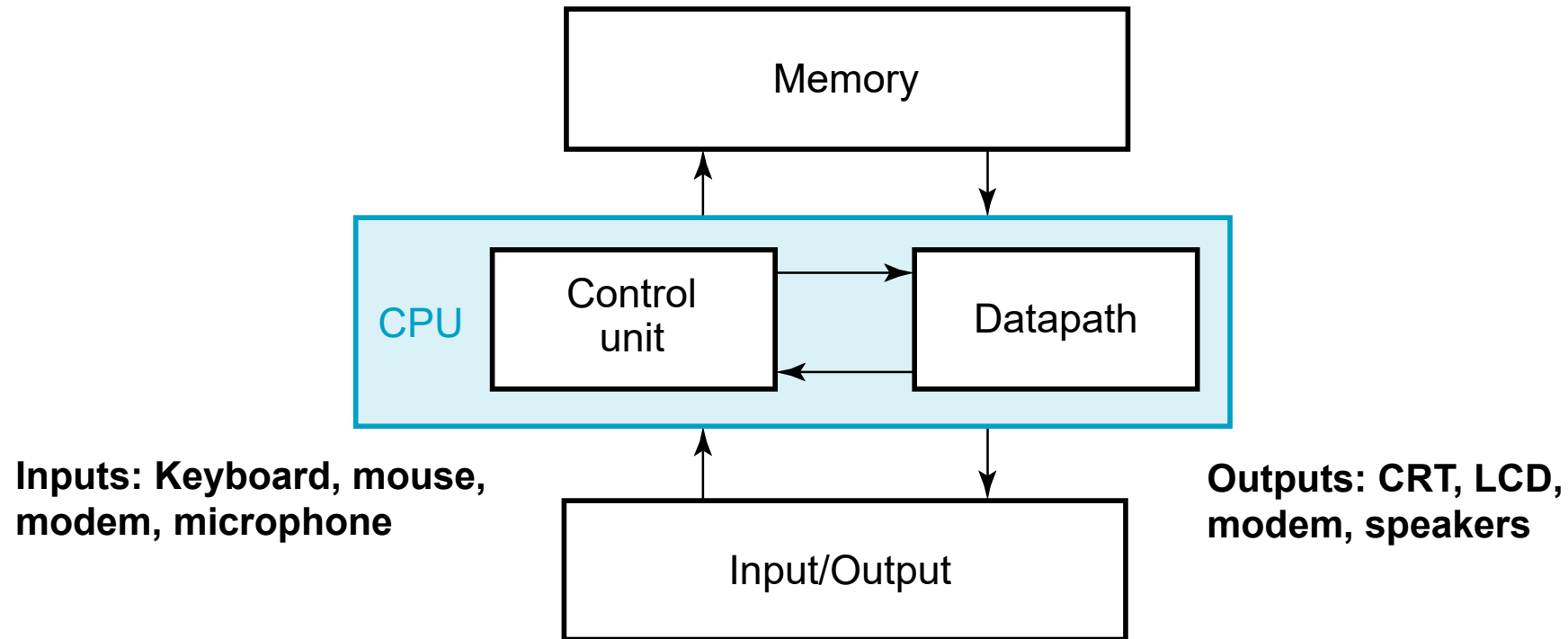

We will look into this model in more details later in this course ...

Checkpoint – Truth tables

- $S = (A + B) \cdot (\bar{A} + \bar{B})$

- $C = A \cdot B$

