

CPT_S 260 Intro to Computer Architecture

Lecture 30

Exam 2 Review
March 30, 2022


Ganapati Bhat
School of Electrical Engineering and Computer Science
Washington State University

2-to-1-Line Multiplexer



- Since $2 = 2^1$, $n = 1$
- The single selection variable S has two values:
 - $S = 0$ selects input I_0
 - $S = 1$ selects input I_1
- The equation:

$$Y = \bar{S}I_0 + SI_1$$

- The circuit:

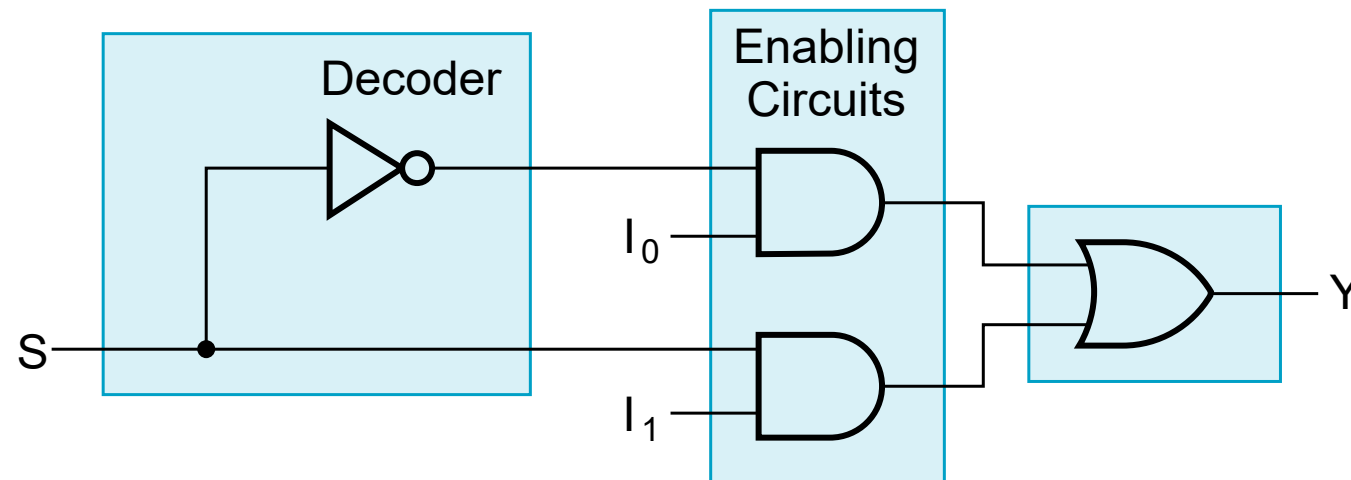

Decoder

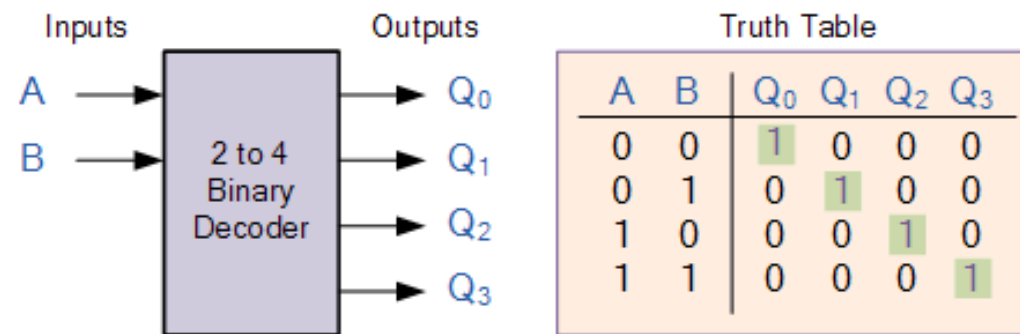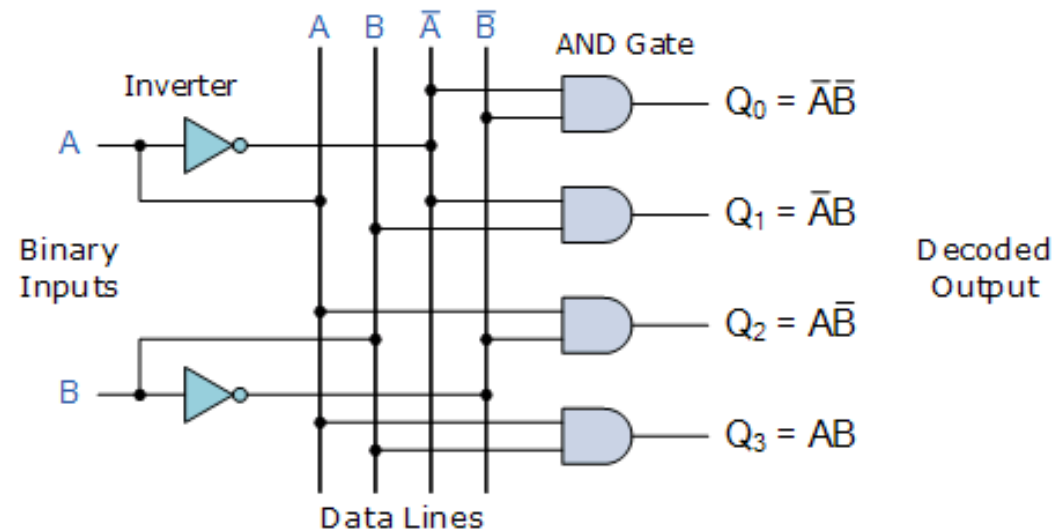

Rules of Boolean Algebra

- **Associative Law of multiplication**

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

- **Distributive Law of multiplication**

$$A + BC = (A + B) \cdot (A + C)$$

- **Annulment law:**

$$A \cdot 0 = 0$$

$$A + 1 = 1$$

- **Identity law:**

$$A \cdot 1 = A$$

$$A + 0 = A$$

Rules of Boolean Algebra

- **Complement law:**

$$\begin{aligned}A + \bar{A} &= 1 \\A \cdot \bar{A} &= 0\end{aligned}$$

- **Double negation law:**

$$\bar{\bar{A}} = A$$

- **Absorption law:**

$$\begin{aligned}A \cdot (A + B) &= A \\A + AB &= A \\A + \bar{A}B &= A + B\end{aligned}$$



- **Idempotent law:**

$$\begin{aligned}A + A &= A \\A \cdot A &= A\end{aligned}$$

De Morgan's Laws

- Transformation rules that help simplification of negations
- Statement:
  
$$\overline{AB} = \bar{A} + \bar{B}$$
$$\overline{(A + B)} = \bar{A} \cdot \bar{B}$$



Sum of Products

- **Minterm Expressions**
- If input is 0 we take the complement of the variable
- If input is 1 we take the variable as is
- To get the desired canonical SOP expression we will add the minterms (product terms) for which the output is 1

$$F = \bar{A}B + A\bar{B} + AB$$

A	B	F	Minterm
0	0	0	A'B'
0	1	1	A'B
1	0	1	AB'
1	1	1	AB


Product of Sums

- **Maxterm Expressions**
- If input is 1, we take the complement of the variable
- If input is 0, we take the variable as is
- To get the desired canonical POS expression we will multiply the maxterms (sum terms) for which the output is 0

$$F = (A + B) \cdot (\bar{A} + \bar{B})$$



A	B	F	Minterm
0	0	0	A'B'
0	1	1	A'B
1	0	1	AB'
1	1	1	AB

1-bit ALU



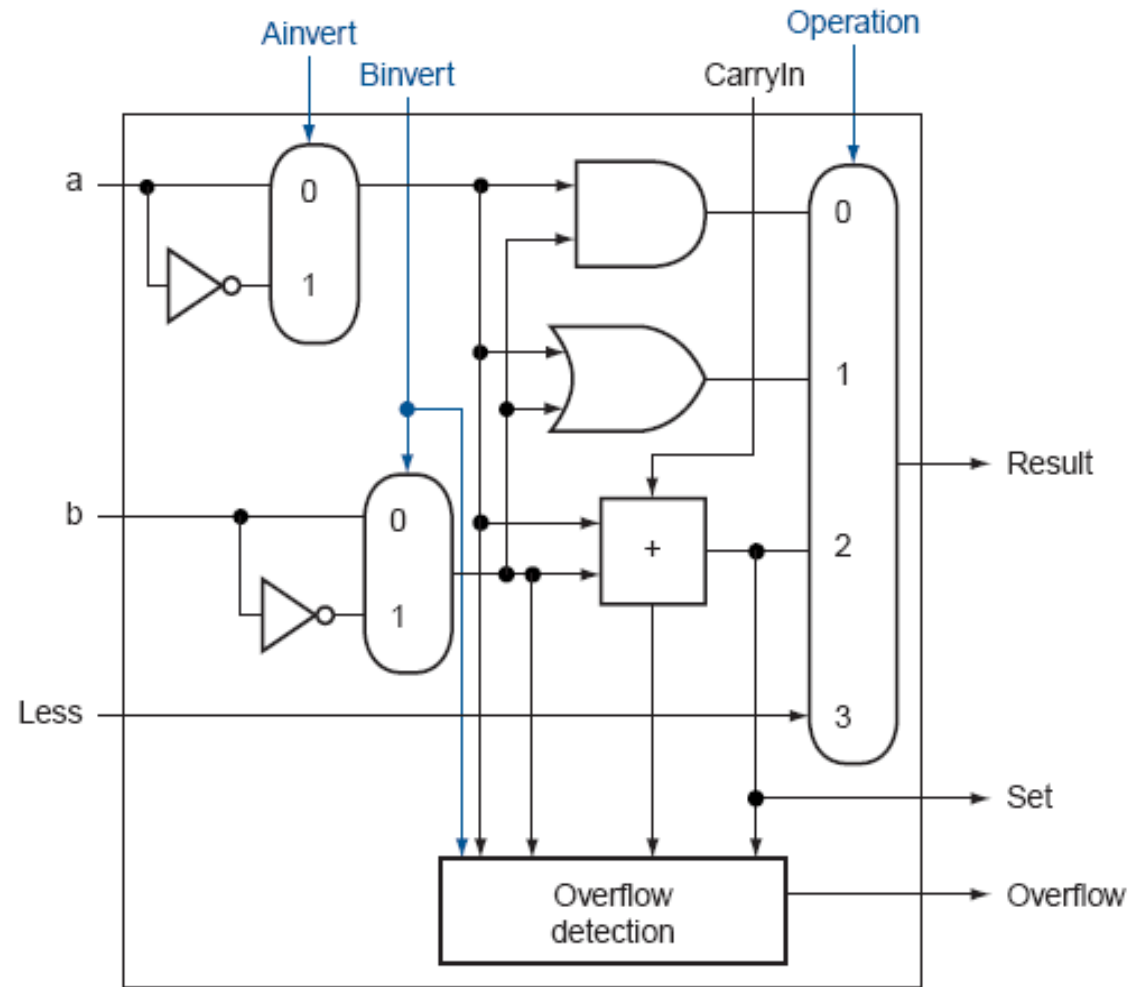


Sequential Elements

  - **Flip flops: stores data in a circuit**
 - Uses a clock signal to determine when to update the stored value
 - Edge-triggered: update when Clk changes from 0 to 1





Clocking Sequence

   

Clocking Methodology

  - **Combinational logic transforms data during clock cycles**
 - Between clock edges
 - Input from state elements, output to state element
 - Longest delay determines clock period



MIPS Datapath

