


# **CPT\_S 260 Intro to Computer Architecture**

## **Lecture 36**


**Pipeline Datapath**  
**April 13, 2022**

**Ganapati Bhat**  
**School of Electrical Engineering and Computer Science**  
**Washington State University**


# Pipelined MIPS Datapath

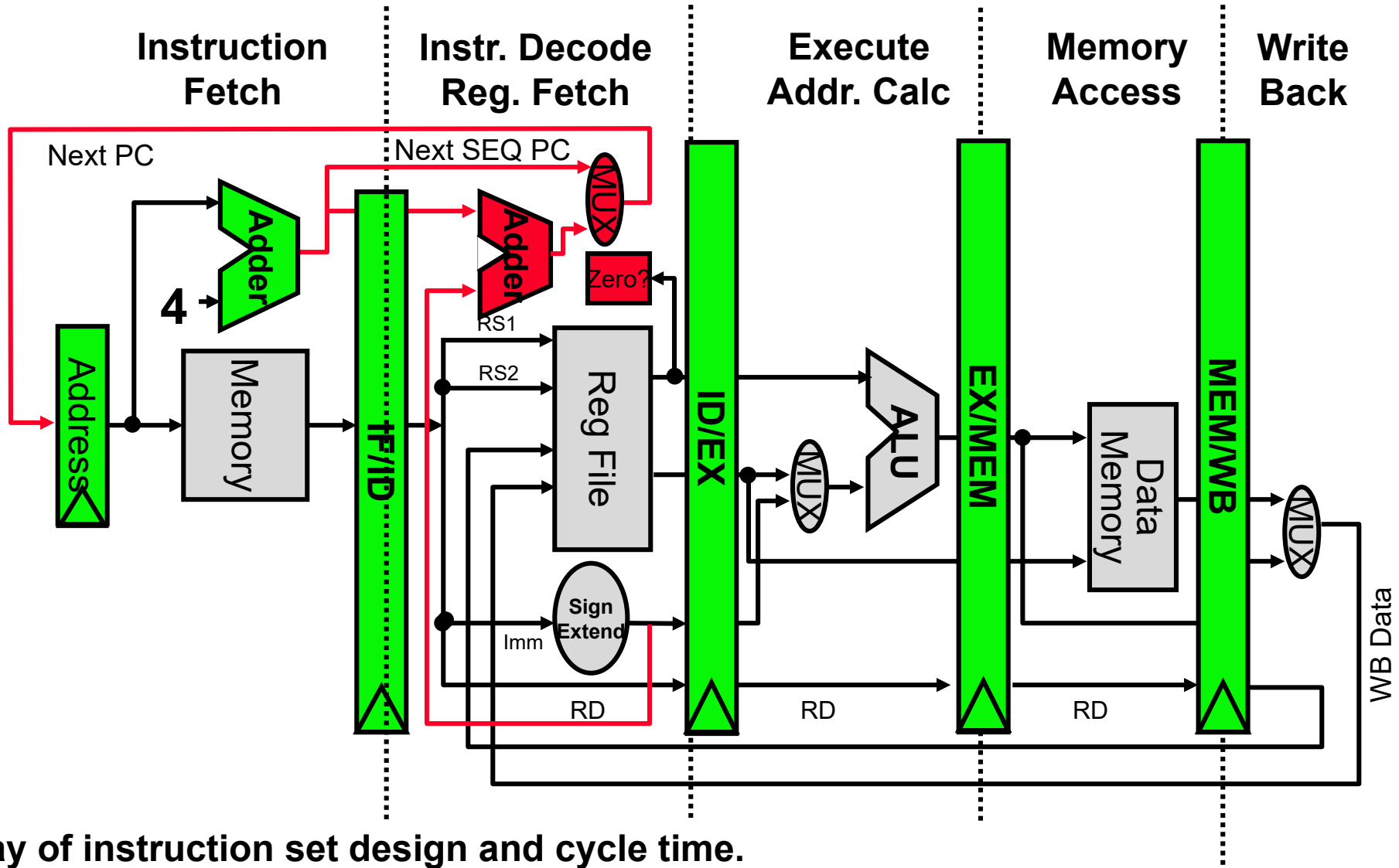


# WB for Load

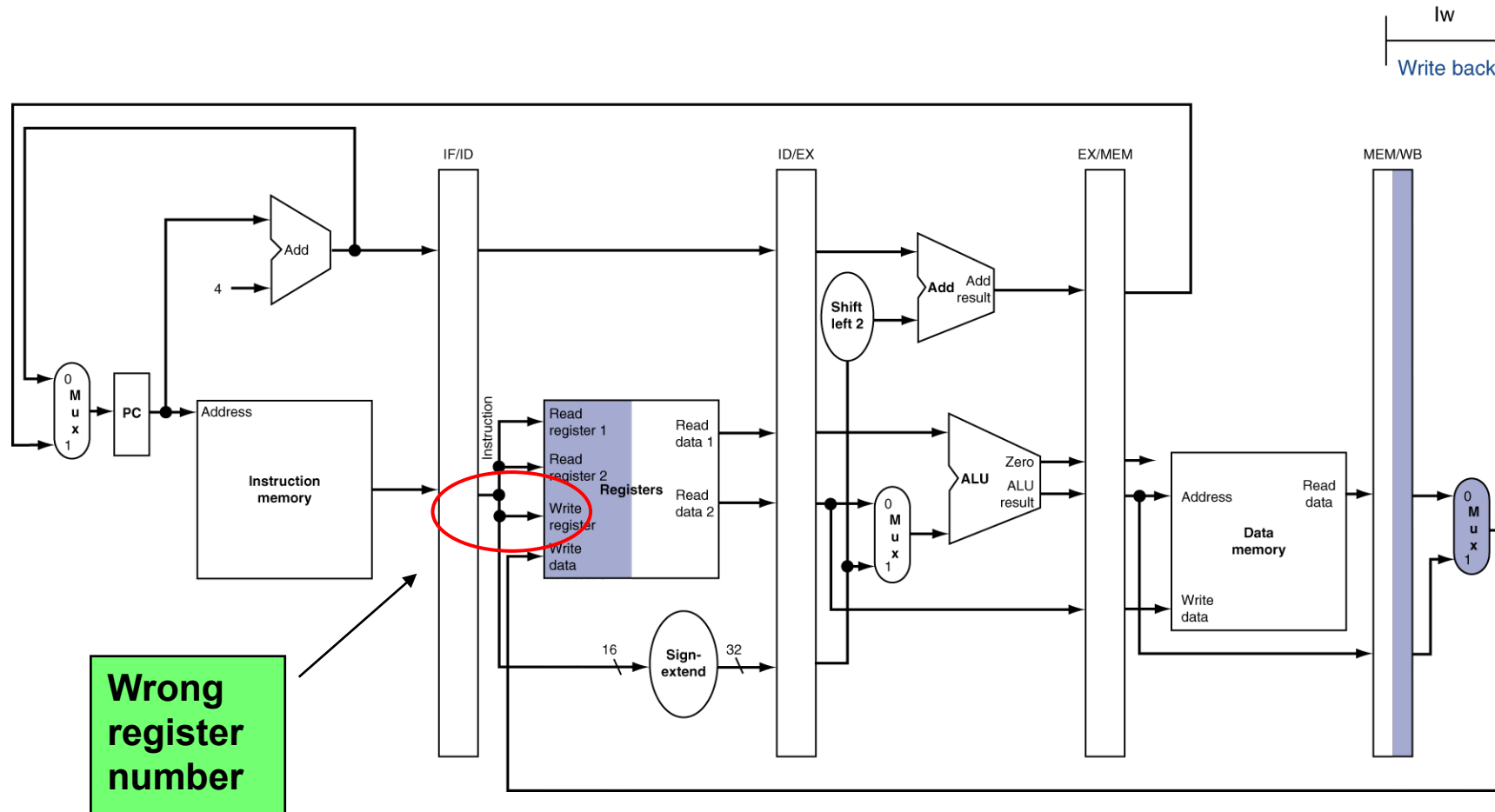


# Corrected Datapath for Load

 


# EX for Store

 

# MEM for Store

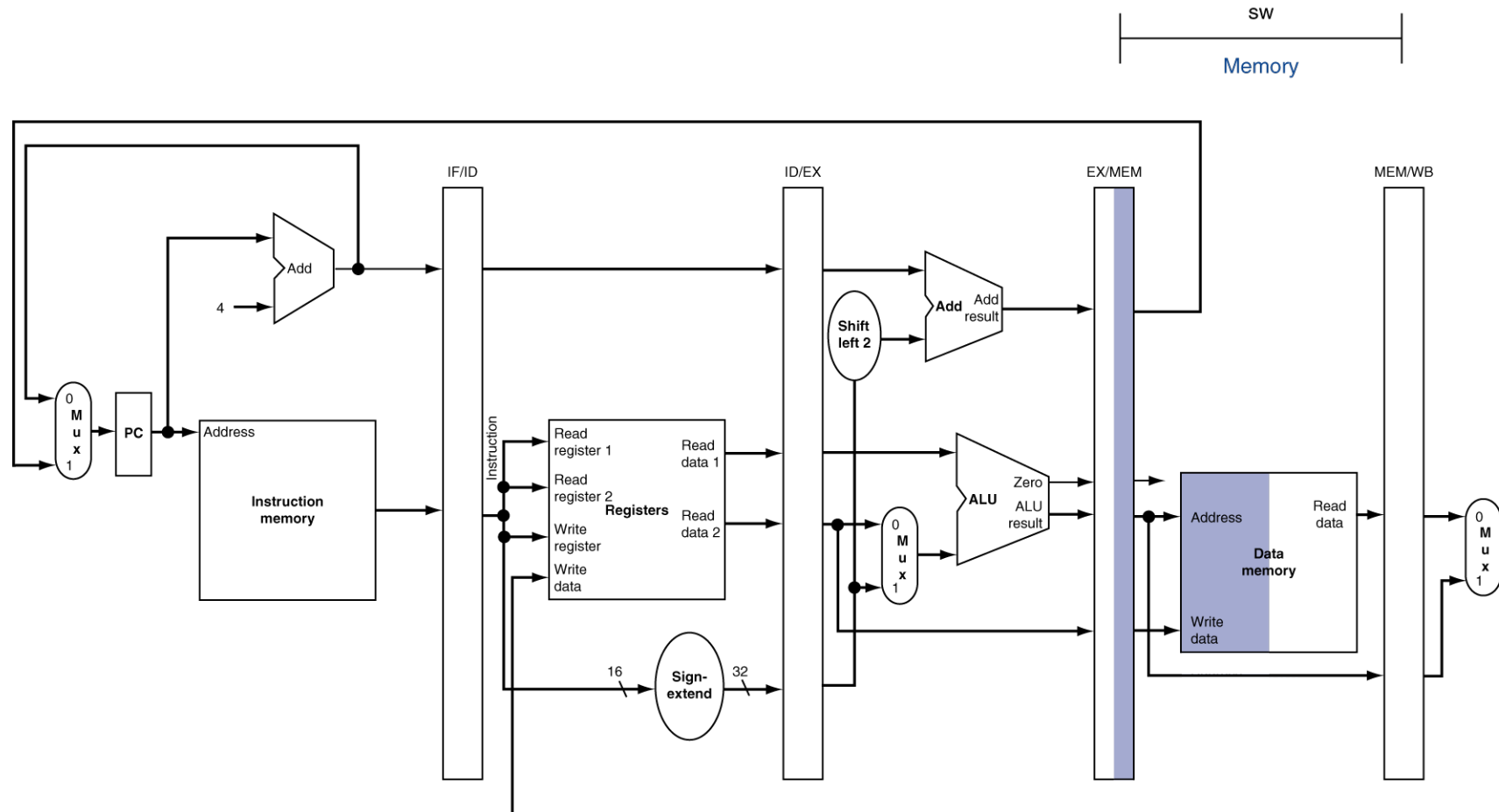

# WB for Store

 


# Example

---

```
lw      $t0, 20($1)
sub     $t1, $2, $3
add     $t2, $3, $4
lw      $t3, 24($1)
add     $t4, $5, $6
```




# Multi-Cycle Pipeline Diagram

 

# Multi-Cycle Pipeline Diagram

## Traditional form

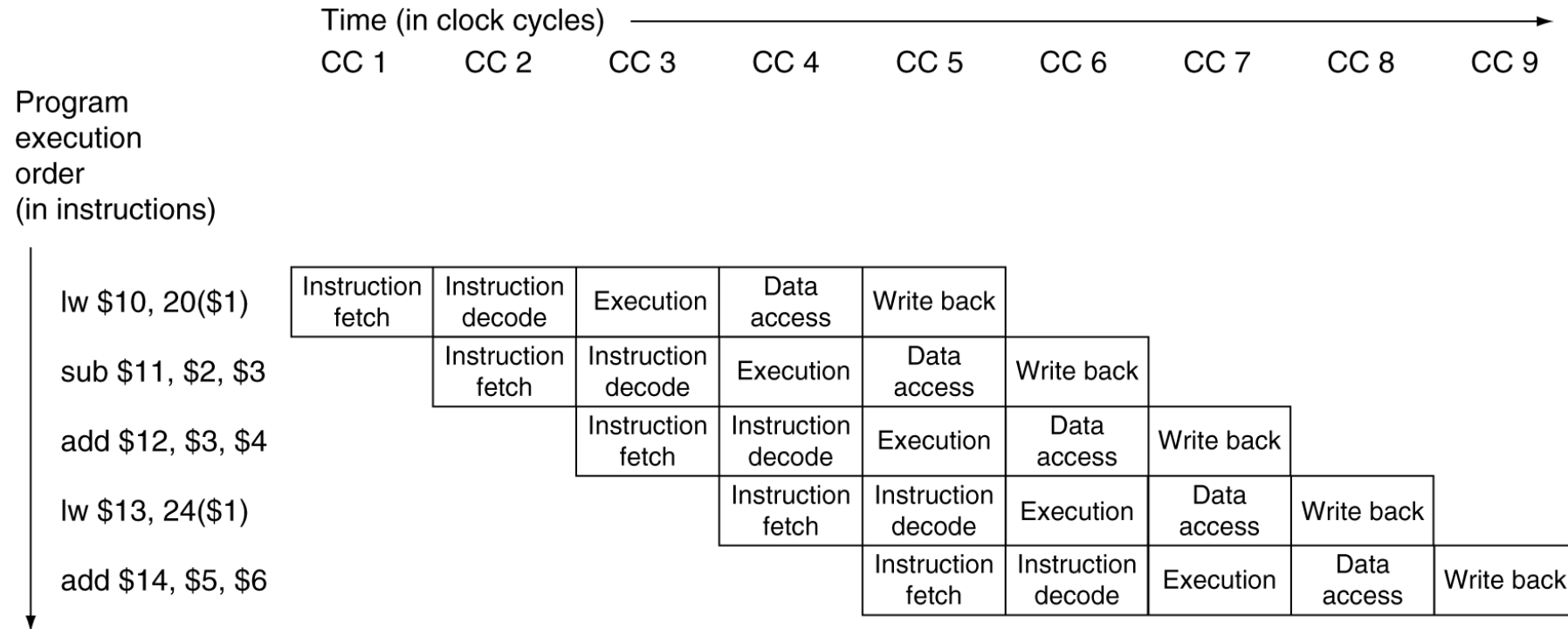


# Single-Cycle Pipeline Diagram


## State of pipeline in a given cycle (Clock cycle 5)

add \$14, \$5, \$6	lw \$13, 24(\$1)	add \$12, \$3, \$4	sub \$11, \$2, \$3	lw \$10, 20(\$1)
Instruction fetch	Instruction decode	Execution	Memory	Write-back

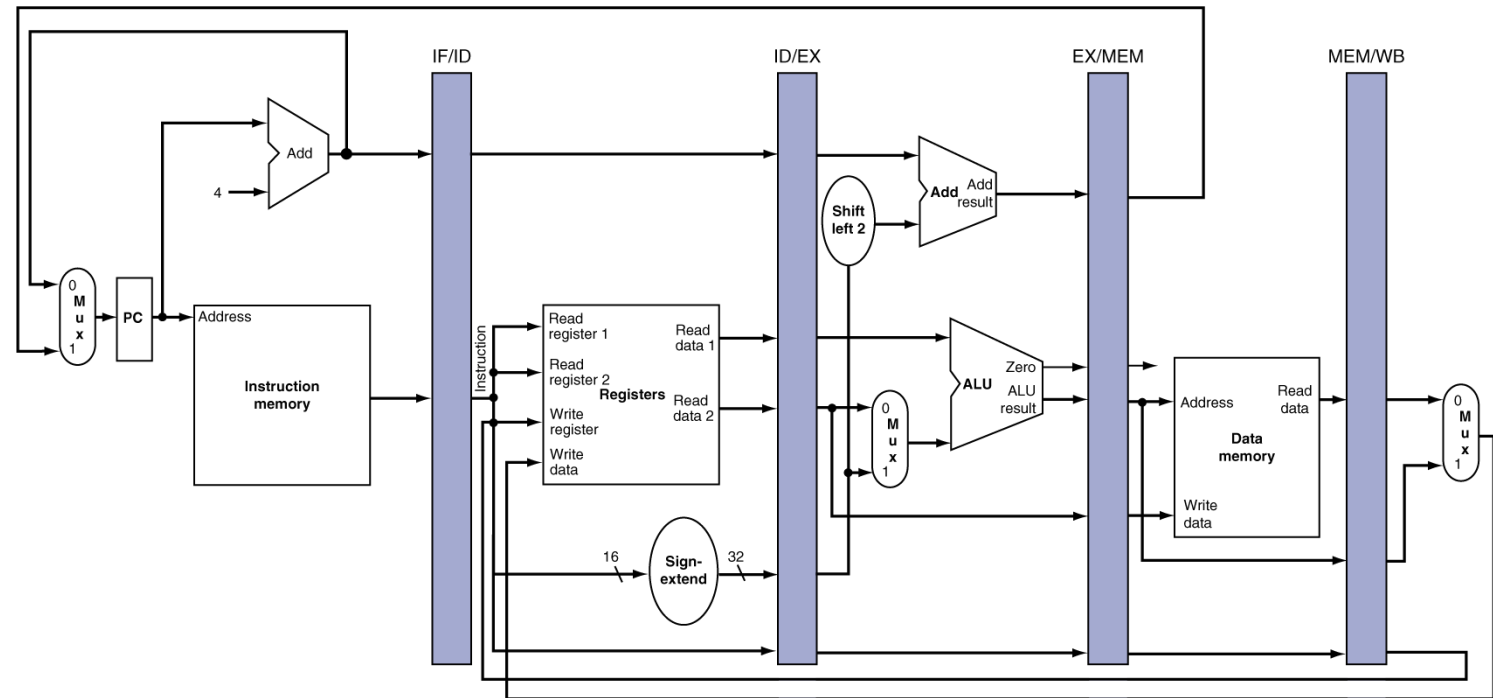lw \$10, 20(\$1)  
sub \$11, \$2, \$3  
add \$12, \$3, \$4  
lw \$13, 24(\$1)  
add \$14, \$5, \$6



# Pipelined Control (Simplified)

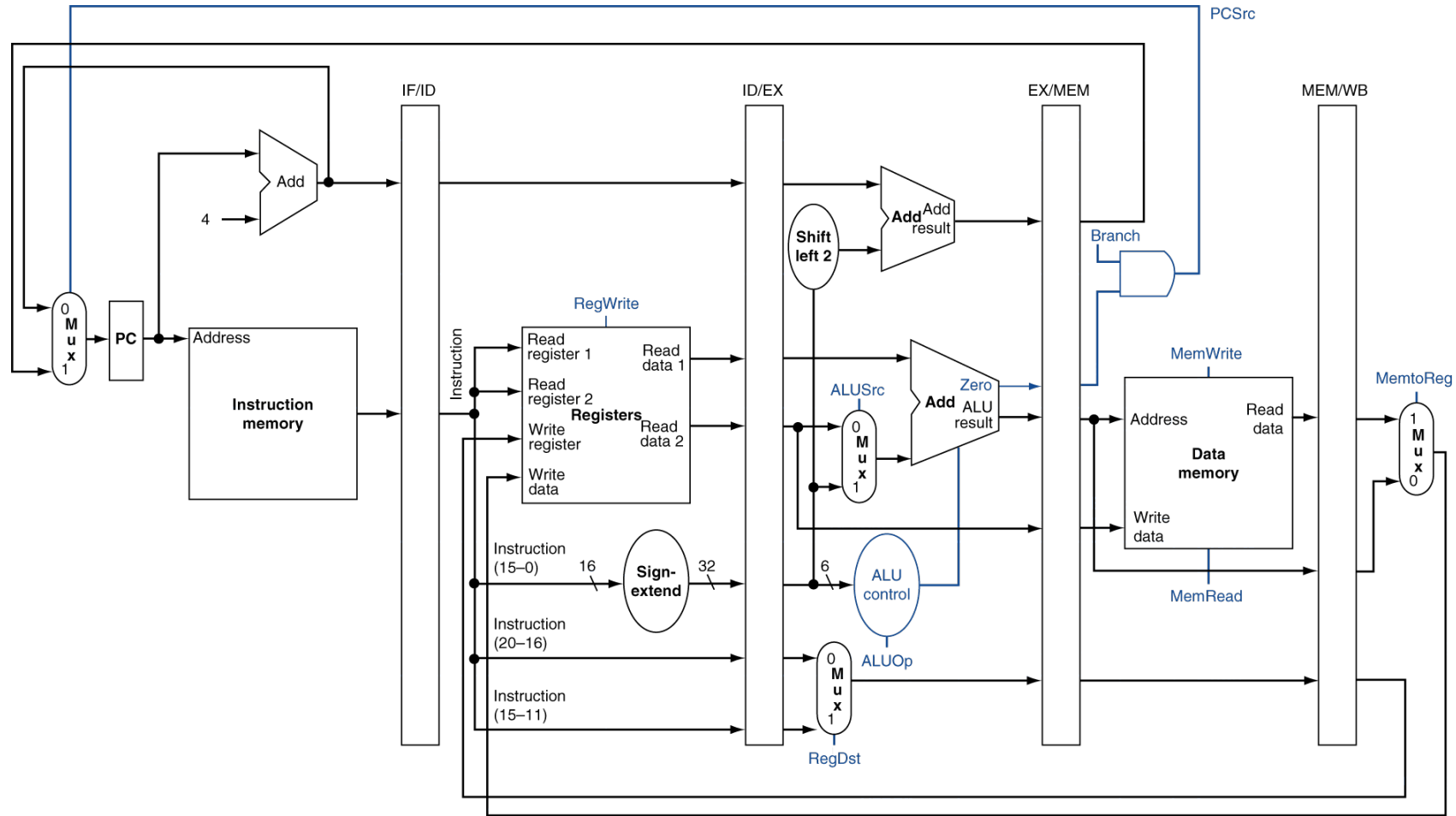


# Control Signals

---


Instruction	Execution/address calculation stage control lines				Memory access stage control lines			Write-back stage control lines	
	RegDst	ALUOp1	ALUOp0	ALUSrc	Branch	Mem- Read	Mem- Write	Reg- Write	Memto- Reg
R-format	1	1	0	0	0	0	0	1	0
lw	0	0	0	1	0	1	0	1	1
sw	X	0	0	1	0	0	1	0	X
beq	X	0	1	0	1	0	0	0	X
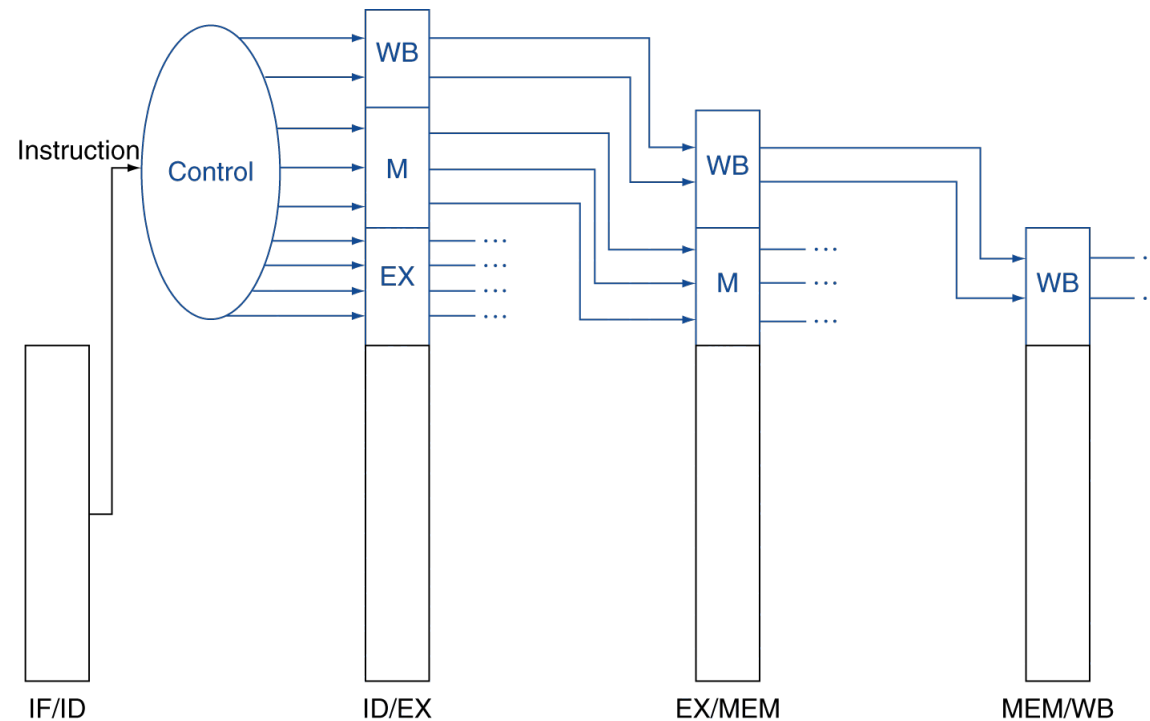
# Pipelined Control

- **Control signals derived from instruction**
  - As in single-cycle implementation



# Pipelined Control

 

# Dealing with Hazards and Changes in Pipeline Datapath & Control



# Data Hazards in ALU Instructions


---

- **Consider this sequence:**

```
sub $2, $1, $3  
and $12, $2, $5  
or  $13, $6, $2  
add $14, $2, $2  
sw  $15, 100($2)
```

- **We can resolve hazards with forwarding**
  - How do we detect when to forward?

# Dependencies & Forwarding

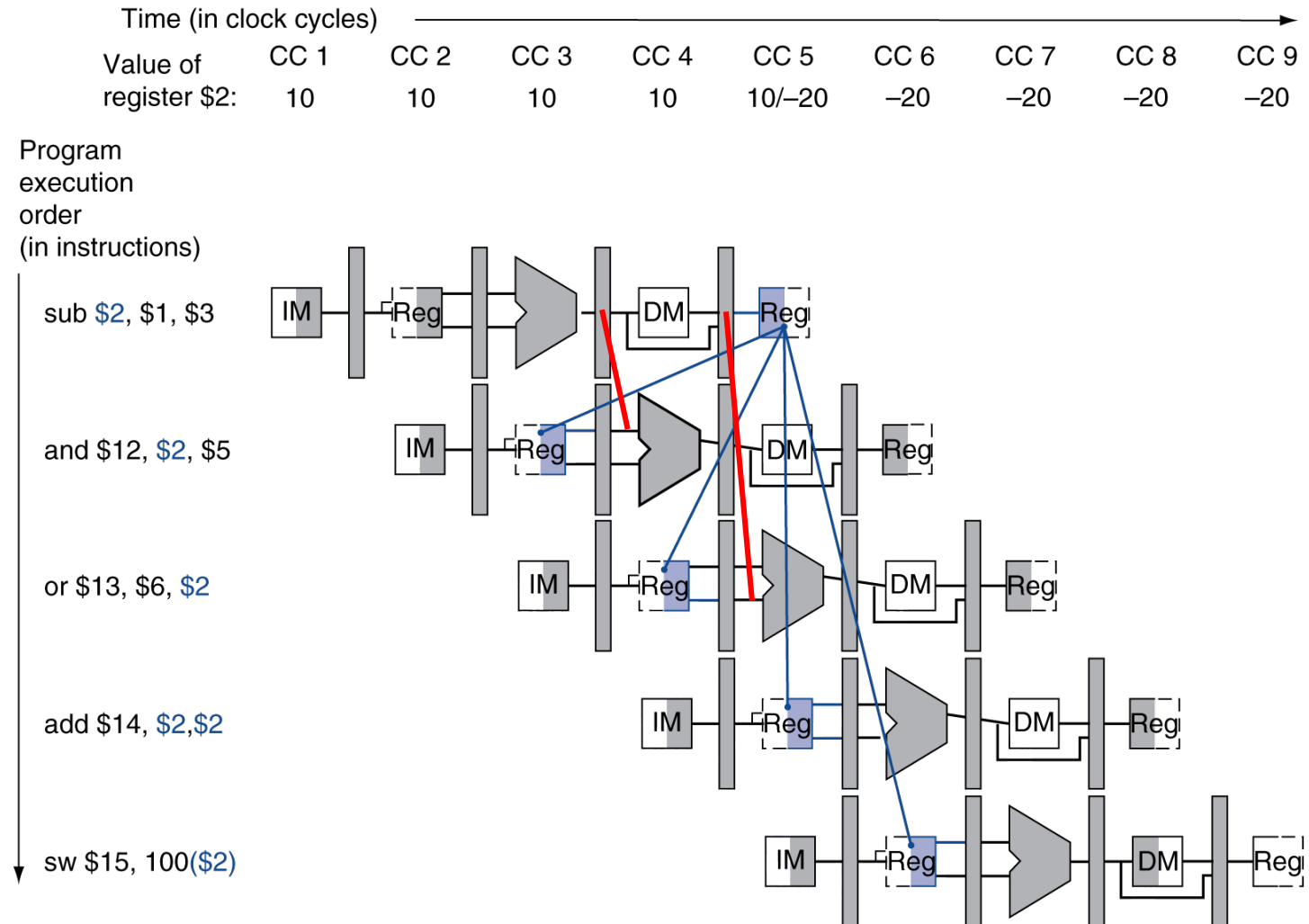

# Detecting the Need to Forward

---

- **Pass register numbers along pipeline**
  - e.g., ID/EX.RegisterRs = register number for Rs sitting in ID/EX pipeline register
- **ALU operand register numbers in EX stage are given by**
  - ID/EX.RegisterRs, ID/EX.RegisterRt
- **Data hazards when**
  - 1a. EX/MEM.RegisterRd = ID/EX.RegisterRs
  - 1b. EX/MEM.RegisterRd = ID/EX.RegisterRt
  - 2a. MEM/WB.RegisterRd = ID/EX.RegisterRs
  - 2b. MEM/WB.RegisterRd = ID/EX.RegisterRt

Fwd from  
EX/MEM  
pipeline reg

Fwd from  
MEM/WB  
pipeline reg


# Data Hazards in ALU Instructions

---

- **Consider this sequence:**

```
sub $2, $1, $3
and $12, $2, $5 # 1a
or  $13, $6, $2 # 2b
add $14, $2, $2 # 2b
sw  $15, 100($2)
```

# Dependencies & Forwarding

 

# Detecting the Need to Forward

---

- **Pass register numbers along pipeline**
  - e.g., ID/EX.RegisterRs = register number for Rs sitting in ID/EX pipeline register
- **ALU operand register numbers in EX stage are given by**
  - ID/EX.RegisterRs, ID/EX.RegisterRt
- **Data hazards when**
  - 1a. EX/MEM.RegisterRd = ID/EX.RegisterRs
  - 1b. EX/MEM.RegisterRd = ID/EX.RegisterRt
  - 2a. MEM/WB.RegisterRd = ID/EX.RegisterRs
  - 2b. MEM/WB.RegisterRd = ID/EX.RegisterRt

Fwd from  
EX/MEM  
pipeline reg


Fwd from  
MEM/WB  
pipeline reg

# Detecting the Need to Forward

---

- **But only if forwarding instruction will write to a register!**
  - EX/MEM.RegWrite, MEM/WB.RegWrite
- **And only if Rd for that instruction is not \$zero**
  - EX/MEM.RegisterRd  $\neq$  0,  
MEM/WB.RegisterRd  $\neq$  0

# Forwarding Paths

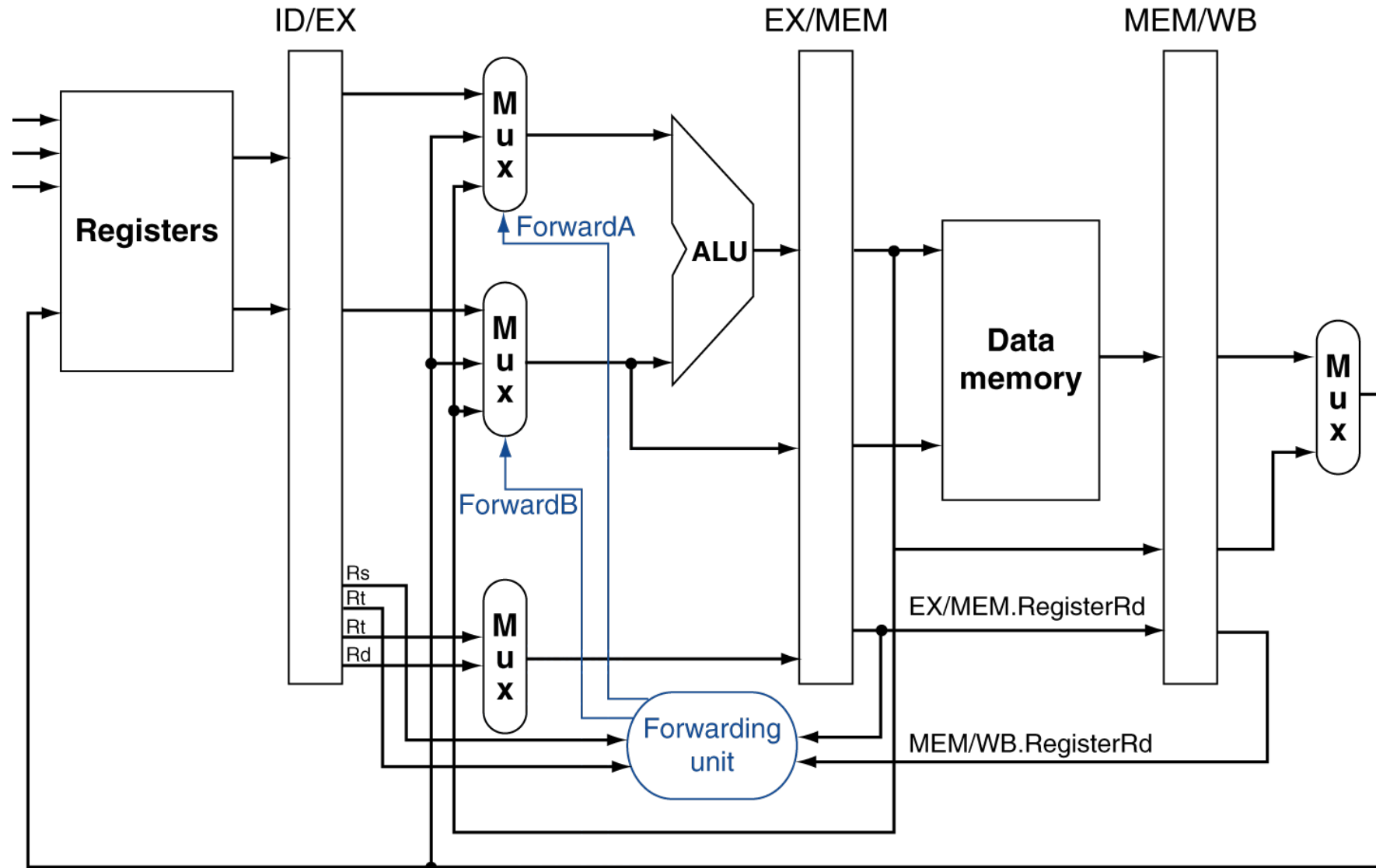



# Forwarding Conditions

---

Mux control	Source	Explanation
ForwardA = 00	ID/EX	The first ALU operand comes from the register file.
ForwardA = 10	EX/MEM	The first ALU operand is forwarded from the prior ALU result.
ForwardA = 01	MEM/WB	The first ALU operand is forwarded from data memory or an earlier ALU result.
ForwardB = 00	ID/EX	The second ALU operand comes from the register file.
ForwardB = 10	EX/MEM	The second ALU operand is forwarded from the prior ALU result.
ForwardB = 01	MEM/WB	The second ALU operand is forwarded from data memory or an earlier ALU result.

# Forwarding Conditions

---

## ▪ EX hazard

- if (EX/MEM.RegWrite and (EX/MEM.RegisterRd  $\neq$  0)  
and (EX/MEM.RegisterRd = ID/EX.RegisterRs))

ForwardA = 10

- if (EX/MEM.RegWrite and (EX/MEM.RegisterRd  $\neq$  0)  
and (EX/MEM.RegisterRd = ID/EX.RegisterRt))

ForwardB = 10

## ▪ MEM hazard

- if (MEM/WB.RegWrite and (MEM/WB.RegisterRd  $\neq$  0)  
and (MEM/WB.RegisterRd = ID/EX.RegisterRs))

ForwardA = 01

- if (MEM/WB.RegWrite and (MEM/WB.RegisterRd  $\neq$  0)  
and (MEM/WB.RegisterRd = ID/EX.RegisterRt))

ForwardB = 01

# Double Data Hazard

---

- **Consider the sequence:**

- add \$1, \$1, \$2

- add \$1, \$1, \$3

- add \$1, \$1, \$4

- **Both hazards occur**

- Want to use the most recent

- **Revise MEM hazard condition**

- Only fwd if EX hazard condition isn't true

# Revised Forwarding Condition

---

- **MEM hazard**


- if (MEM/WB.RegWrite and (MEM/WB.RegisterRd  $\neq$  0)  
    and not (EX/MEM.RegWrite and (EX/MEM.RegisterRd  $\neq$  0)  
        and (EX/MEM.RegisterRd = ID/EX.RegisterRs))  
    and (MEM/WB.RegisterRd = ID/EX.RegisterRs))

ForwardA = 01


- if (MEM/WB.RegWrite and (MEM/WB.RegisterRd  $\neq$  0)  
    and not (EX/MEM.RegWrite and (EX/MEM.RegisterRd  $\neq$  0)  
        and (EX/MEM.RegisterRd = ID/EX.RegisterRt))  
    and (MEM/WB.RegisterRd = ID/EX.RegisterRt))

ForwardB = 01


# Datapath with Forwarding

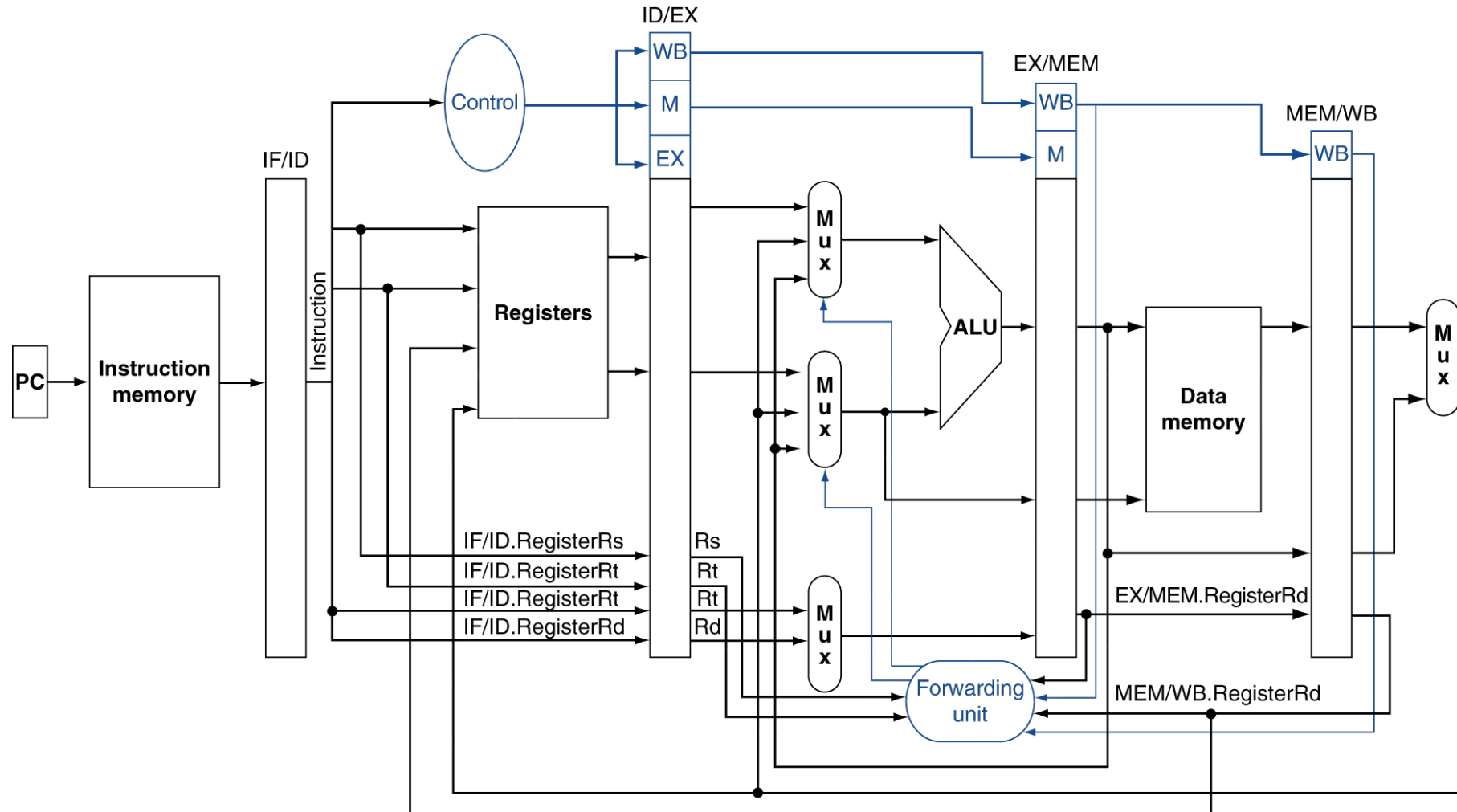


# Dependencies & Forwarding

 

# Forwarding Implemented

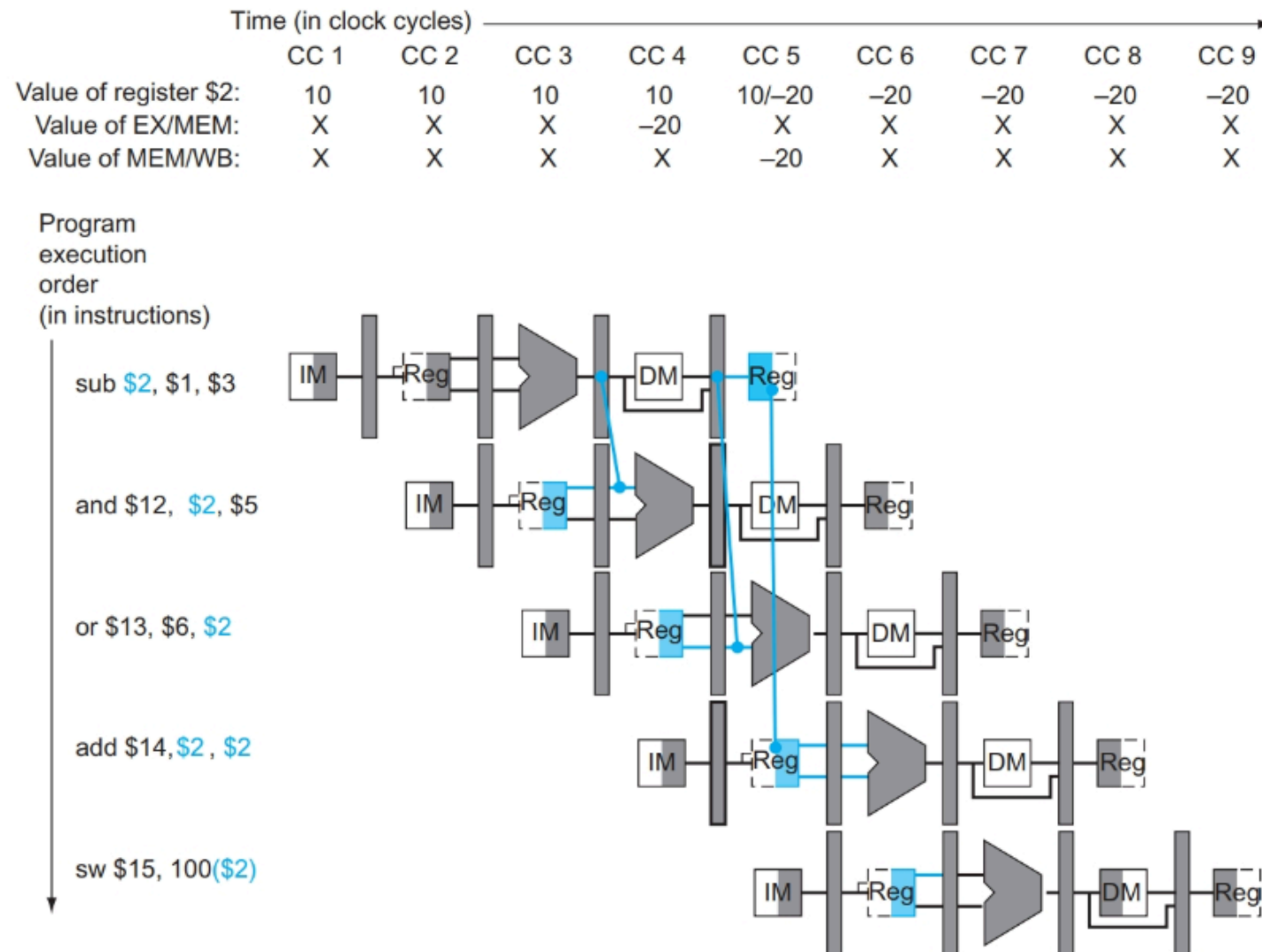

# Load-Use Data Hazard

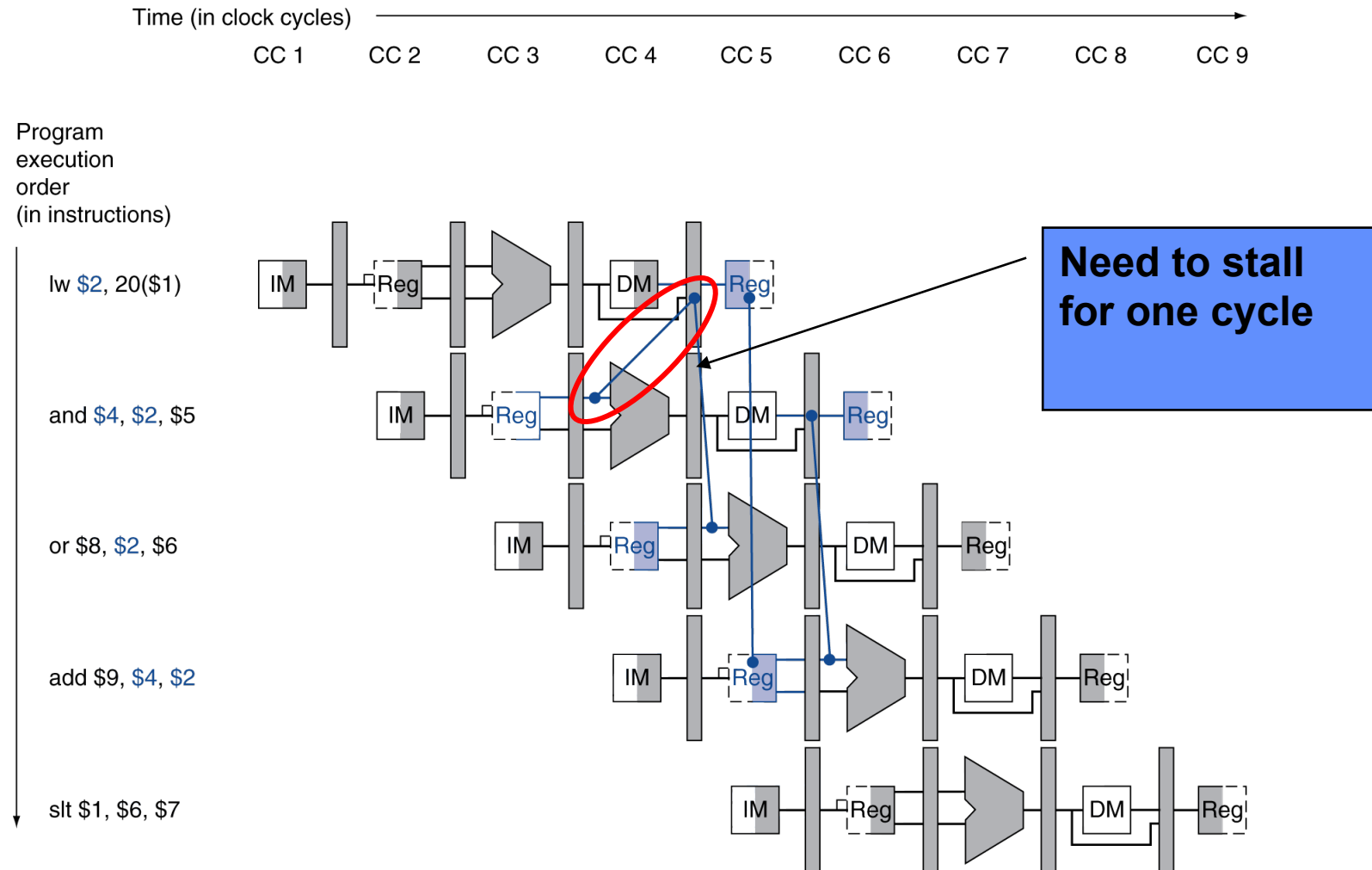



# Load-Use Hazard Detection

---


- **Check when using instruction is decoded in ID stage**
- **ALU operand register numbers in ID stage are given by**
  - IF/ID.RegisterRs, IF/ID.RegisterRt
- **Load-use hazard when**
  - ID/EX.MemRead and  
((ID/EX.RegisterRt = IF/ID.RegisterRs) or  
(ID/EX.RegisterRt = IF/ID.RegisterRt))
- **If detected, stall and insert bubble**

# How to Stall the Pipeline


---

- **Force control values in ID/EX register to 0**
  - EX, MEM and WB do nop (no-operation)
- **Prevent update of PC and IF/ID register**
  - Using instruction is decoded again
  - Following instruction is fetched again
  - 1-cycle stall allows MEM to read data for 1w
    - » Can subsequently forward to EX stage

# Stall/Bubble in the Pipeline

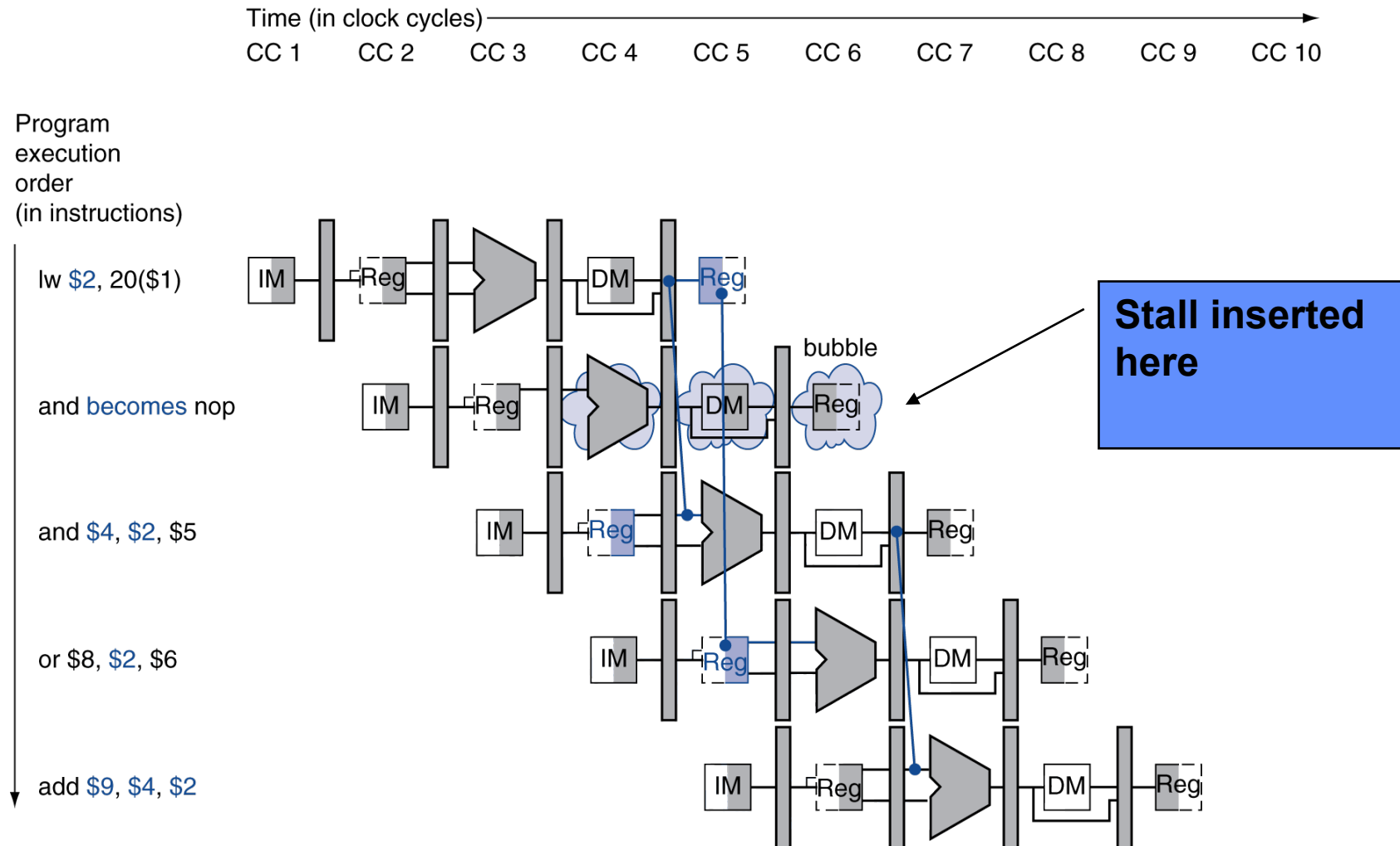

# Stall/Bubble in the Pipeline

 

# Datapath with Hazard Detection

