

# **CPT\_S 260 Intro to Computer Architecture**

## **Lecture 25**

**Digital Design IV**  
**March 9, 2022**

**Ganapati Bhat**  
**School of Electrical Engineering and Computer Science**  
**Washington State University**

# Recap: Rules of Boolean Algebra

---

- **Associative Law of multiplication**

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

- **Distributive Law of multiplication**

$$A + BC = (A + B) \cdot (A + C)$$

- **Annulment law:**

$$A \cdot 0 = 0$$

$$A + 1 = 1$$

- **Identity law:**

$$A \cdot 1 = A$$

$$A + 0 = A$$

# Recap: Rules of Boolean Algebra

---

- **Complement law:**

$$\begin{aligned}A + \bar{A} &= 1 \\A \cdot \bar{A} &= 0\end{aligned}$$

- **Double negation law:**

$$\bar{\bar{A}} = A$$

- **Absorption law:**

$$\begin{aligned}A \cdot (A + B) &= A \\A + AB &= A \\A + \bar{A}B &= A + B\end{aligned}$$



- **Idempotent law:**

$$\begin{aligned}A + A &= A \\A \cdot A &= A\end{aligned}$$
  
# Recap: De Morgan's Laws

- Transformation rules that help simplification of negations
- Statement:

$$\overline{AB} = \bar{A} + \bar{B}$$
$$\overline{(A + B)} = \bar{A} \cdot \bar{B}$$



# Sum of Products

---

- **Minterm Expressions**
- If input is 0 we take the complement of the variable
- If input is 1 we take the variable as is
- To get the desired canonical SOP expression we will add the minterms (product terms) for which the output is 1

$$F = \bar{A}B + A\bar{B} + AB$$

A	B	F	Minterm
0	0	0	A'B'
0	1	1	A'B
1	0	1	AB'
1	1	1	AB

# Product of Sums

---

- **Maxterm Expressions**
- If input is 1, we take the complement of the variable
- If input is 0, we take the variable as is
- To get the desired canonical POS expression we will multiply the maxterms (sum terms) for which the output is 0

$$F = (A + B)$$

A	B	F	Maxterm
0	0	0	$A + B$
0	1	1	$A + \bar{B}$
1	0	1	$\bar{A} + B$
1	1	1	$\bar{A} + \bar{B}$

---

# **Designing a Simple ALU**

## **(Arithmetic Logic Unit)**

# Adder Algorithm

---

	1	0	0	1
	0	1	0	1
Sum (S)	1	1	1	0
Carry (C)	0	0	0	1

Truth Table for the above operations:

A	B	Cin	Sum	Cout
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		



# Adder Algorithm

	1	0	0	1
	0	1	0	1
Sum	1	1	1	0
Carry	0	0	0	1

Truth Table for the above operations:


A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Equations:

$$\begin{aligned} \text{Sum} = & \text{Cin} \cdot \bar{A} \cdot \bar{B} + \\ & B \cdot \bar{\text{Cin}} \cdot \bar{A} + \\ & A \cdot \bar{\text{Cin}} \cdot \bar{B} + \\ & A \cdot B \cdot \text{Cin} \end{aligned}$$

$$\begin{aligned} \text{Cout} = & A \cdot B \cdot \text{Cin} + \\ & A \cdot B \cdot \bar{\text{Cin}} + \\ & A \cdot \text{Cin} \cdot \bar{B} + \\ & B \cdot \text{Cin} \cdot \bar{A} \\ = & A \cdot B + \\ & A \cdot \text{Cin} + \\ & B \cdot \text{Cin} \end{aligned}$$

# Carry Out Logic

 


Equations:

$$\begin{aligned} \text{Sum} = & \text{Cin} \cdot \bar{A} \cdot \bar{B} + \\ & B \cdot \bar{\text{Cin}} \cdot \bar{A} + \\ & A \cdot \bar{\text{Cin}} \cdot \bar{B} + \\ & A \cdot B \cdot \text{Cin} \end{aligned}$$

$$\begin{aligned} \text{Cout} = & A \cdot B \cdot \text{Cin} + \\ & A \cdot B \cdot \bar{\text{Cin}} + \\ & A \cdot \text{Cin} \cdot \bar{B} + \\ & B \cdot \text{Cin} \cdot \bar{A} \\ = & A \cdot B + \\ & A \cdot \text{Cin} + \\ & B \cdot \text{Cin} \end{aligned}$$

# Carry Out Logic

 

$$\begin{aligned}C_{out} &= A \cdot B \cdot Cin + A \cdot B \cdot \overline{Cin} + A \cdot Cin \cdot \bar{B} + B \cdot Cin \cdot \bar{A} \\&= A \cdot B \cdot (Cin + \overline{Cin}) + A \cdot Cin \cdot \bar{B} + A \cdot B \cdot Cin + B \cdot Cin \cdot \bar{A} + A \cdot B \cdot Cin \\&= A \cdot B + A \cdot Cin \cdot (B + \bar{B}) + B \cdot Cin \cdot (A + \bar{A})\end{aligned}$$

# Full-Adder (3 inputs, 2 outputs)

---

- Full-Adder Truth Table:

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


- Same as the previous example:

$$S = X \bar{Y} \bar{Z} + \bar{X} Y \bar{Z} + \bar{X} \bar{Y} Z + X Y Z$$
$$C = X Y + X Z + Y Z$$
 
# 4-bit Ripple-Carry Binary Adder


---

- A four-bit Ripple Carry Adder made from four 1-bit Full Adders:


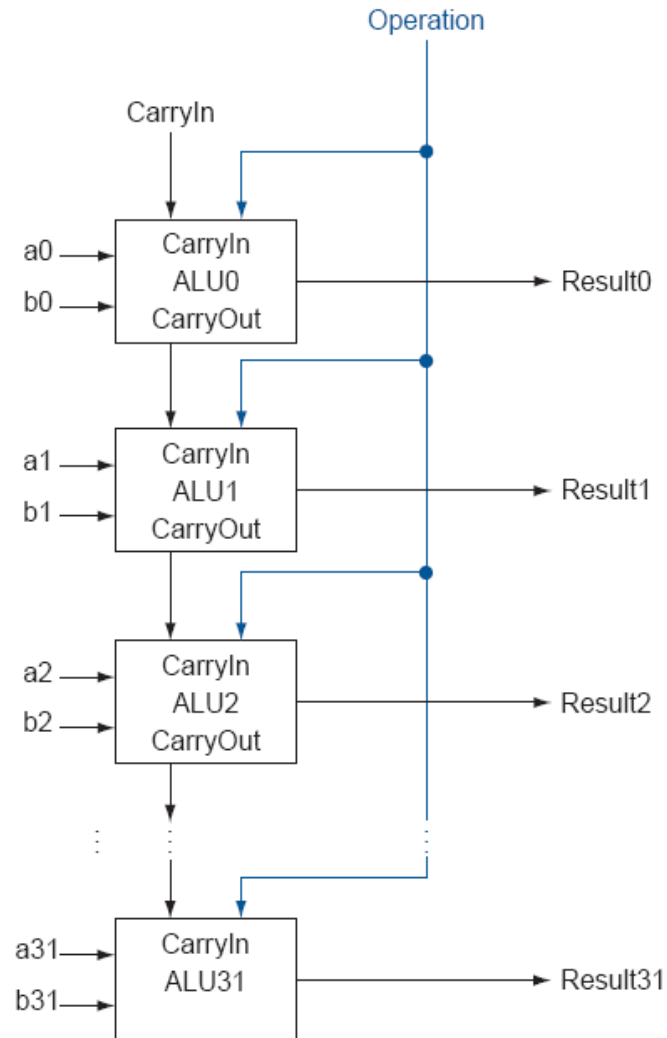
# 32-bit Ripple Carry Adder


**1-bit ALUs are connected  
“in series” with the  
carry-out of 1 box  
going into the carry-in  
of the next box**



# Designing a Simple ALU (Arithmetic Logic Unit)
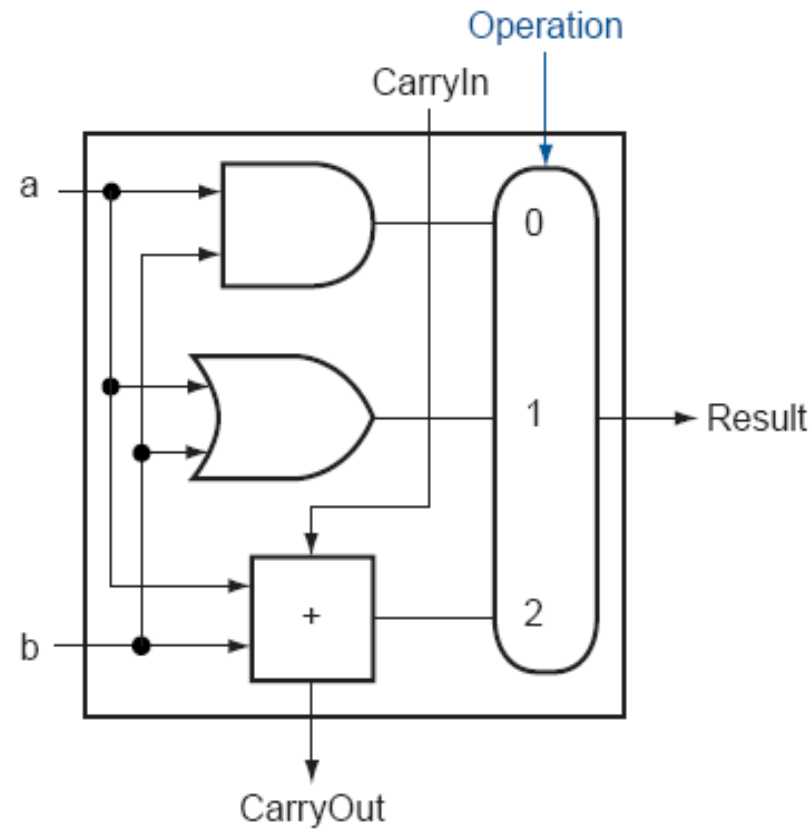
# 1-Bit ALU with Add, Or, And


- Multiplexor selects between Add, Or, And operations





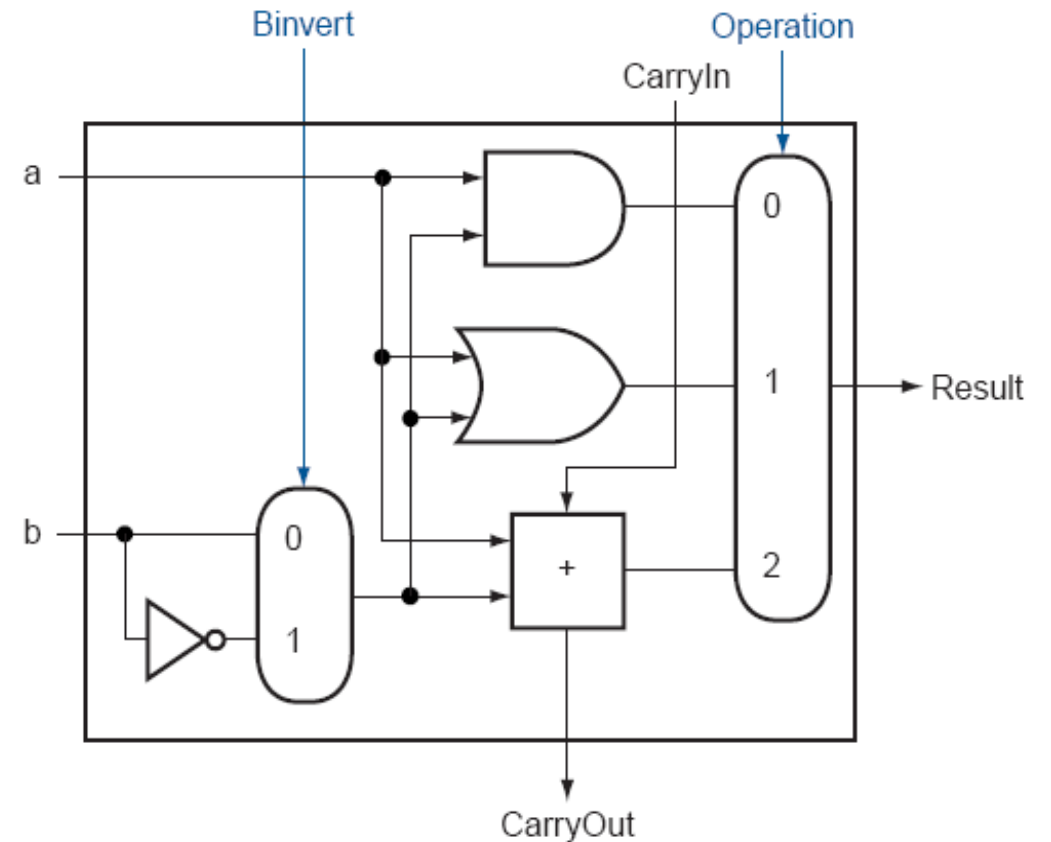
# Incorporating Subtraction

- **Must invert bits of B and add a 1**
  - Include an inverter
- **CarryIn for the first bit is 1**
- **The CarryIn signal (for the first bit) can be the same as the Binvert signal**




# Incorporating NOR

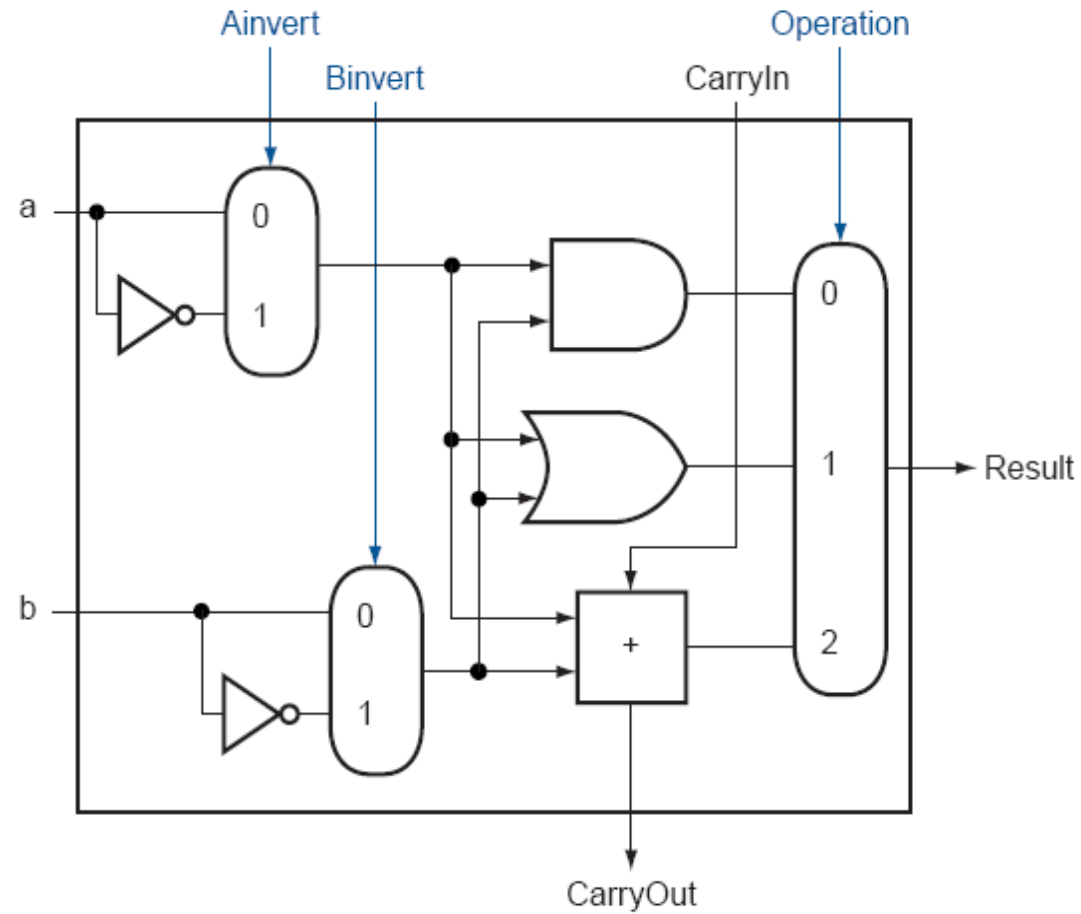


# Comparator: Equality

## Symbol

 


## Implementation

 

- Perform  $a - b$  and confirm that the result is all zero's
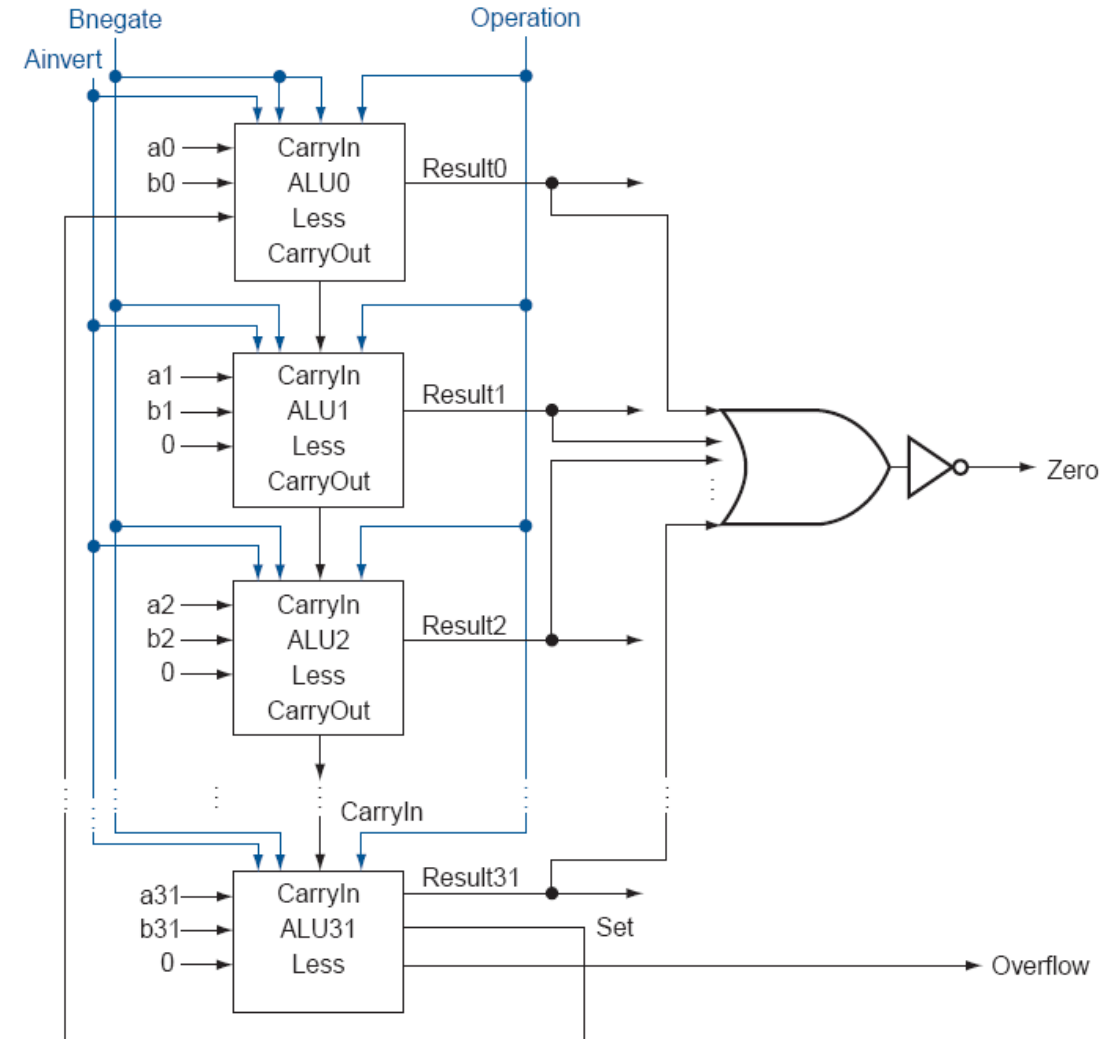
# Incorporating beq

- **Perform  $a - b$  and**
  - Confirm that the
  - Result is all zero's



# Incorporating slt

- Perform  $a - b$  and check the sign
- New signal (Less) that is zero for ALU boxes 1-31
- The 31st box has a unit to detect overflow and sign – the sign bit serves as the Less signal for the 0th box

