

CPT_S 260 Intro to Computer Architecture

Lecture 26

Digital Design: Sequential Logic
March 21, 2022


Ganapati Bhat
School of Electrical Engineering and Computer Science
Washington State University

Announcements

- **Mid term exam 2**


- Friday, April 1, 2022
- Format will be similar to exam 1
- Tentative topics: MIPS, digital logic, single cycle MIPS implementation


Recap: Incorporating NOR

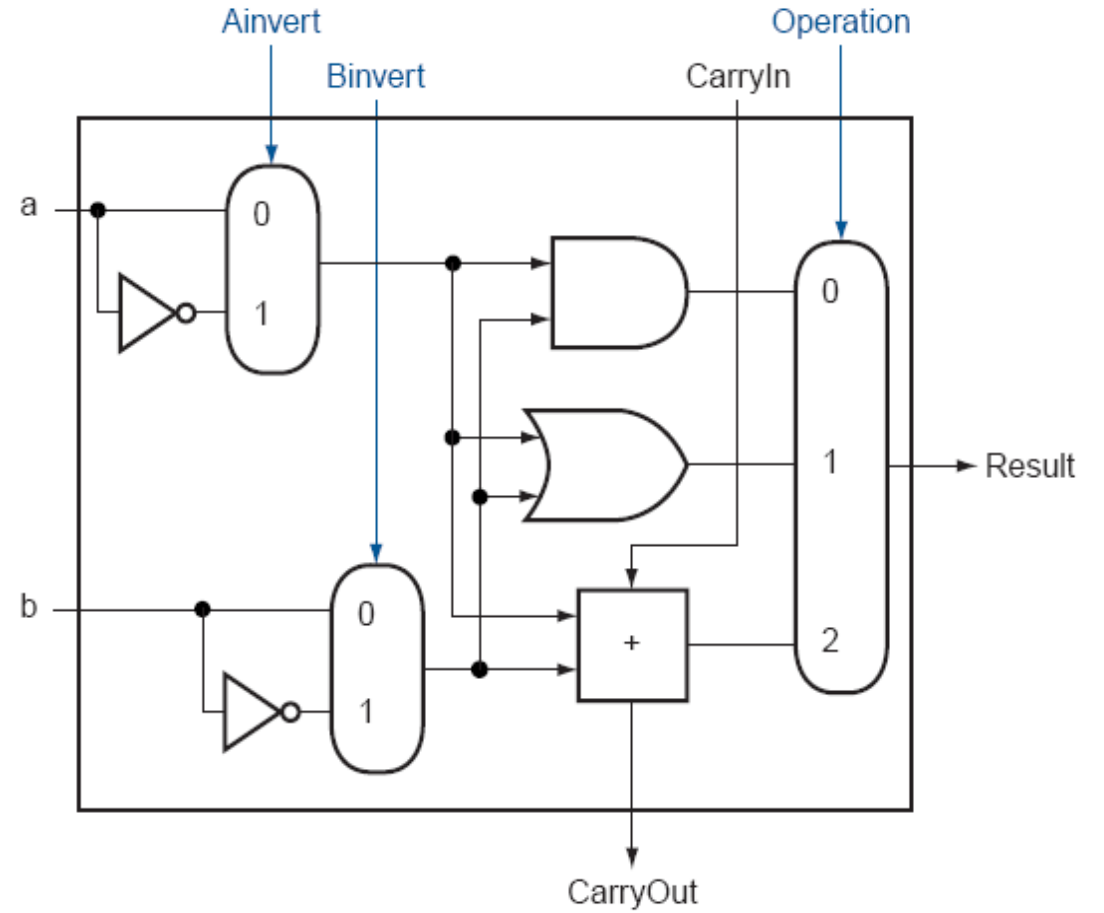

Recap: Incorporating slt

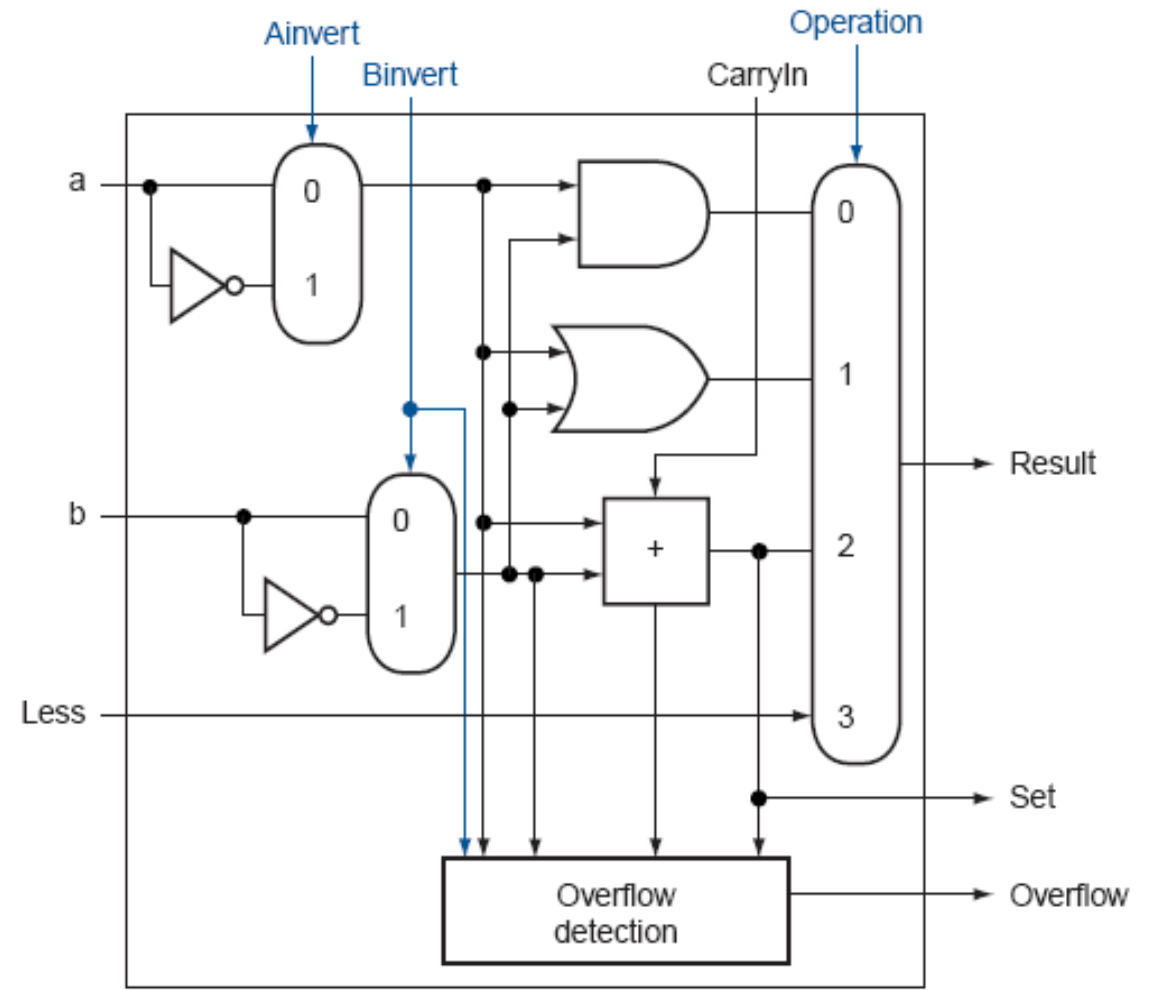- Perform $a - b$ and check the sign
- New signal (Less) that is zero for ALU boxes 1-31
- The 31st box has a unit to detect overflow and sign – the sign bit serves as the Less signal for the 0th box




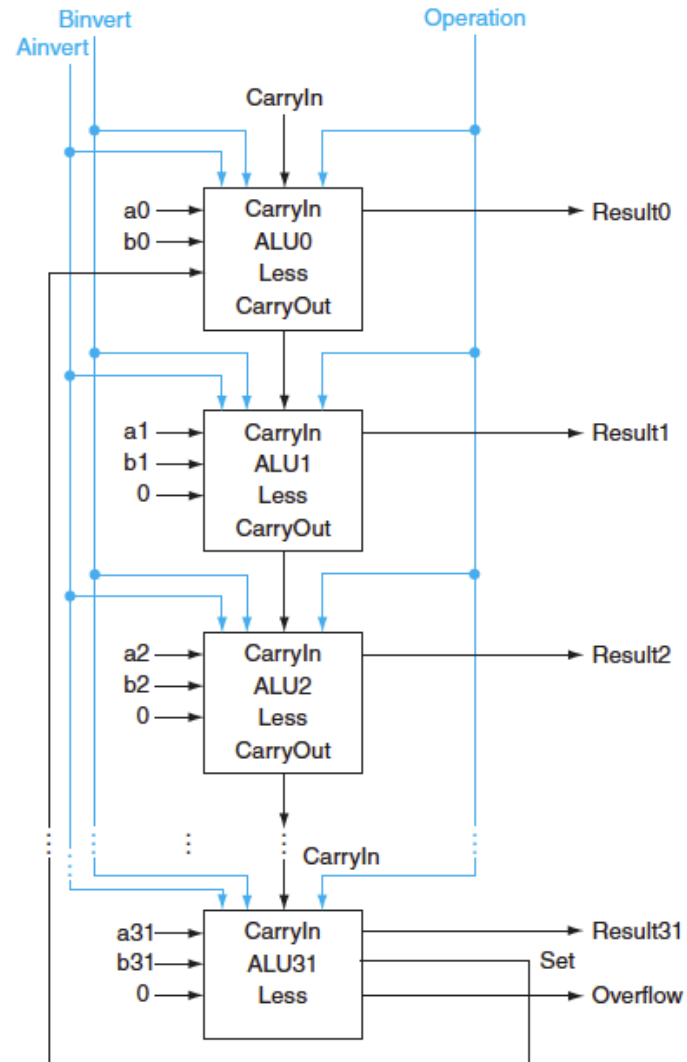

Recap: Incorporating beq

- Perform $a - b$ and
 - Confirm that the
 - Result is all zero's

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set on less than
1100	NOR

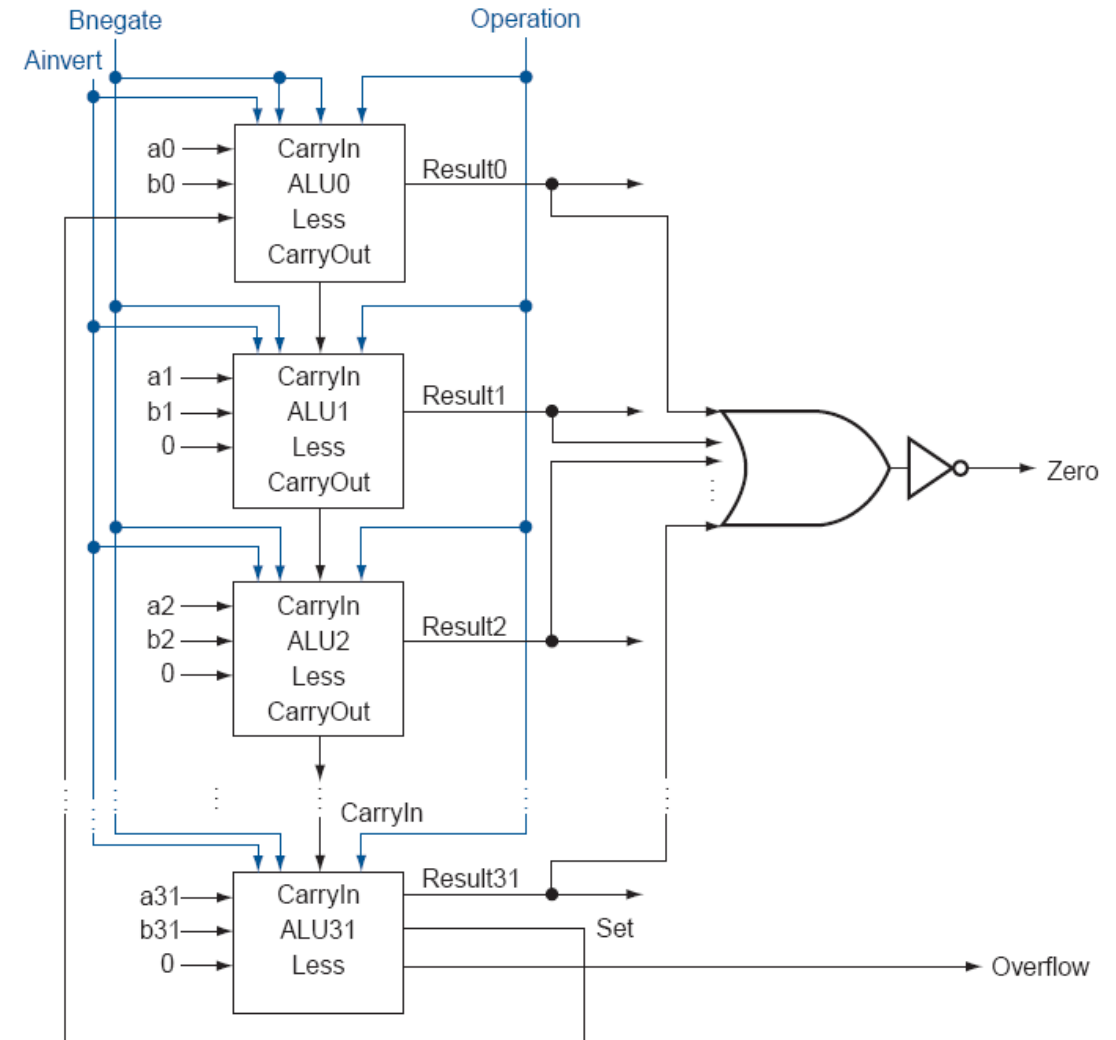


Sequential Logic

Registers

- Register – a collection of binary storage elements
- In theory, a register is sequential logic which can be defined by a state table
- More often think of a register as storing a vector of binary values
- Frequently used to perform simple data storage and data movement and processing operations

Clock

Load

 

Example: 4-bit Register


SI -> Shift In

SO -> Shift Out

Clear -> Clears the bits in register



Load -> Reads the inputs into register

Clock -> Provides timing for read/writes



 


Sequential Elements

  - **Flip flops: stores data in a circuit**
 - Uses a clock signal to determine when to update the stored value
 - Edge-triggered: update when Clk changes from 0 to 1





Clocking Sequence

   

Sequential Elements

▪ Flip flop with write control

 
 
- Only updates on clock edge when write control input is '1'
- Used when stored value is required later



12

Clocking Methodology

  - **Combinational logic transforms data during clock cycles**
 - Between clock edges
 - Input from state elements, output to state element
 - Longest delay determines clock period




Example

 5. **Sequential Logic (10 points).** The following figure shows a sequential circuit with two D Flip Flops with a common input clock. Assume that the flip flops are initialized at '0'. That is, $Q_1 = Q_2 = 0$ during Cycle 0. This means the output of this circuit is initially $Q_2Q_1 = '00'$.

- (5 points) Compute the value of each output signal (Q_2 and Q_1) for 8 cycles using the table below.
- (5 points) Convert the 3-bit binary Q_2Q_1 to its equivalent decimal in the table. How many unique output states (i.e., Q_2Q_1) does this circuit produce?

$$\begin{cases} D_1 = Q_1 \oplus Q_2 \\ D_2 = \overline{Q_2} \end{cases}$$



$$Q_1 \times (2)^0 + Q_2 \times (2)^1$$

Clock Cycle	Q_2	Q_1	Decimal ($Q = Q_2Q_1$)
0	0	0	0
1	1	0	2
2	0	1	1
3	1	1	3
4	0	0	0
5	1	0	2
6	0	1	1
7	1	1	3
8	0	0	0

Example

3. Consider the following Boolean expression:

$$F = (\bar{A} + AB) [(A + A)B + A\bar{B}]$$

Assume that you are allowed to use only these three gate types: NOT, 2-input AND, 2-input OR to design the digital circuit for 'F' although you are not required to use all the three types. Furthermore, assume that the latency of each gate is 500 ps (i.e., 500 picoseconds).


- Simplify function 'F' as much as possible. What is the final simplified expression of 'F'?
- Draw equivalent digital circuit for the simplified function.
- What is the overall latency of the simplified circuit?

a.
$$F = (\bar{A} + AB) [(A + A)B + A\bar{B}]$$

rule $A + A = A$ rule $B + \bar{B} = 1$

$$F = (\bar{A} + AB) (A \cancel{A} B + A \bar{B}) = (\bar{A} + AB) (A (B + \bar{B}))$$
$$F = (\bar{A} + AB) (A) = A \bar{A} + A A B = AB$$

rule $A \bar{A} = 0$ rule $AA = A$

 


c.
$$\text{latency} = 1 \times 500 \text{ ps} = 500 \text{ ps}$$

one gate

Example

 5. **Basics of Digital Design (10 points).** The following figure shows a sequential circuit with three D Flip Flops with a common input clock. Note that the inverted output of the last flip-flop (\bar{Q}_0) is connected to the input of the first flip-flop (D input of the far left flip flop). Assume that the flip flops are initialized at '0'. That is, $Q_2 = Q_1 = Q_0 = 0$ during Cycle 0. This means the output of this circuit is initially $Q_2Q_1Q_0 = '000'$.

- (5 points) Compute the value of each output signal (Q_2 , Q_1 , and Q_0) for 10 cycles using the table below.
- (5 points) Convert the 3-bit binary $Q_2Q_1Q_0$ to its equivalent decimal in the table. How many unique output states (i.e., $Q_2Q_1Q_0$) does this circuit produce?



Clock Cycle	Q_2	Q_1	Q_0	Decimal ($Q = Q_2Q_1Q_0$)
0	0	0	0	0
1	1	0	0	4
2	1	1	0	6
3	1	1	1	7
4	0	1	1	3
5	0	0	1	1
6	0	0	0	0
7	1	0	0	4
8	1	1	0	6
9	1	1	1	7
10	0	1	1	3


There are 6 distinct states: 0, 4, 6, 7, 3, 1

Memory Definitions

- **Memory** — A collection of storage cells together with the necessary circuits to transfer information to and from them.
- **Memory Organization** — the basic architectural structure of a memory in terms of how data is accessed.
- **Random Access Memory (RAM)** — a memory organized such that data can be transferred to or from any cell (or collection of cells) in a time that is not dependent upon the particular cell selected.
- **Memory Address** — A vector of bits that identifies a particular memory element (or collection of elements).

Memory Block Diagram

 - A basic memory system is shown here:
- k address lines are decoded to address 2^k words of memory.
- Each word is n bits.
- Read and Write are single control lines defining the simplest of memory operations.



Memory Organization Example

- **Example memory contents:**

- A memory with 3 address bits & 8 data bits has:
- $k = 3$ and $n = 8$ so $2^3 = 8$ addresses labeled 0 to 7.
- $2^3 = 8$ words of 8-bit data

Memory Address		Memory Content
Binary	Decimal	
0 0 0	0	1 0 0 0 1 1 1 1
0 0 1	1	1 1 1 1 1 1 1 1
0 1 0	2	1 0 1 1 0 0 0 1
0 1 1	3	0 0 0 0 0 0 0 0
1 0 0	4	1 0 1 1 1 0 0 1
1 0 1	5	1 0 0 0 0 1 1 0
1 1 0	6	0 0 1 1 0 0 1 1
1 1 1	7	1 1 0 0 1 1 0 0