

CPT_S 260 Intro to Computer Architecture

Lecture 27

Single Cycle MIPS
March 23, 2022

Ganapati Bhat
School of Electrical Engineering and Computer Science
Washington State University

Announcements

- **Mid term exam 2**



- Friday, April 1, 2022
- Format will be similar to exam 1
- Tentative topics: MIPS, digital logic, single cycle MIPS implementation

- **Final exam**

- May 4, 2022
- 7:30 pm to 9:30 pm
- If you're taking Calculus 3, please reach out to me

Recap: Sequential Elements

  - **Flip flops: stores data in a circuit**
 - Uses a clock signal to determine when to update the stored value
 - Edge-triggered: update when Clk changes from 0 to 1



Single Cycle MIPS Processor Design

- **Topics:**

- Introduction
- Instruction Execution
- Use Digital Blocks to Build the Data Path!
 - » Arithmetic/Logic
 - » Load/Store
 - » Branch/Jump
- Control Unit
 - » ALU Control
 - » Datapath Control
- Complete Hardware


Introduction

- **CPU performance factors**
 - Instruction count
 - » Determined by ISA and compiler
 - CPI and Cycle time
 - » Determined by CPU hardware
- **We will examine two MIPS implementations**
 - A simplified version
 - A more realistic pipelined version
- **Simple subset, shows most aspects**
 - Memory reference: lw, sw
 - Arithmetic/logical: add, sub, and, or, slt
 - Control transfer: beq, j


Instruction Execution

- **PC → instruction memory, fetch instruction**
- **Register numbers → register file, read registers**
- **Depending on instruction class**
 - Use ALU to calculate
 - » Arithmetic result
 - » Memory address for load/store
 - » Branch target address
 - Access data memory for load/store
 - $PC \leftarrow \text{target address or } PC + 4$

CPU Overview

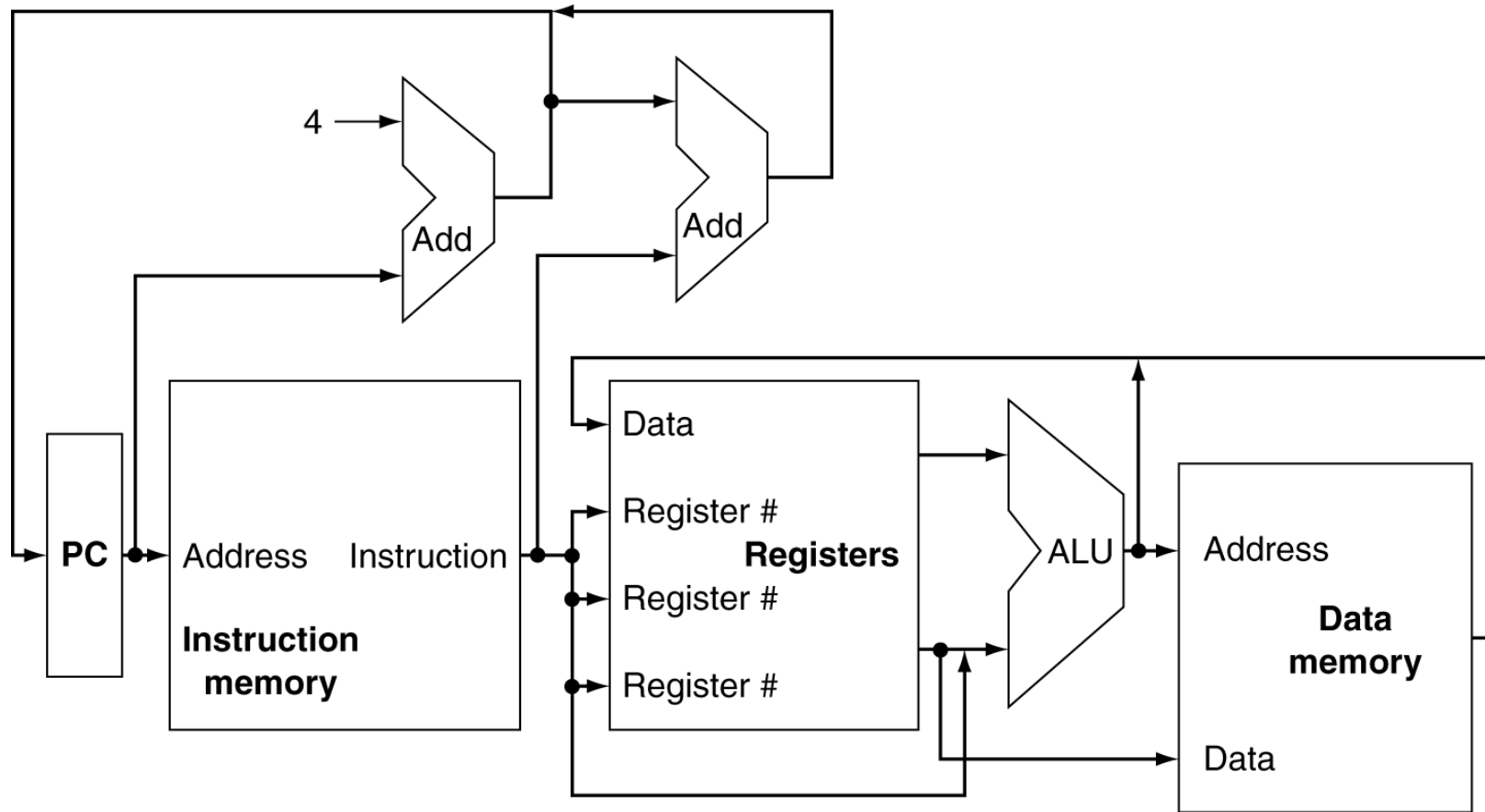


Multiplexers

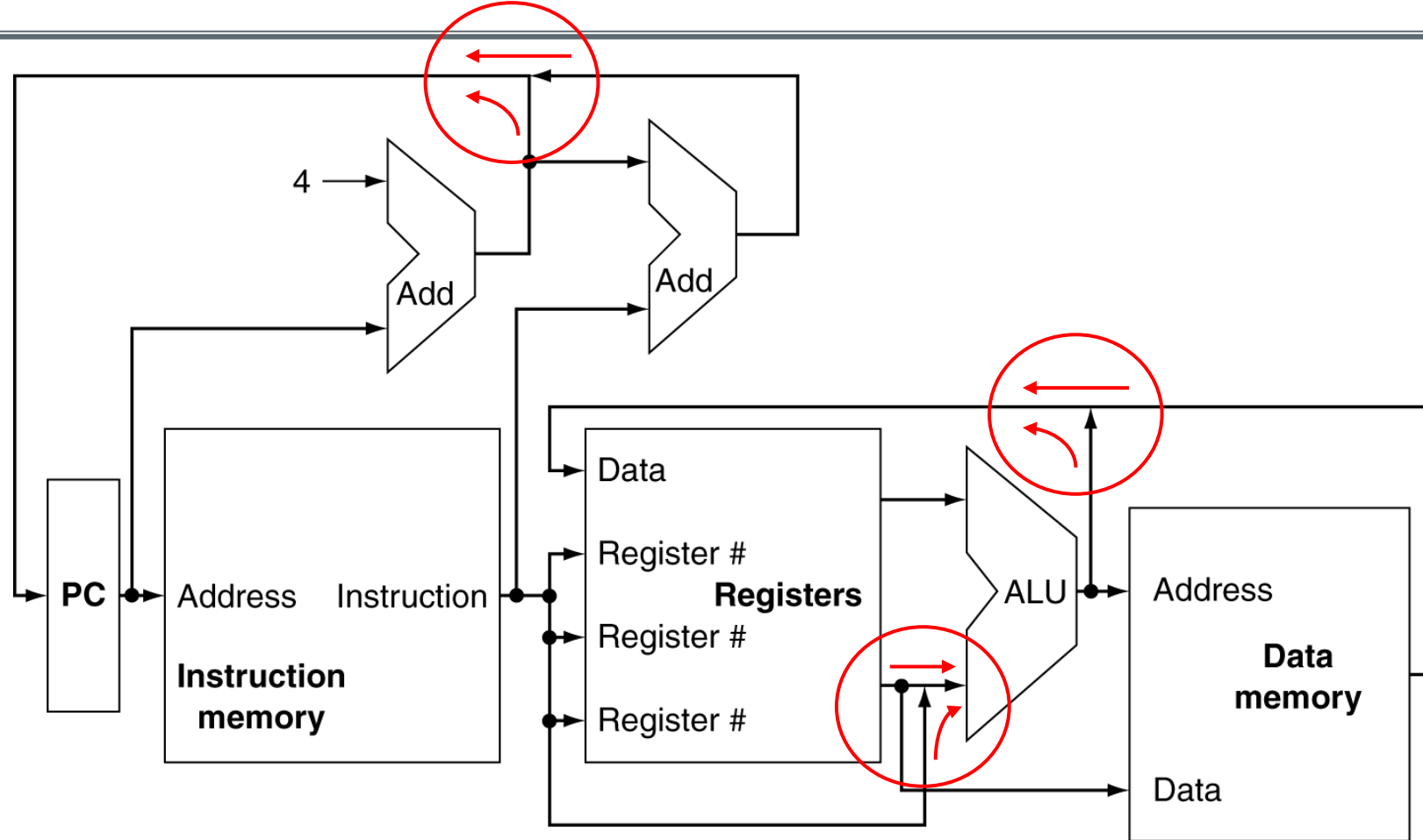

- **Can't just join wires together**
 - **Use multiplexers**

Control

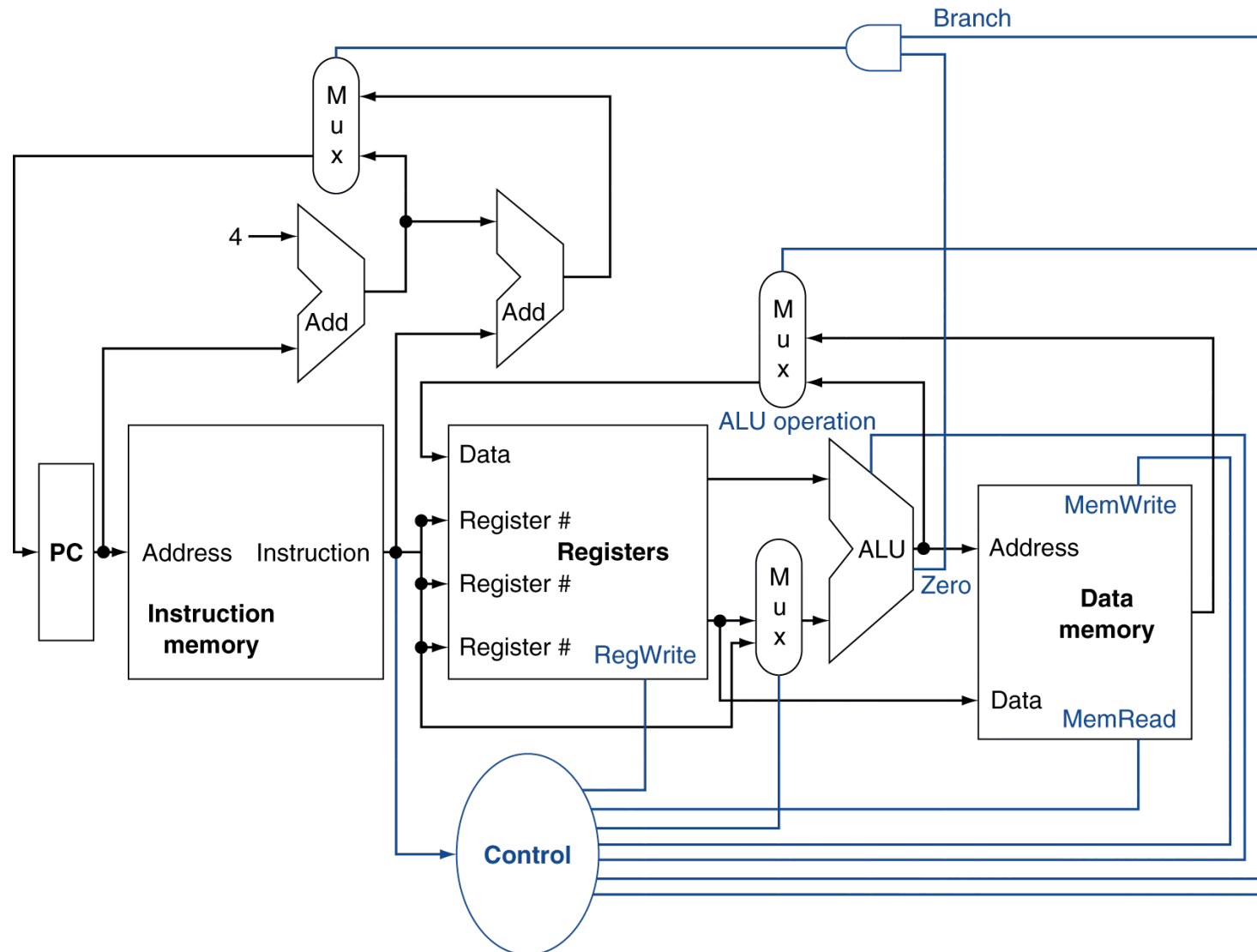

Building a Datapath


- **Datapath**

- Elements that process data and addresses in the CPU
 - » Registers, ALUs, mux's, *memories*, ...

- **We will build a MIPS datapath incrementally**


- Refining the overview design

Instruction Fetch

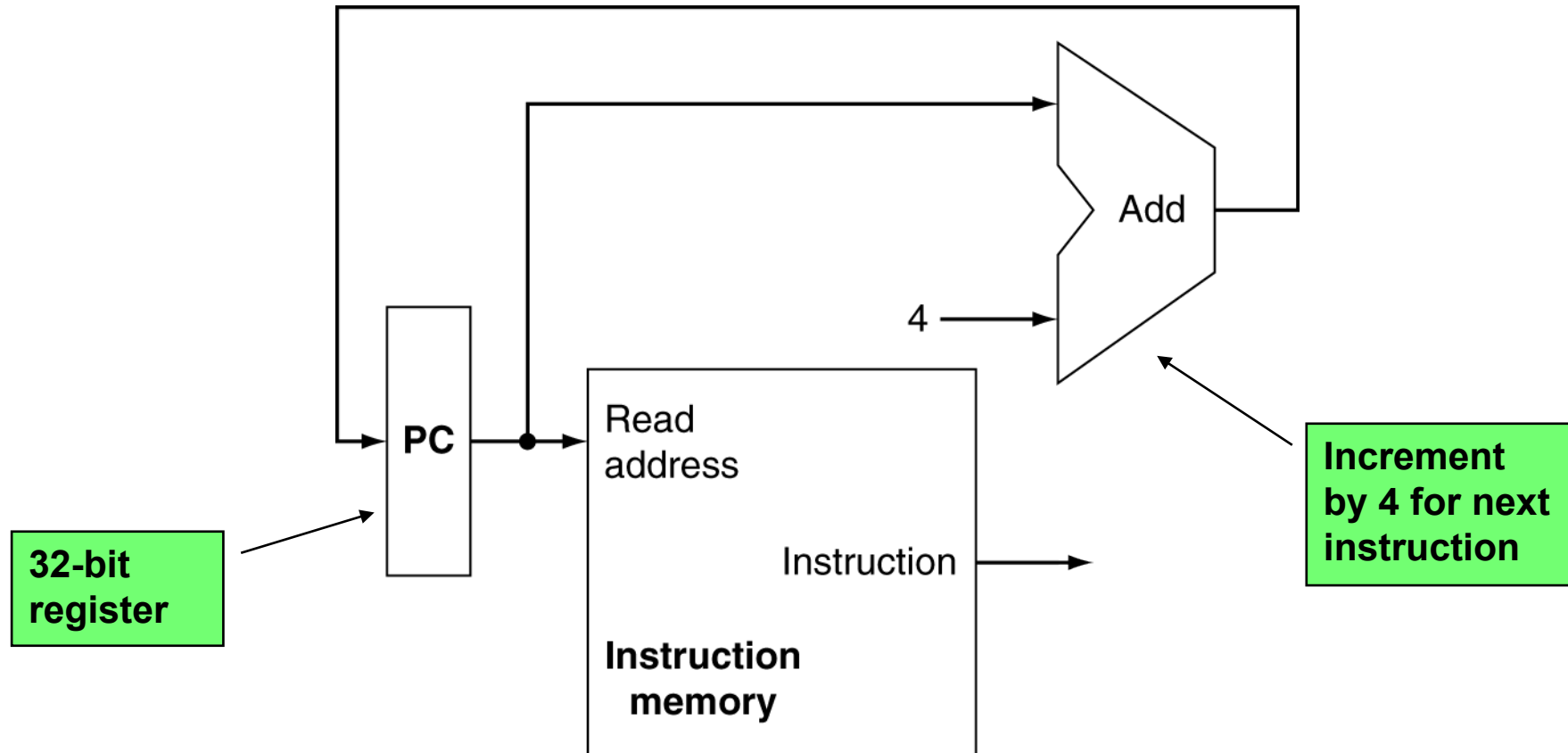


R-Format Instructions

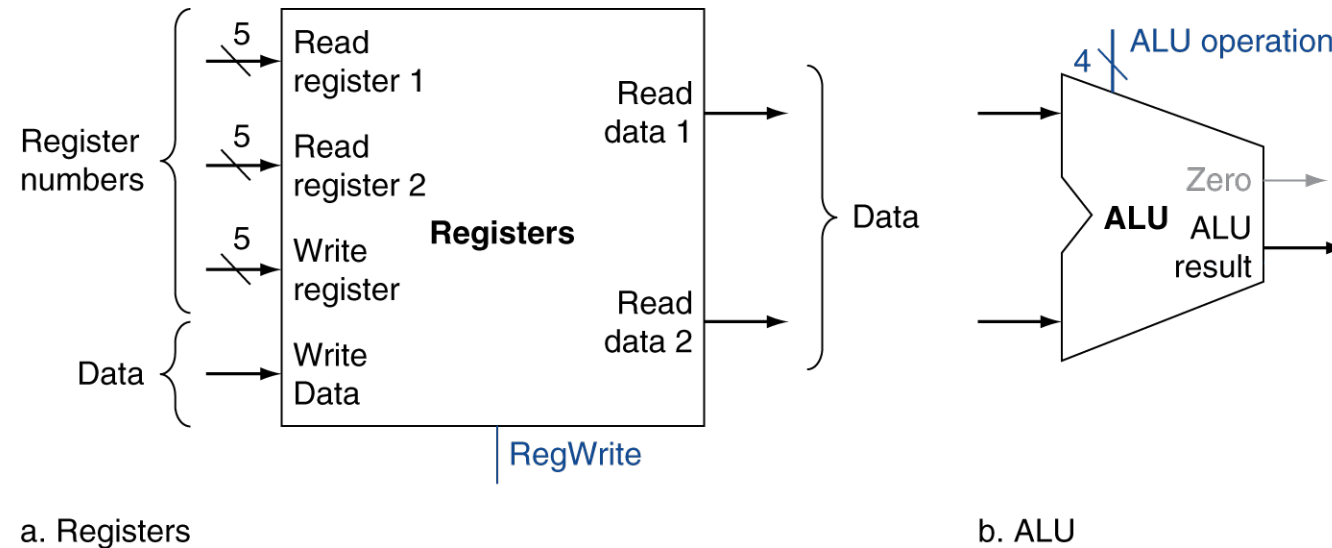- Read two register operands
- Perform arithmetic/logical operation
- Write register result



Load/Store Instructions

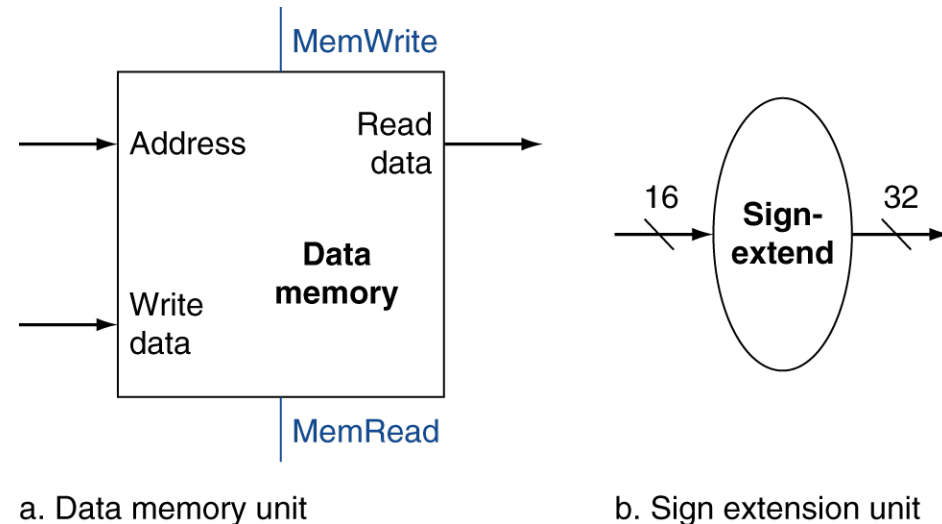
- Read register operands
- Calculate address using 16-bit offset
 - Use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory



Branch Instructions

- **Read register operands**
- **Compare operands**
 - Use ALU, subtract and check Zero output
- **Calculate target address**
 - Sign-extend displacement
 - Shift left 2 places (word displacement)
 - Add to PC + 4
 - » Already calculated by instruction fetch

Branch Instructions

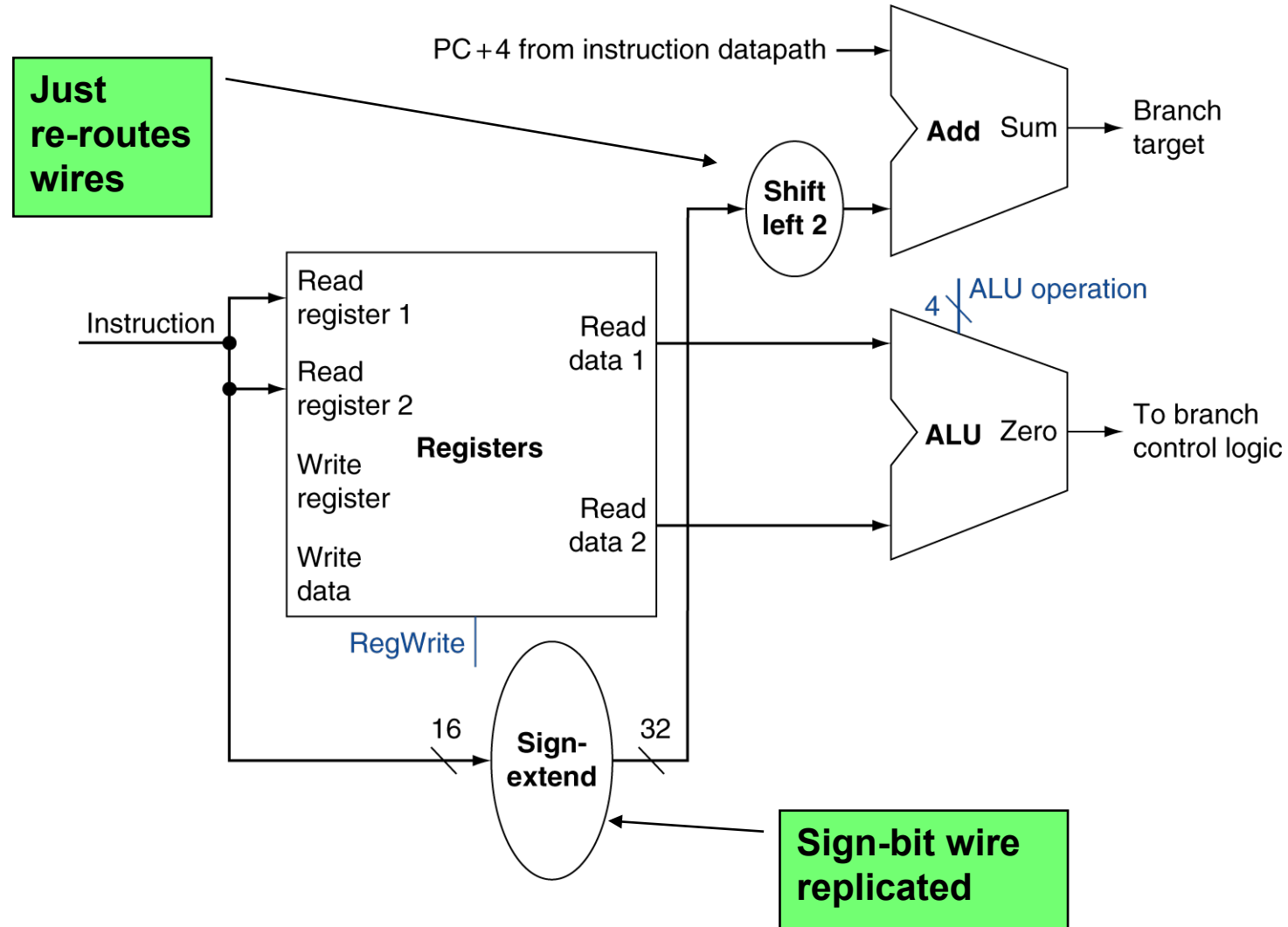


Composing the Elements

- **First-cut data path does an instruction in one clock cycle**
 - Each datapath element can only do one function at a time
 - Hence, we need separate instruction and data memories
- **Use multiplexers where alternate data sources are used for different instructions**

R-type/ Load-Store Datapath

- Operations of arithmetic-logical (or R-type) instructions and the memory instructions are quite similar
- The arithmetic-logical instructions use the ALU, with the inputs coming from the two registers
- The memory instructions can also use the ALU to do the address calculation
 - Second input is the sign-extended 16-bit off set field from the instruction
- The value stored into a destination register comes from the ALU (for an R-type instruction) or the memory (for a load).

R-Type/Load/Store Datapath

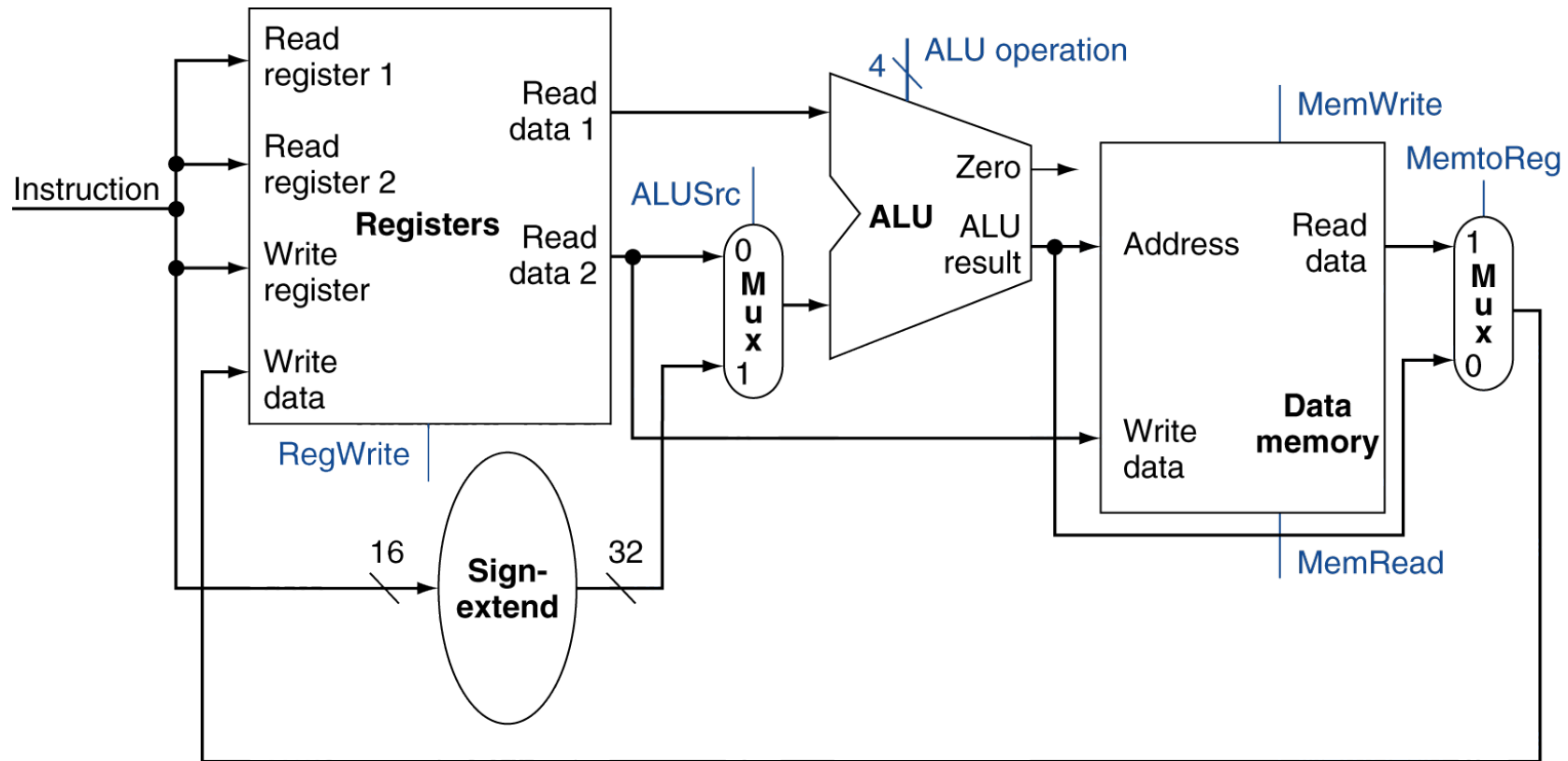

Full Datapath

