

**School of Electrical Engineering and Computer Science**

**CptS 260 - Introduction to Computer Architecture  
Fall 2019**

**Midterm #2**

**Fall 2019**

**Duration: 50 minutes**

NAME:

*Solution*

ID:

	Total Points	Earned
Problem 1	15	
Problem 2	28	
Problem 3	20	
Problem 4	15	
Problem 5	15	
Problem 6	15	
Bonus	3	

Notes:

- You may bring a calculator to the test. No other resources are allowed! In particular, NO textbook, lecture notes, internet access, smartphone usage, etc. are allowed!
- Make sure to write your name and WSU ID down on the first page
- Show your work for each question.
- MIPS reference data is provided!

1. (15 points) Consider the following Boolean Expression:

$$F = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}B\bar{C}$$

Assume that you are allowed to use only these three gate types: NOT, 2-input AND, 2-input OR. Furthermore, assume that the latency of each gate is 300 ps (i.e., 300 picoseconds).

5 pts a. Simplify function 'F' as much as possible. What is the final simplified expression of 'F'?


5 pts b. Draw equivalent digital circuit for the simplified function.

5 pts c. What is the overall latency of the simplified circuit?

a.  $F = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}B\bar{C} = \bar{C}(\bar{A}\bar{B} + A\bar{B} + \bar{A}B)$


(5)  $= \bar{C}(\bar{A}(B + \bar{B}) + A\bar{B}) = \bar{C}(\bar{A} + A\bar{B}) = \bar{C}(\bar{A} + \bar{B})$

$$F = \bar{A}\bar{C} + \bar{B}\bar{C}$$

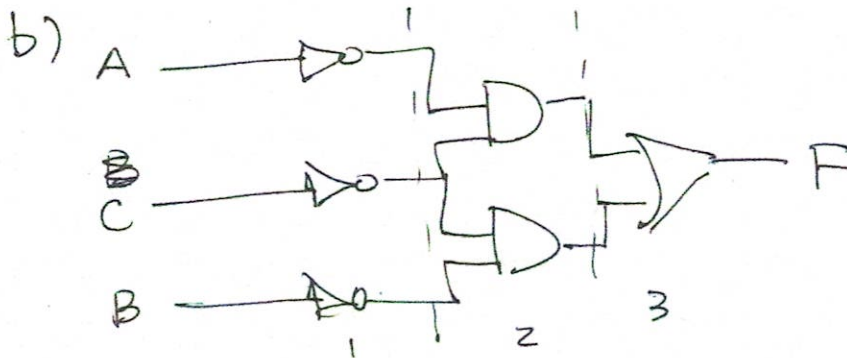

c)  $3 \times 300 \text{ ps} = 900 \text{ ps}$

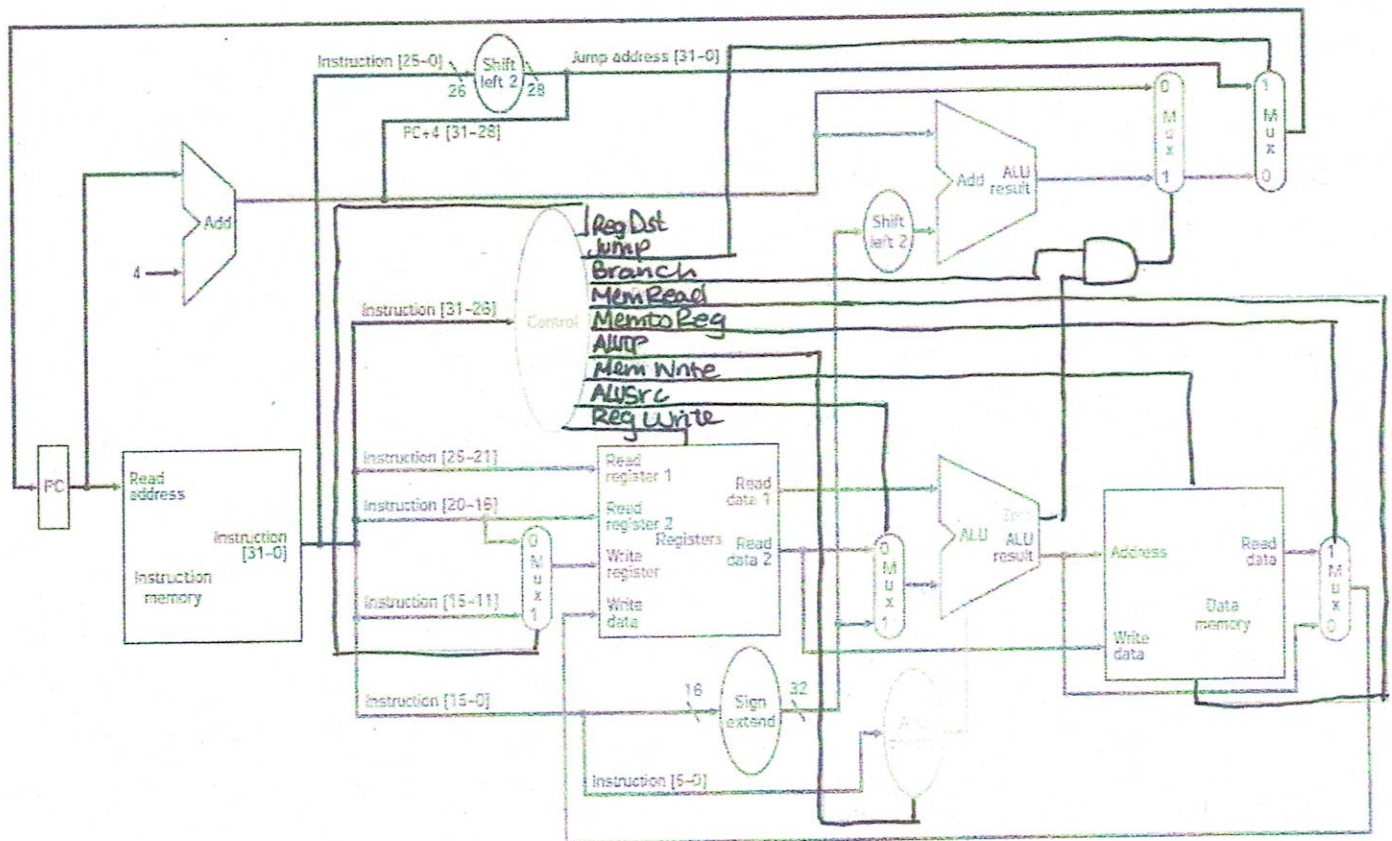2. (20 Points) Consider the following simple single cycle MIPS architecture, which is the same architecture discussed in the class.



- a. (8 pts) What is the value (i.e., '0', '1', 'x') of each one of the following control signals during execution of 'AND' instruction?

RegDst = 1  
Branch = 0  
MemtoReg = 0  
AluSrc = 0

Jump = 0  
MemRead = 0  
MemWrite = 0  
RegWrite = 1

- b. (8 pts) What is the value (i.e., '0', '1', 'x') of each one of the following control signals during execution of 'SW' instruction?

RegDst = X  
Branch = 0  
MemtoReg = X  
AluSrc = 1

Jump = 0  
MemRead = 0  
MemWrite = 1  
RegWrite = 0

- c. (8 pts) What is the value (i.e., '0', '1', 'x') of each one of the following control signals during execution of 'LW' instruction?

RegDst = 0

Branch = 0

MemtoReg = 1

AluSrc = 1

Jump = 0

MemRead = 1

MemWrite = 0

RegWrite = 1


- d. (4 pts) Assume instruction "AND \$t0, \$t1, \$t2" is located at address (1000)<sub>D</sub> (i.e., address 1000 in decimal) in the instruction memory. What is the value of PC in decimal after this instruction is executed?

$PC \rightarrow PC + 4 \rightarrow (1004)_D$



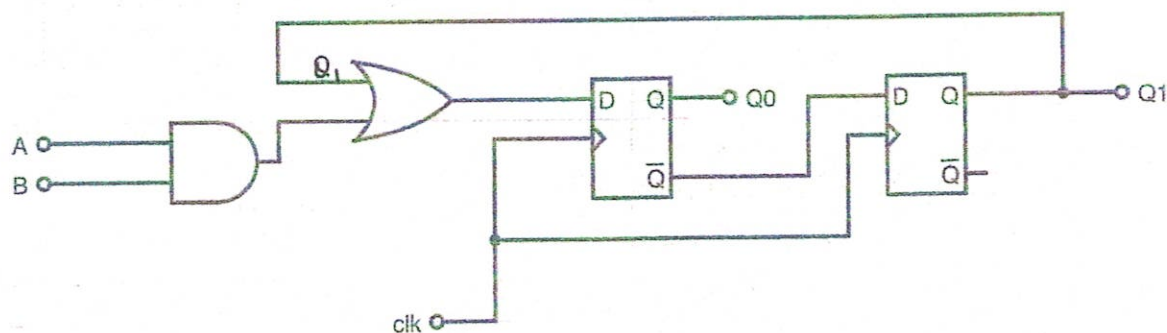3. (20 Points) The following figure shows a sequential circuit with three D Flip Flops with a common input clock. Note that the inverted output of the first flip-flop ( $\bar{Q}_0$ ) is connected to the input of the second flip-flop (D input of the far right flip flop). Assume that the flip flops are initialized at '1'. That is,  $Q_1 = Q_0 = 1$  during Cycle 0. This means the output of this circuit is initially  $Q_1Q_0 = '11'$ .


- Compute the value of each output signal ( $Q_1$ , and  $Q_0$ ) for 10 cycles using the table below.
- Convert the 2-bit binary  $Q_1Q_0$  to its equivalent decimal in the table.
- How many unique output states (i.e.,  $Q_1Q_0$ ) does this circuit produce after the initial state?



Clock Cycle	A	B	$Q_1$	$Q_0$	Decimal ( $Q = Q_1Q_0$ )
0	0	1	1	1	3
1	1	1	0	1	1
2	1	0	0	0	0
3	1	1	1	1	3
4	0	0	0	1	1
5	0	0	0	0	0
6	0	1	1	0	2
7	0	1	1	1	3
8	1	1	0	1	1
9	1	1	0	1	1
10	0	0	0	0	0

C. 0, 1, 2, 3.

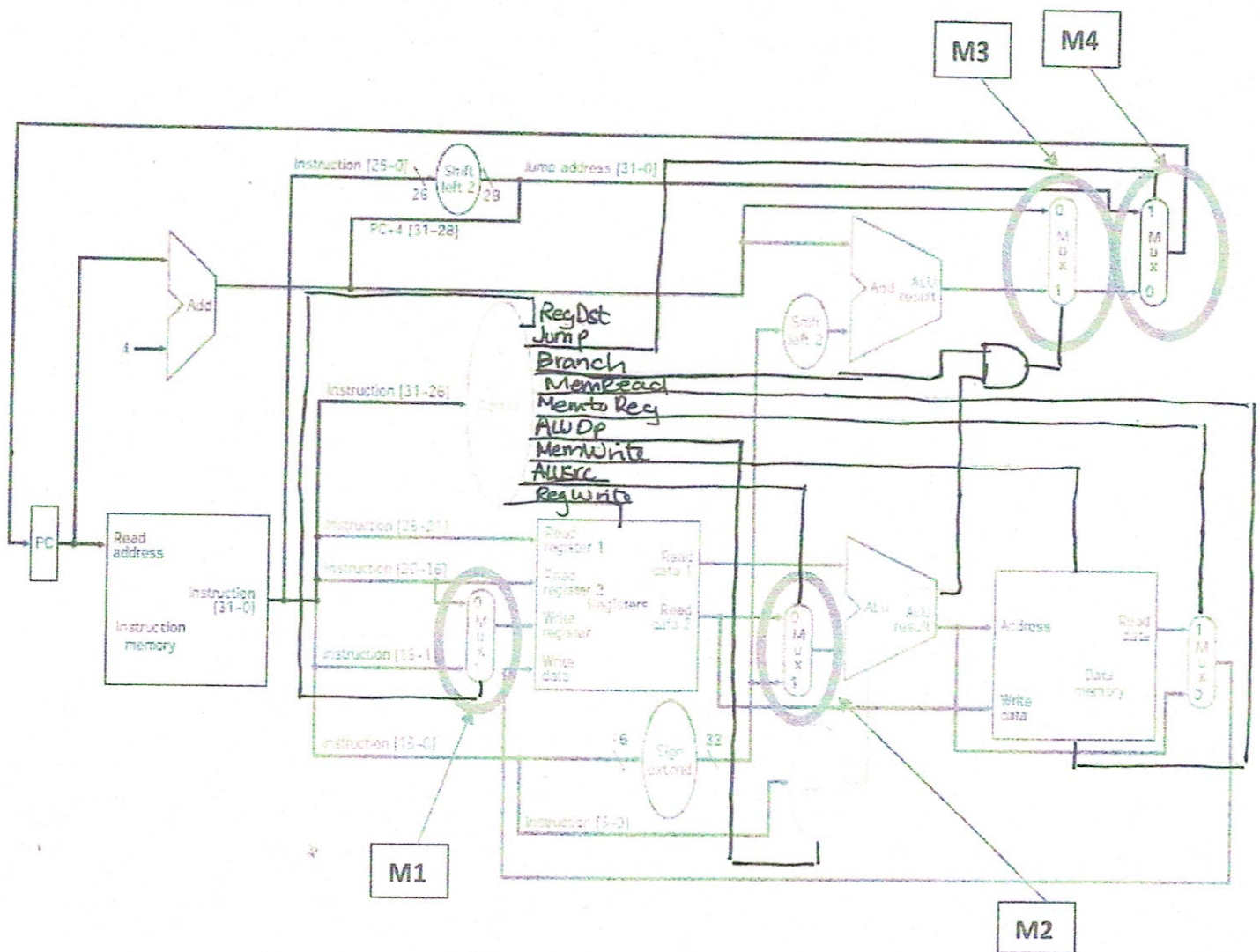4. (15 points) Consider the following single cycle MIPS architecture and instruction format, which is the same architecture discussed in the class.



Instruction Format for R-Type, I-Type, and Jump instructions

<b>R</b>	opcode	rs	rt	rd	shamt	funct
	31	26 25	21 20	16 15	11 10	6 5 0
<b>I</b>	opcode	rs	rt	immediate		
	31	26 25	21 20	16 15	0	
<b>J</b>	opcode	address				
	31	26 25	0			

Assume that the following instruction is in the datapath to execute. The instruction is located in address  $(1000)_D$  (i.e., address 1000 decimal) in the instruction memory. We also know that  $\$t1 = (10)_D$ , and  $\$t2 = (24)_D$ .

BEQ  $\$t1, \$t2, 10$

- (3) a. What is the value of PC after this instruction is executed?

$$PC \rightarrow PC + 4 = (1004)_D$$

- b. What is the value of selection pin for each multiplexer in the datapath (0 or 1). The MUXs are labeled as M1, M2, M3, and M4.

3 each

M1: X

M2: 0

M3: 0

M4: 0



5. (15 points) The following MIPS assembly code is expected to implement the 'for' loop mentioned below. There are four mistakes in the assembly code that you need to find. Assume that the base address of array 'A' is in register \$s0. Find the mistakes and write correct instruction with correct arguments for each.

```
for (i=0; i<100; i++)
{
    A[i] = 256;
}
```

```
li    $t0, $s0
li    $t1, 100d
sll   $t1, $t1, 4
add   $t1, $t1, $s0
ori   $t2, $zero, 256d
```

top:

```
sltu  $t3, $s0, $t1
beq   $t3, $zero, done
```

```
sw    $t2, 12($t0)
```

```
addi  $t0, $t0, 1
```

```
j     top
```

done:

4 X

sll \$t1, \$t1, 4 → sll \$t1, \$t1, 2

4 X

sltu \$t3, \$s0, \$t1 → sltu \$t3, \$t0, \$t1

beq \$t3, \$zero, done

sw \$t2, 12(\$t0) → sw \$t2, 0(\$t0)

addi \$t0, \$t0, 1 → addi \$t0, \$t0, 4

j top

done:

1pt  
for  
correction

- 2 pts for error
- 2 pts for correction



6. (15 points) Write a Boolean Sum of Product (SOP) expression for this truth table, then simplify that expression as much as possible. Draw the circuits for simplified expressions.


A	B	C	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + ABC$$

$$(\bar{A} + A)\bar{B}\bar{C} + ABC$$

(5) pts  $\bar{A}\bar{B}\bar{C} + AB(\bar{C} + C)$

$$\bar{A}\bar{B}\bar{C} + AB$$

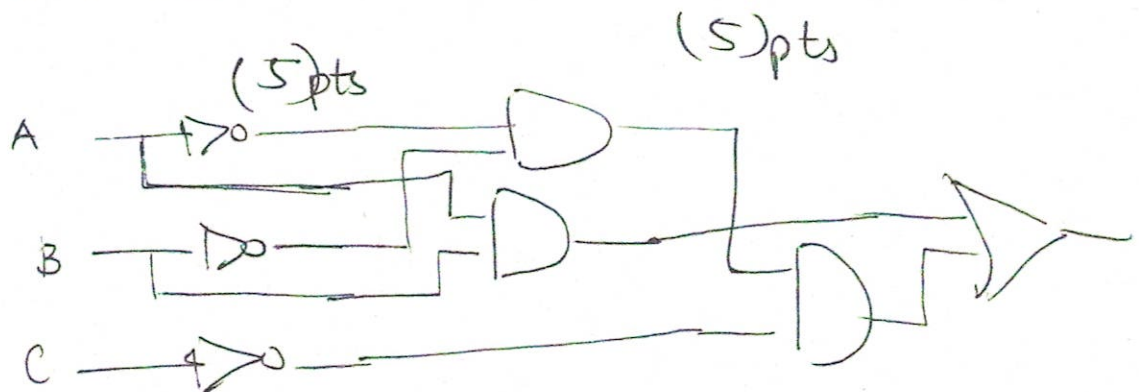

OR 3 input AND gate for  $\bar{A}\bar{B}\bar{C}$ .

**Bonus Question: (3 points)**

Mr Brown was killed on Sunday afternoon. The wife said she was reading a book. The butler said He was taking a shower. The chef said he was making breakfast. The maid said she was folding clothes, and the gardener said he was planting tomatoes. Who did it?

The Chef  
breakfast in the afternoon.

**Boolean Expression Rules:**

$$A + \bar{A} = 1$$

$$A \cdot \bar{A} = 0$$

$$\bar{\bar{A}} = A$$

$$A \cdot (A + B) = A$$

$$A + AB = A$$

$$A + \bar{A}B = A + B$$

$$A + A = A$$

$$A \cdot A = A$$

$$A \cdot 0 = 0$$

$$A + 1 = 1$$

$$A \cdot 1 = A$$

$$A + 0 = A$$