

CPT_S 260 Intro to Computer Architecture

Lecture 23

Digital Design II
March 4, 2022


Ganapati Bhat
School of Electrical Engineering and Computer Science
Washington State University

Announcements


- Homework 4 due next week
- No quiz this week

Recap: NAND and NOR

 - NAND : NOT of AND : $A \text{ nand } B = \overline{A \cdot B}$
- NOR : NOT of OR : $A \text{ nor } B = \overline{A + B}$
- NAND and NOR are *universal gates*, i.e., they can be used to construct any complex logical function




NAND

 

NOR

Recap: Stateful (Sequential) Digital Circuits

 - This circuit utilizes one of the wire loops from the right to the left providing feedback
- “flip flop” building blocks to preserve state.



R-S Latch

Input		Output
R	S	Q
1	1	Q_{prev}
1	0	1
0	1	0
0	0	Invalid

Truth Tables

- *Truth table* – a tabular listing of the values of a function for all possible combinations of values on its arguments
- Example: Truth tables for the basic logic operations:

AND		
X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1


OR		
X	Y	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1

NOT	
X	$Z = \overline{X}$
0	1
1	0

Checkpoint – Truth tables

- $S = (A + B) \cdot (\bar{A} + \bar{B})$

- $C = A \cdot B$

 

Selecting

- **Selecting of data or information is a critical function in digital systems and computers**
- **Circuits that perform selecting have:**
 - A set of information inputs from which the selection is made
 - A single output
 - A set of control lines for making the selection
- **Logic circuits that perform selecting are called *multiplexers***
- **Selecting can also be done by three-state logic or transmission gates**

Multiplexers

- A multiplexer selects information from an input line and directs the information to an output line
- A typical multiplexer has n control inputs ($S_{n-1}, \dots S_0$) called *selection inputs*, 2^n information inputs ($I_{2^n-1}, \dots I_0$), and one output Y
- A multiplexer can be designed to have m information inputs with $m < 2^n$ as well as n selection inputs


2-to-1-Line Multiplexer

- Since $2 = 2^1$, $n = 1$
- The single selection variable S has two values:
 - $S = 0$ selects input I_0
 - $S = 1$ selects input I_1

- The equation:

$$Y = \bar{S}I_0 + SI_1$$

- The circuit:

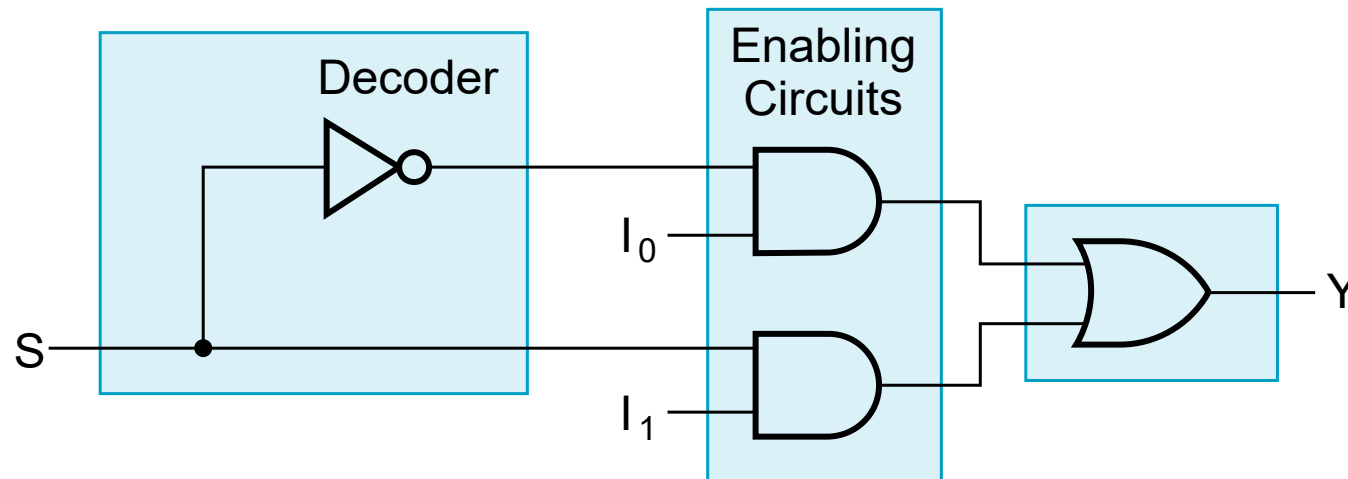


Decoders

- **Decoding** - the conversion of an n -bit input code to an m -bit output code with $n \leq m \leq 2^n$ such that each valid code word produces a unique output code
- Circuits that perform decoding are called *decoders*
- Here, functional blocks for decoding are
 - called n -to- m line decoders, where $m \leq 2^n$, and
- **Example: 2-to-4 decoder:**



EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

(a)

 


(b)


Decoder

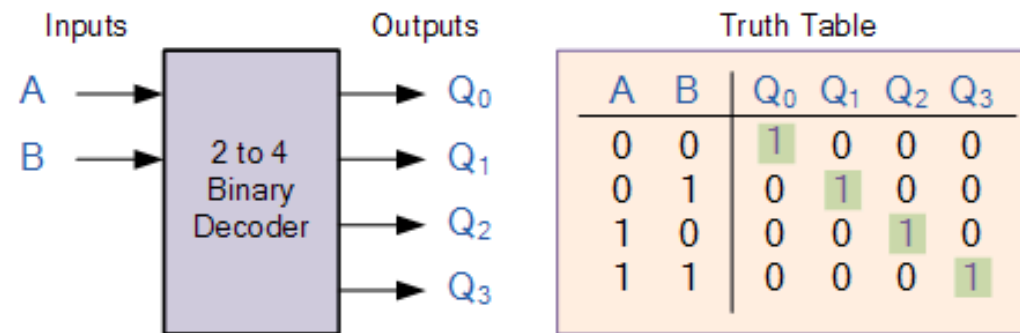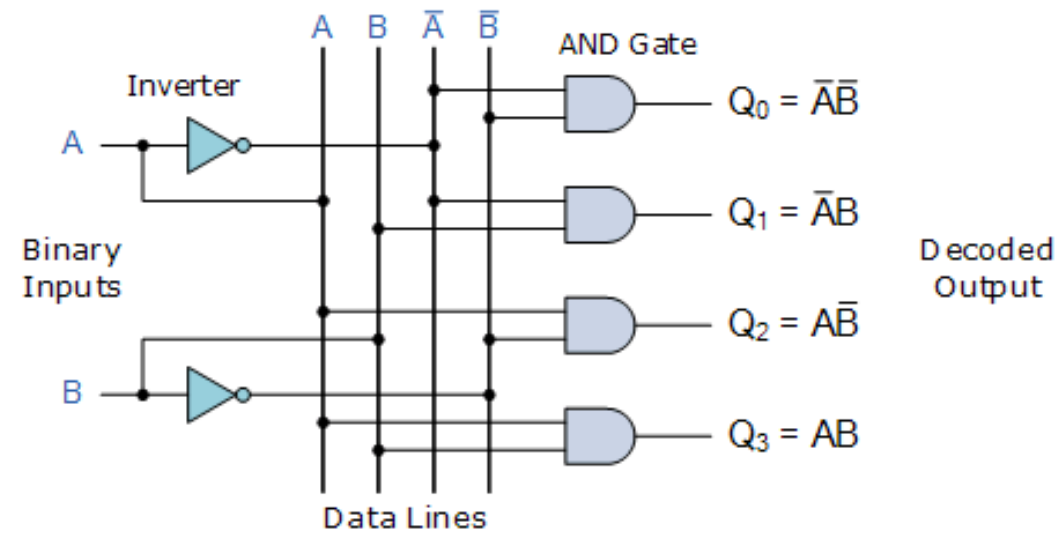

3-to-8 Decoder

 


Memory Address Decoding

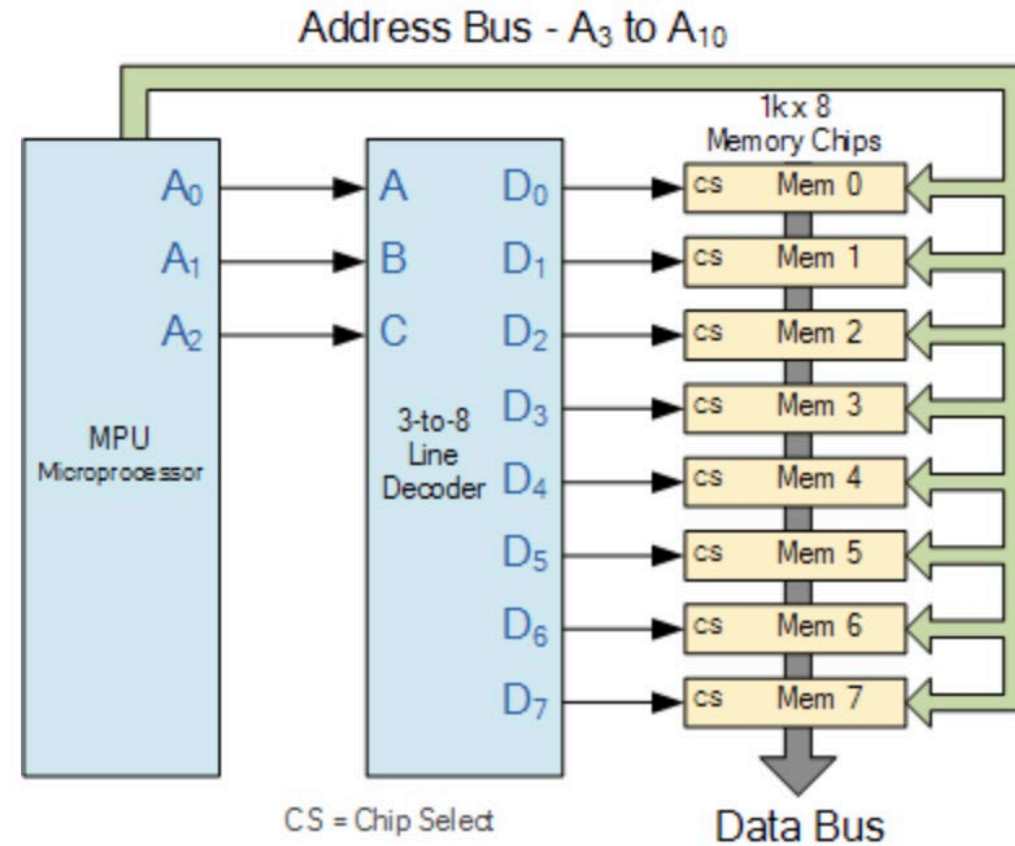

Encoder


- **Encoding - the opposite of decoding - the conversion of an m -bit input code to a n -bit output code with $n \leq m \leq 2^n$ such that each valid code word produces a unique output code**
- **An encoder has 2^n (or fewer) input lines and n output lines which generate the binary code corresponding to the input values**
- **Takes ALL its data inputs one at a time and then converts them into a single encoded output.**

Encoder

 

Inputs				Outputs	
D_3	D_2	D_1	D_0	Q_1	Q_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1
0	0	0	0	x	x

Encoder Digital Circuit

 

Logic Simplification

Rules of Boolean Algebra

- **Associative Law of multiplication**

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

- **Distributive Law of multiplication**

$$A + BC = (A + B) \cdot (A + C)$$

- **Annulment law:**

$$A \cdot 0 = 0$$

$$A + 1 = 1$$

- **Identity law:**

$$A \cdot 1 = A$$

$$A + 0 = A$$

Rules of Boolean Algebra

- **Complement law:**

$$\begin{aligned}A + \bar{A} &= 1 \\A \cdot \bar{A} &= 0\end{aligned}$$

- **Double negation law:**

$$\bar{\bar{A}} = A$$

- **Absorption law:**

$$\begin{aligned}A \cdot (A + B) &= A \\A + AB &= A \\A + \bar{A}B &= A + B\end{aligned}$$



- **Idempotent law:**

$$\begin{aligned}A + A &= A \\A \cdot A &= A\end{aligned}$$

De Morgan's Laws


- Transformation rules that help simplification of negations
- Statement:
  
$$\overline{AB} = \bar{A} + \bar{B}$$
$$\overline{(A + B)} = \bar{A} \cdot \bar{B}$$



Simplification Using Boolean Algebra



 
- A simplified Boolean expression uses the fewest gates possible to implement a given expression.



Simplification Using Boolean Algebra

▪ $AB + A(B + C) + B(B + C)$

   - (distributive law)
 - » $AB + AB + AC + BB + BC$
- ($BB = B$)
 - » $AB + AB + AC + \textcolor{red}{B} + BC$
- ($AB + AB = AB$)
 - » $\textcolor{red}{AB} + AC + B + BC$
- ($B + BC = B$)
 - » $AB + AC + \textcolor{red}{B}$
- ($AB + B = B$)
 - » $\textcolor{red}{B} + AC$



Examples

- $[A\bar{B}(C + BD) + \bar{A}\bar{B}]C$
- $\bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}C + ABC$
- $\overline{AB + AC} + \bar{A}\bar{B}C$

Standard Forms of Boolean Expressions

- **All Boolean expressions, regardless of their form, can be converted into either of two standard forms:**
 - The sum-of-products (SOP) form (minterms)
 - The product-of-sums (POS) form (maxterms)
- **Standardization makes the evaluation, simplification, and implementation of Boolean expressions much more systematic and easier**

Sum of Products

- **Minterm Expressions**
- If input is 0 we take the complement of the variable
- If input is 1 we take the variable as is
- To get the desired canonical SOP expression we will add the minterms (product terms) for which the output is 1

$$F = \bar{A}B + A\bar{B} + AB$$

A	B	F	Minterm
0	0	0	A'B'
0	1	1	A'B
1	0	1	AB'
1	1	1	AB

Product of Sums

- **Maxterm Expressions**
- If input is 1, we take the complement of the variable
- If input is 0, we take the variable as is
- To get the desired canonical POS expression we will multiply the maxterms (sum terms) for which the output is 0

$$F = (A + B) \cdot (\bar{A} + \bar{B})$$

A	B	F	Minterm
0	0	0	A'B'
0	1	1	A'B
1	0	1	AB'
1	1	1	AB